

ECET 337
Low and High Pass Filter Project Demonstration


A. Filter Specifications

Filter Design Problem

Enter the first five non-zero digits of your Purdue ID number: **You entered 12345**

You are correct. [Previous Tries](#)

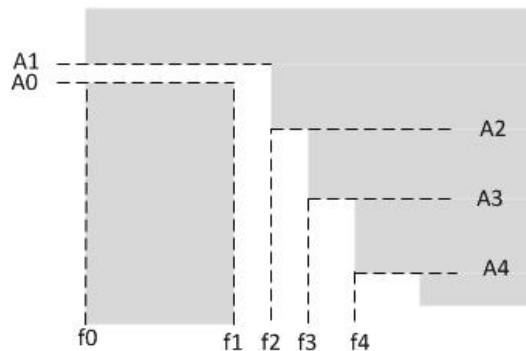Build a filter with the following characteristics.



	$f(\text{Hz})$	$A(\text{dB})$	Matlab	Multisim	Hardware
0					
1					
2					
3					
4					

1. Pass band ripple ___ dB to ___ dB => Type of filter _____
2. $A_o =$ _____
3. Pick $f_{-3\text{dB}} =$ _____
4. A second order filter will give _____ A 4th order filter will give _____.
Pick _____

B. Coefficients

Table 7-5 Higher order filter damping (α) and low pass frequency correction factors

Filter Order	Section		Bessel	Butterworth	1 dB Chebyshev	2 dB Chebyshev
3	1	α	—	—	—	—
		k_{lp}	0.753	1	2.212	3.105
	2	α	1.447	1	0.496	0.402
4		k_{lp}	0.687	1	1.098	1.095
	2	α	1.916	1.848	1.275	1.088
		k_{lp}	0.696	1	1.992	2.146
	2	α	1.241	0.765	0.281	0.224
		k_{lp}	0.621	1	1.060	1.057

$A_o =$ _____

$a_1 =$ _____



$k_{lp1} =$ _____ $f_{-3dB} =$ _____

$a_2 =$ _____

$k_{lp2} =$ _____ $f_{-3dB} =$ _____

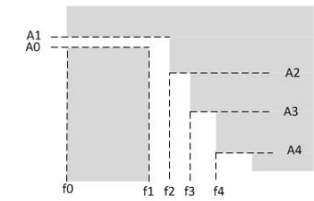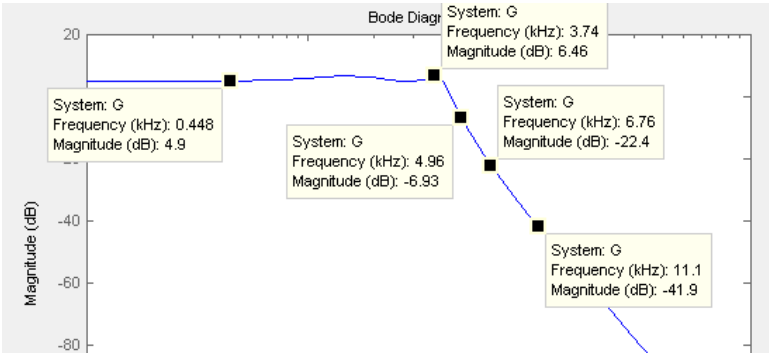C. Matlab

```
1 - clear
2 - format short G
3 - s=tf('s')
4
5 - Ao= _____;
6
7 - f3dB= _____;
8 - fo1=f3dB _____;
9 - wo1= _____;
10 - fo2= _____;
11 - wo2= _____;
12
13 - alpha1= _____;
14 - alpha2= _____;
15
16 - G=Ao*(wo1^2/(s^2+alpha1*wo1*s+wo1^2))*(wo2^2/(s^2+alpha2*wo2*s+wo2^2))
17 - ltiview('bode',G)
18
```



	f(Hz)	A(dB)	Matlab	Multisim	Hardware
0					
1					
2					
3					
4					

D. Sallen Key Design

Stage 1

$$f_{o1} = \underline{\hspace{2cm}}$$

Pick $C = 10 \text{ nF}$

$$R \underline{\hspace{2cm}}$$

$$A_{\text{int1}} = \underline{\hspace{2cm}}$$

Pick $R_{i1} = 10 \text{ k}\Omega$

$$R_{f1} = \underline{\hspace{2cm}}$$

Stage 2

$$f_{o2} = \underline{\hspace{2cm}}$$

Pick $C = 10 \text{ nF}$

$$R = \underline{\hspace{2cm}}$$

$$A_{\text{int2}} = \underline{\hspace{2cm}}$$

Pick $R_{i2} = 10 \text{ k}\Omega$


$$R_{f2} = \underline{\hspace{2cm}}$$

Gain stage



$$A_o = \underline{\hspace{2cm}}$$

Pick $R_{i3} = 10 \text{ k}\Omega$

$$R_{f3} = \underline{\hspace{2cm}}$$

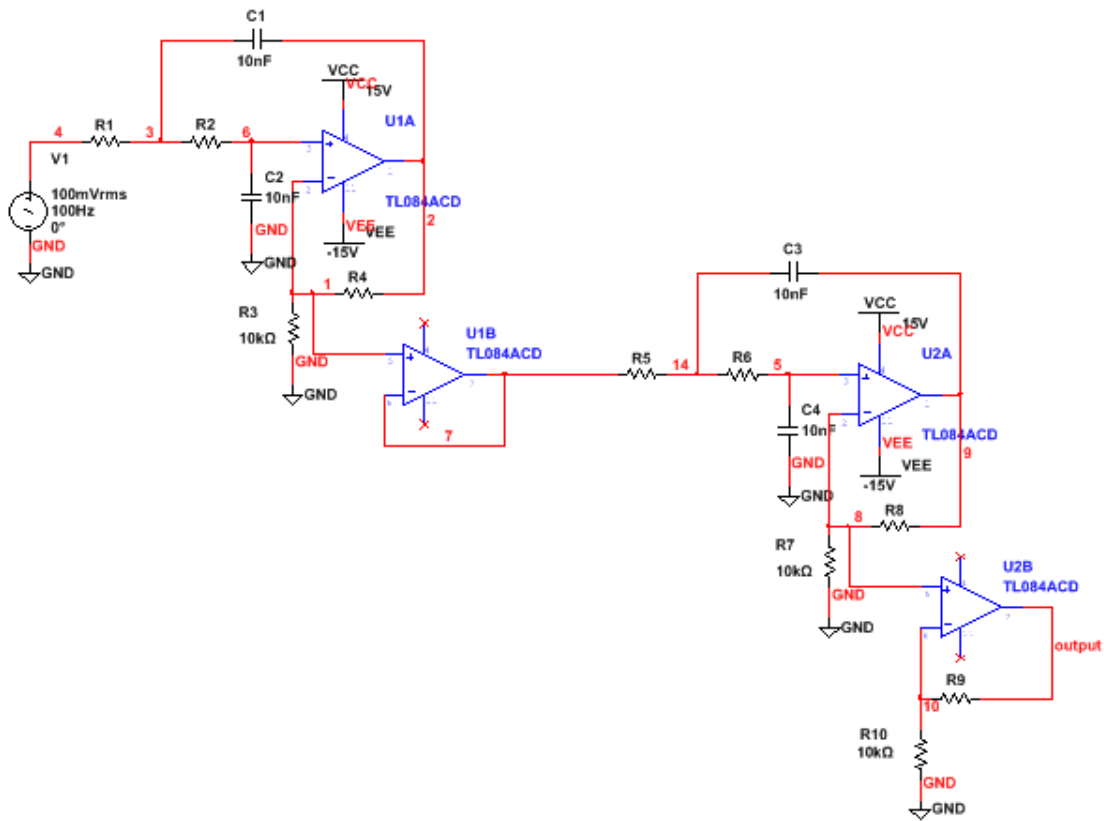

4thOrder2dB0nebyLP
AC Sweep

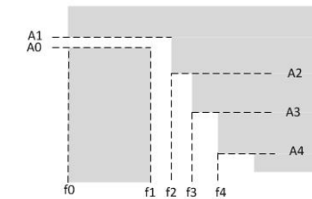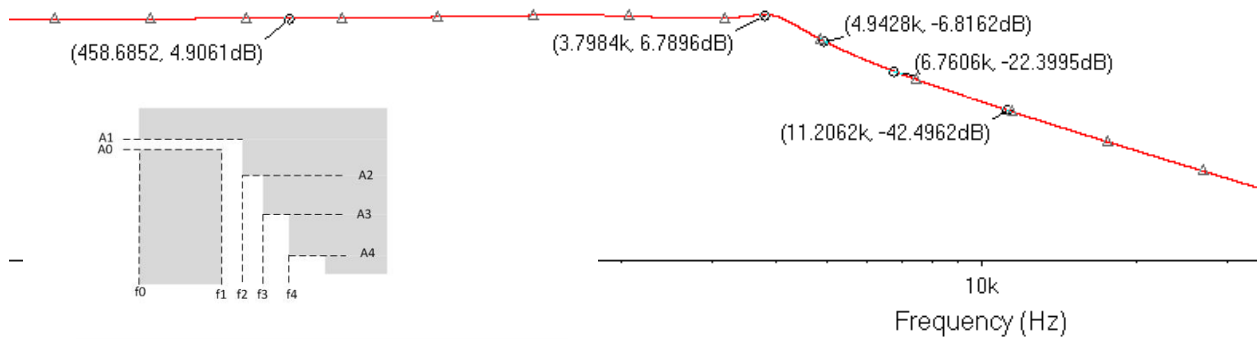

f(Hz)	A(dB)	Matlab	Multisim	Hardware
0				
1				
2				
3				
4				