

ECET 377
RLC Series Circuit Design Homework

name

1. Draw the schematic of an RLC circuit whose output follows the general shape of the square wave input, but may have ringing, or a quick or slow exponential rise to the same level as the input.
2. Determine the transfer function of this circuit in terms of R, L, and C.
3. Write the general second order transfer function.
4. The 5% settling time is the time from when the input step occurs until the output *settles* to within 5% of its final level. Look at Figure 1.



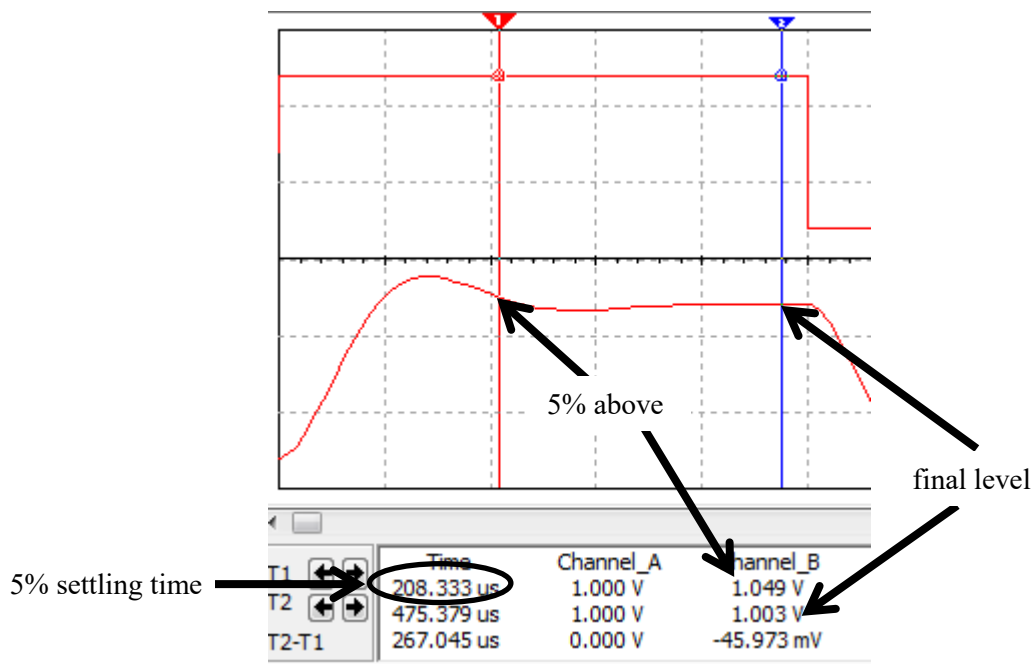


Figure 1 5% settling time measurement

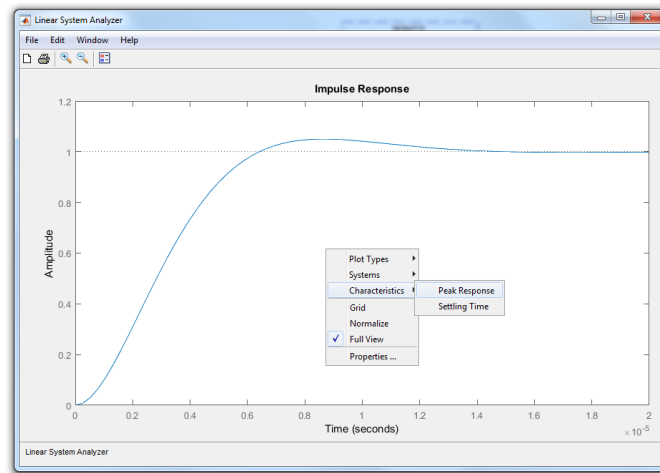
- 1) In **Matlab *ltiview***, right click on the plot and select: Characteristics > Settling Time



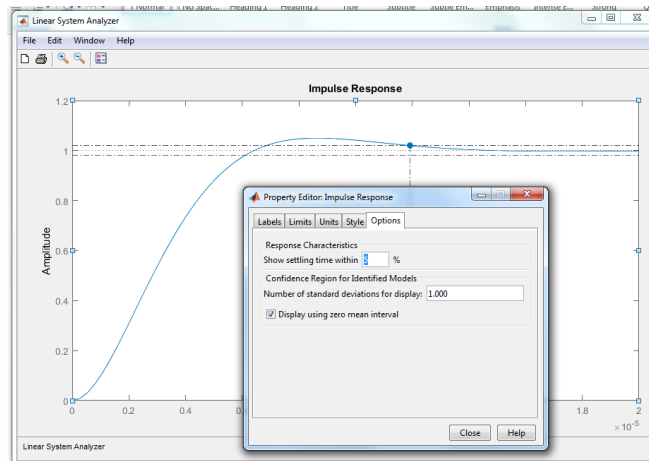- 2) Double click on the graph. Go to: Options > Change “Show settling time within” to 5% > Close



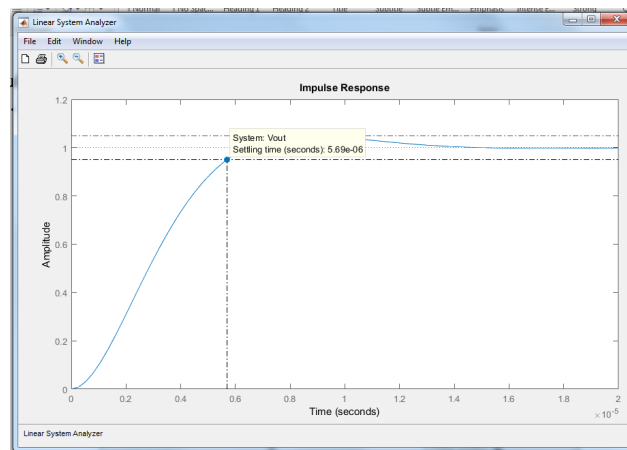- 3) Mouse over the point to see the settling time, or double click it to keep it on the screen to screenshot.



5. Using Multisim's Arbitrary Laplace Function with a 1 V square wave @ 1kHz, or Matlab's ltiview, $\xi = 0.99$, determine the response of your transfer for $f_o = 5$ kHz, then 20 kHz, then 80 kHz. Submit these three output plots. [Matlab produces a bad plot when $\xi = 1$, but is fine with 0.99, which is close enough.]
6. Which f_o produces the fastest settling time? (5kHz, 20kHz, 80kHz) _____
7. Using that f_o experimentally find the ξ that gives the fastest 5% settling time. Submit that transient response (or oscilloscope display), with cursors properly placed.

Settling time_{Laplace} = _____ ξ = _____

8. Determine the values for R, L, and C to implement your design. Since you have three components to set two parameters, pick $L = 33$ mH or $L = 450$ μ H. These are the two inductors you have. Show your work below. If your work produces unreasonably sized R or C, try the other inductor.

L = _____ R = _____ C = _____

9. Simulate your design using the closest standard values to the ones chosen in step 8. Use a 0 V to 1 V square wave input at 20 kHz. Capture and submit that schematic and transient analysis or oscilloscope display, with cursors properly placed.

5% settling time_{RLC} = _____