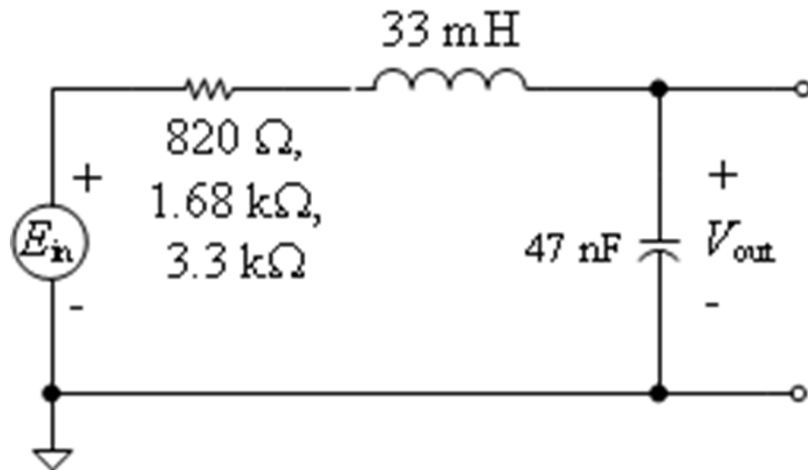



Low Pass – Quick Look



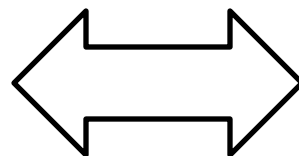1. V_{out} at DC ?
cap is _____
inductor is _____
2. V_{out} at high f ?
cap is _____
inductor is _____

$$\frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$




$$\frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

```

1- clear
2- format short G
3- s=tf('s')
4-
5- Ao=1;
6- fo=1e3;
7- wo=2*pi*fo;
8- zeta=0.707;
9-
10- G=Ao*wo^2/(s^2+2*zeta*wo*s+wo^2)
11-
12- opts = bodeoptions('cstprefs');
13- opts.FreqUnits = 'Hz';
14- opts.grid = 'on';
15- opts.PhaseWrapping = 'on';
16- opts.MagLowerLimMode = 'manual';
17- opts.MagLowerLim = -90;
18-
19- bodeplot(G,{1e2,1e6},opts);

```

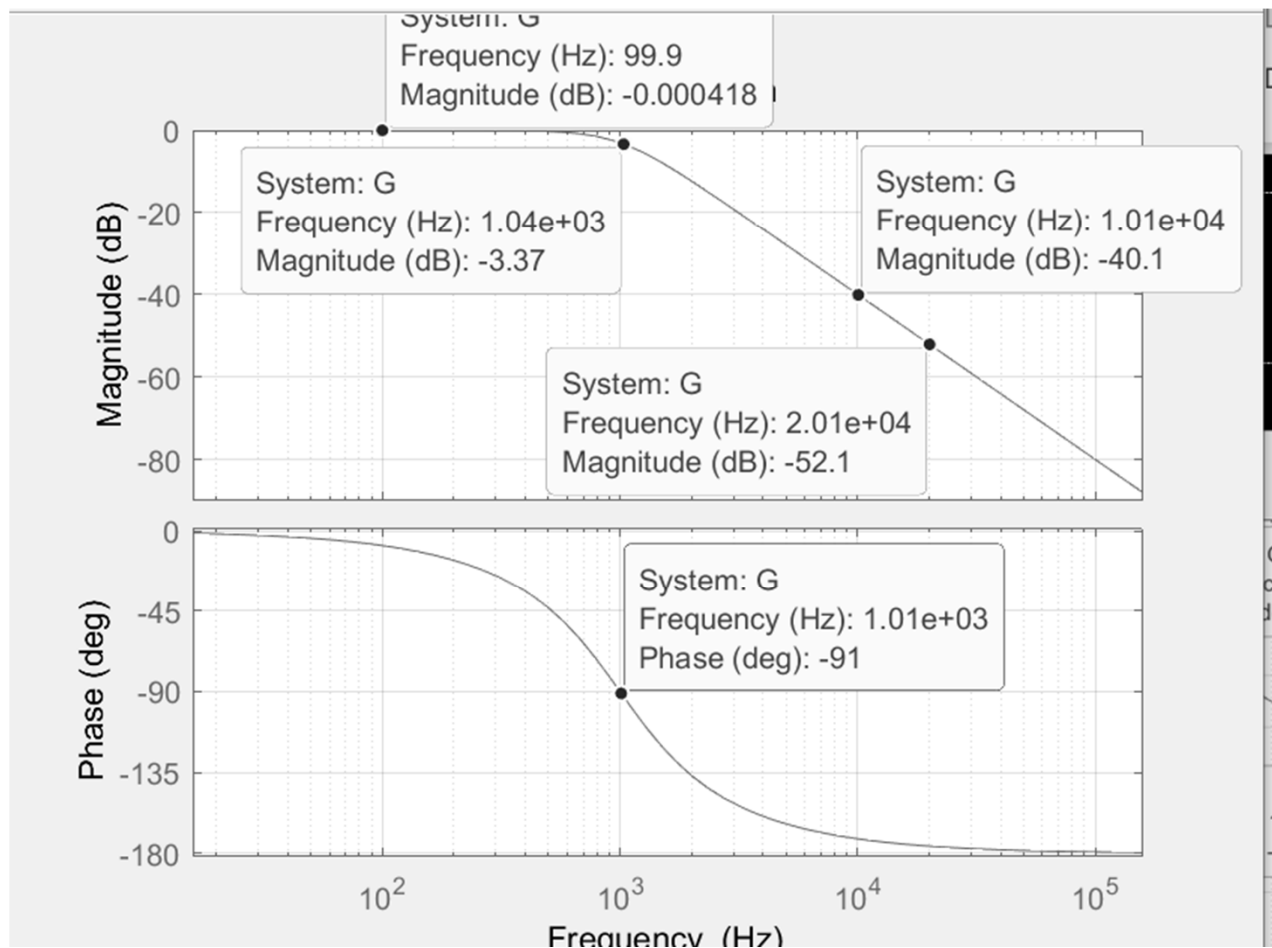

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = s^2 + \frac{R}{L}s + \frac{1}{LC}$$

$$\omega_n^2 = 2\zeta\omega_n =$$





$$\omega_n = \zeta =$$

$$f_o = \frac{1}{2*\pi\sqrt{LC}}$$


$$\zeta =$$

Butterworth low pass design

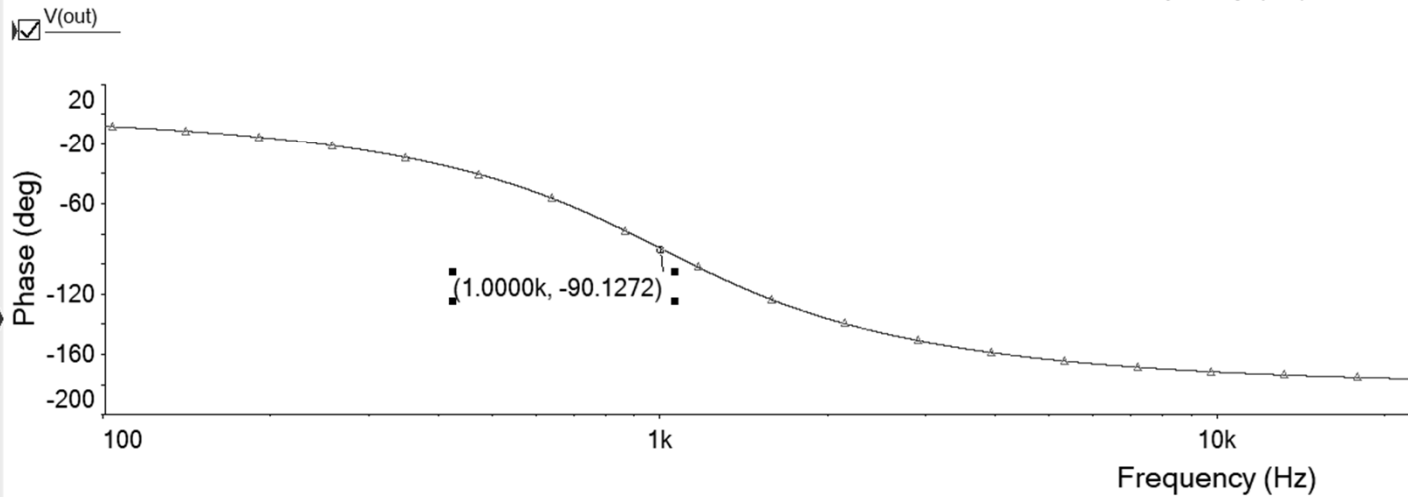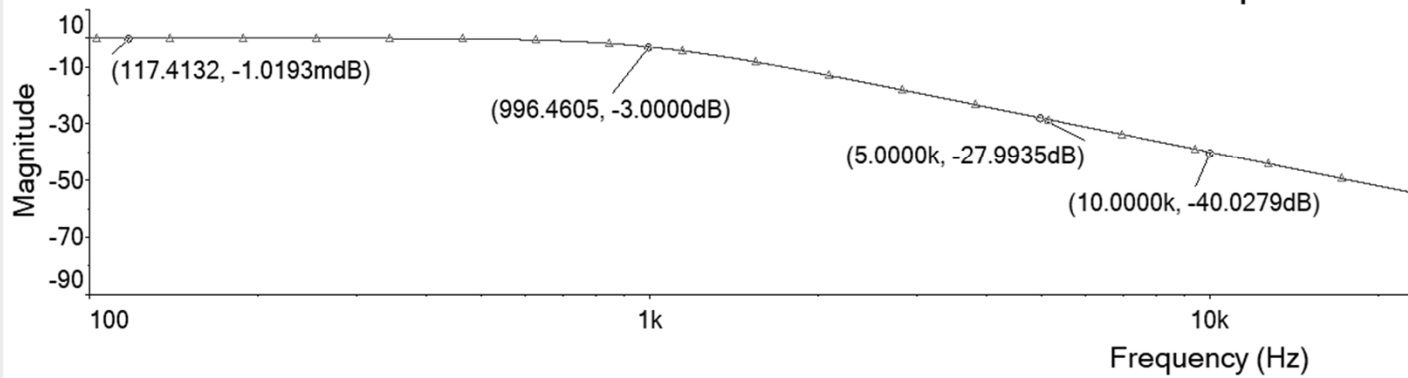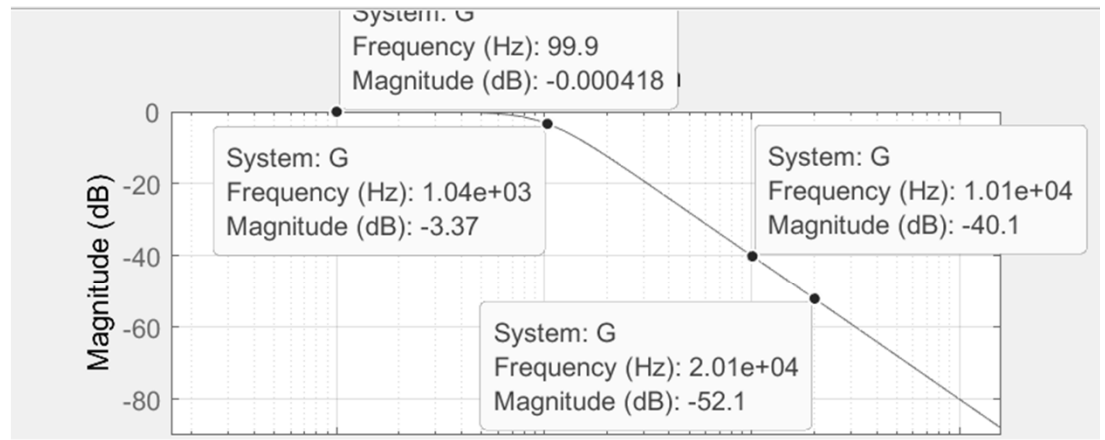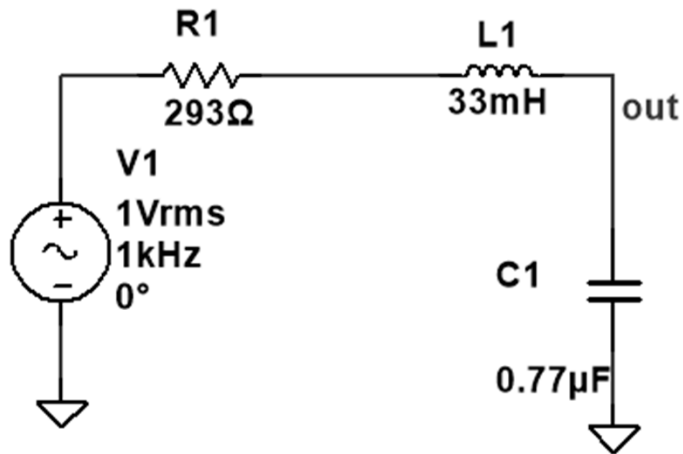- Given: $\zeta =$ $A_o = 1$ $f_o = 1$ kHz
- Pick $L = 33$ mH
- Calculate $C =$ _____ $f_o = \frac{1}{2 * \pi \sqrt{LC}}$
- Calculate $R =$ _____ $\zeta = \frac{1}{2} R \sqrt{\frac{C}{L}}$



High Pass – Quick Look

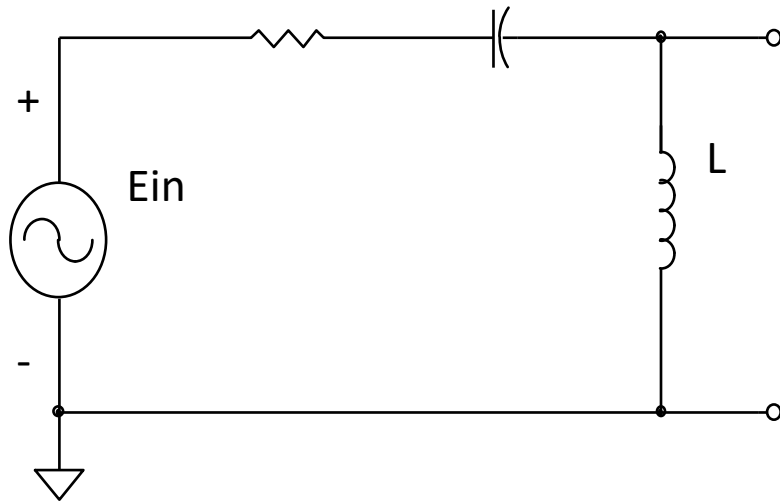

1. V_{out} at DC ?
cap is _____
inductor is _____


2. V_{out} at high f ?
cap is _____
inductor is _____

$$\frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\omega_n^2 =$$


$$2\zeta\omega_n =$$
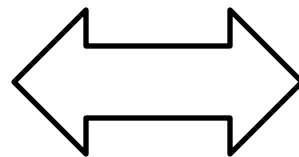
$$\frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



$$\frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

High Pass – transfer function

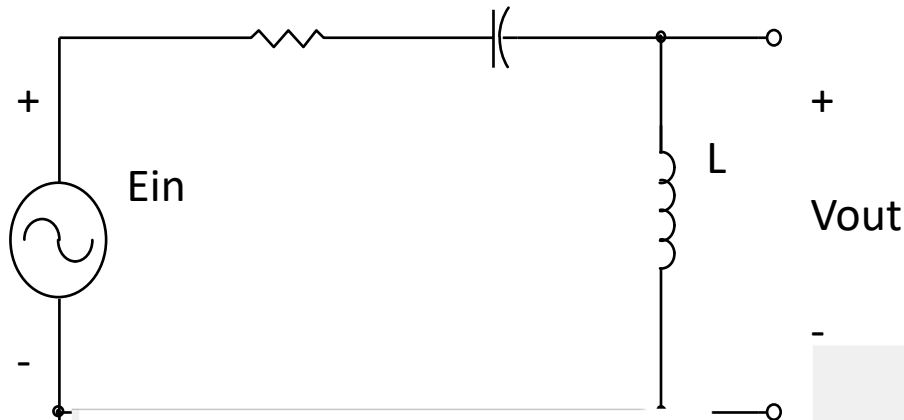

$$\frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


```
clear
format short G
s=tf('s')
```





```
Ao=1;
fo=1e3;
wo=2*pi*fo;
zeta=0.707;
```

```
G=Ao*s^2/(s^2+2*zeta*wo*s+wo^2)
```


```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G,{1e2,1e6},opts);
```

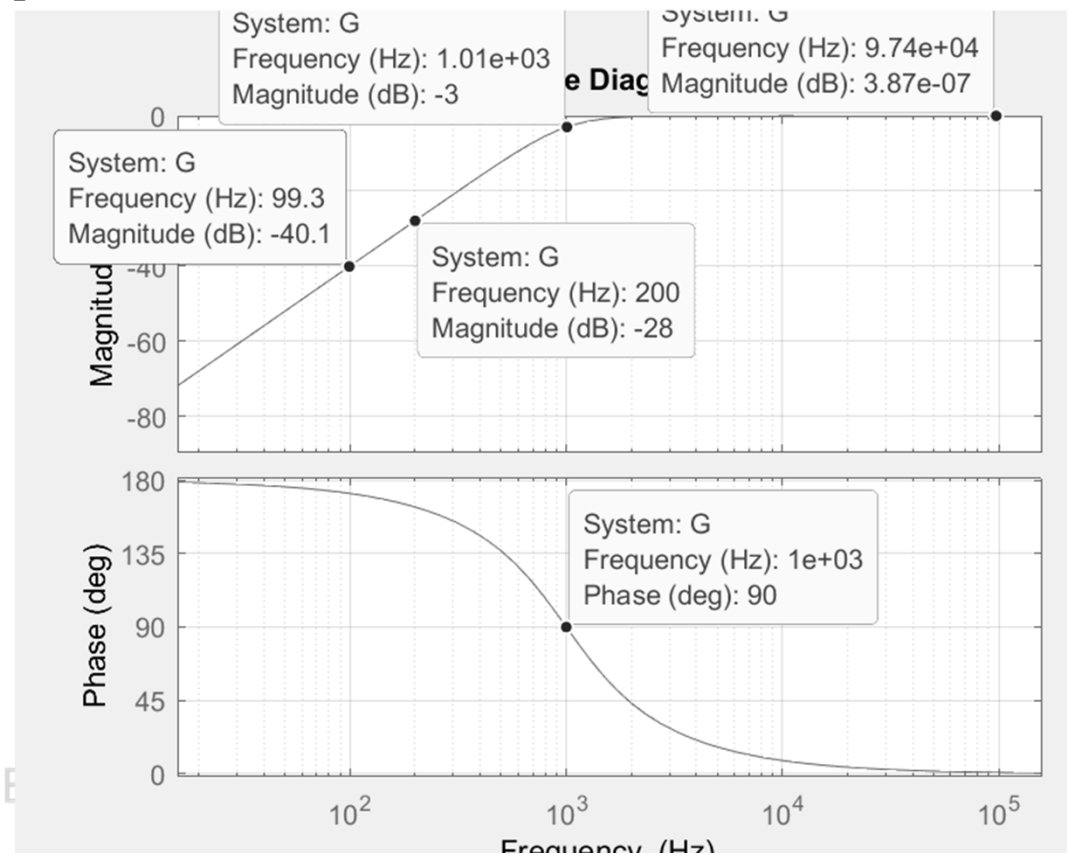

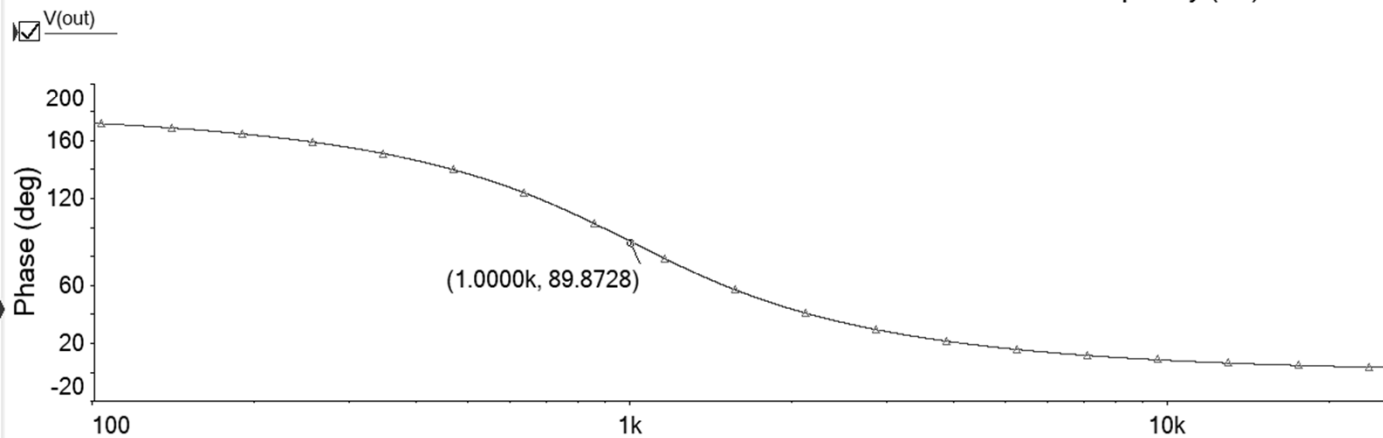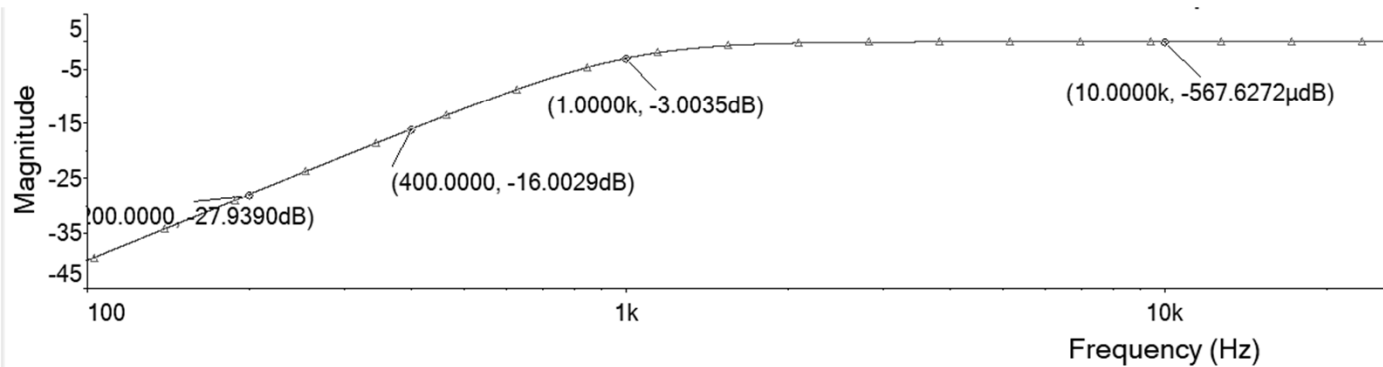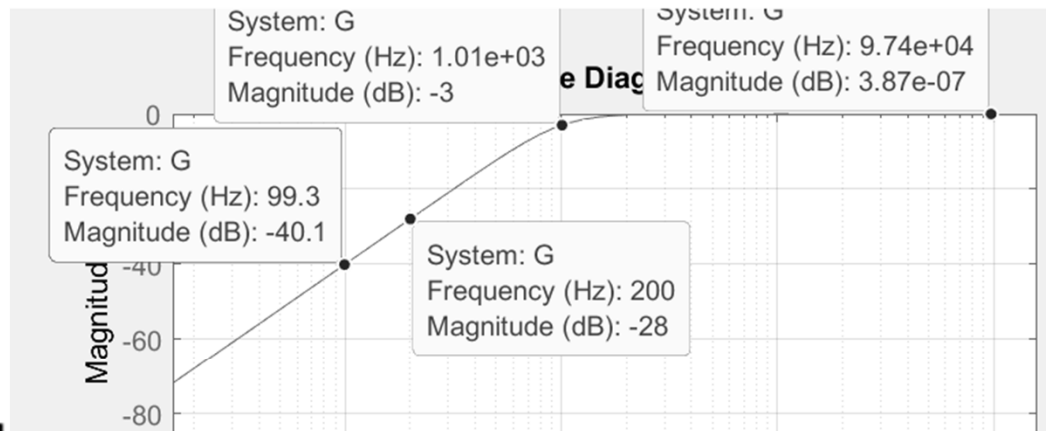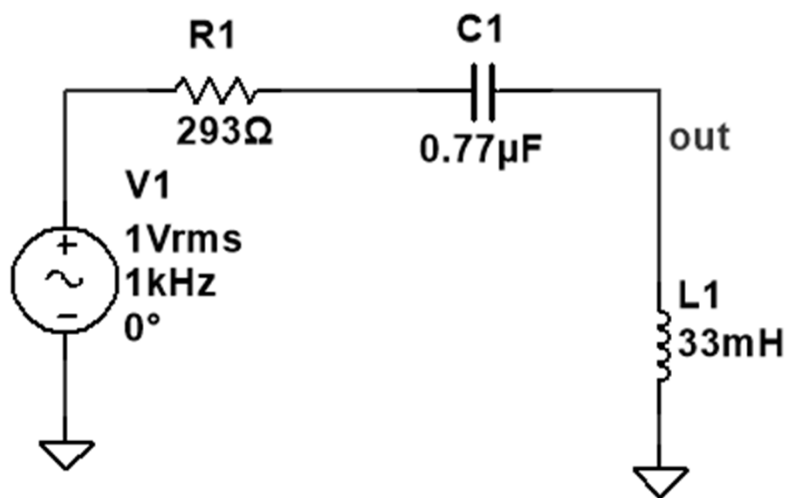

Band Pass – Quick Look

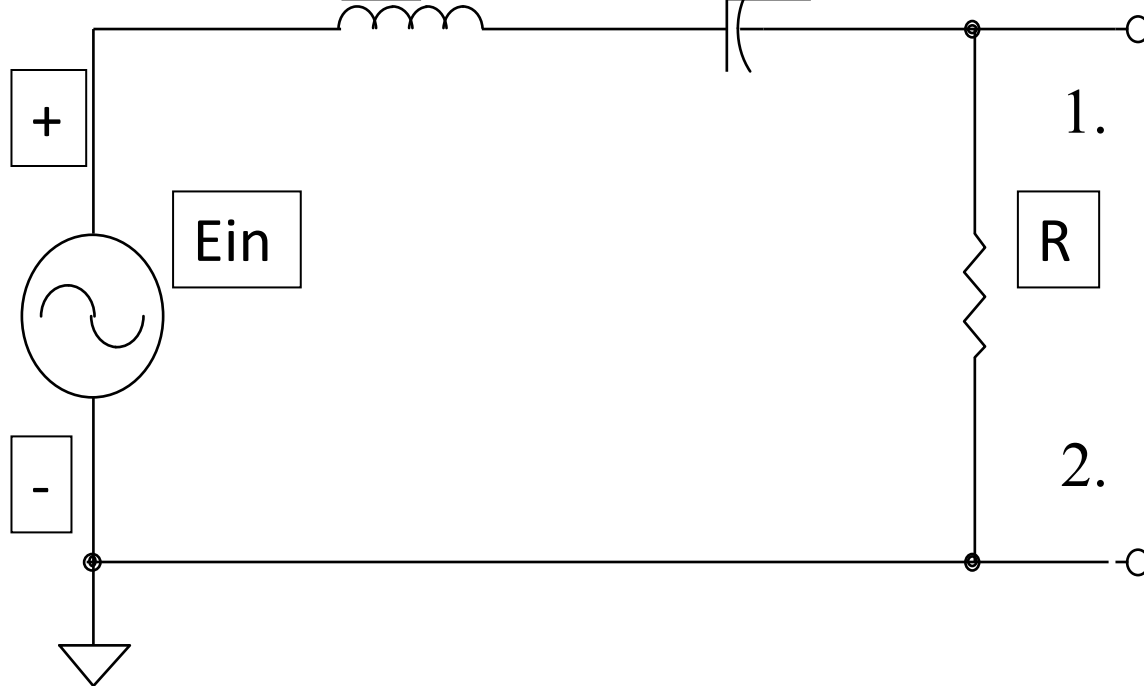

1. V_{out} at DC ?

cap is _____

inductor is _____

2. V_{out} at high f ?

cap is _____


? inductor is _____

$$\frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\omega_n^2 =$$

$$2\zeta\omega_n =$$
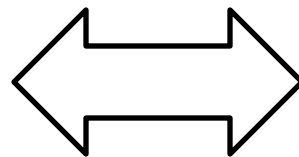
$$\frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



$$\frac{2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

```
clear
format short G
s=tf('s')
```


```
Ao=1;
fo=1e3;
wo=2*pi*fo;
zeta=0.707;
```





```
G=Ao*2*zeta*wo*s/(s^2+2*zeta*wo*s+wo^2)
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```


```
bodeplot(G,{1e2,1e6},opts);
```
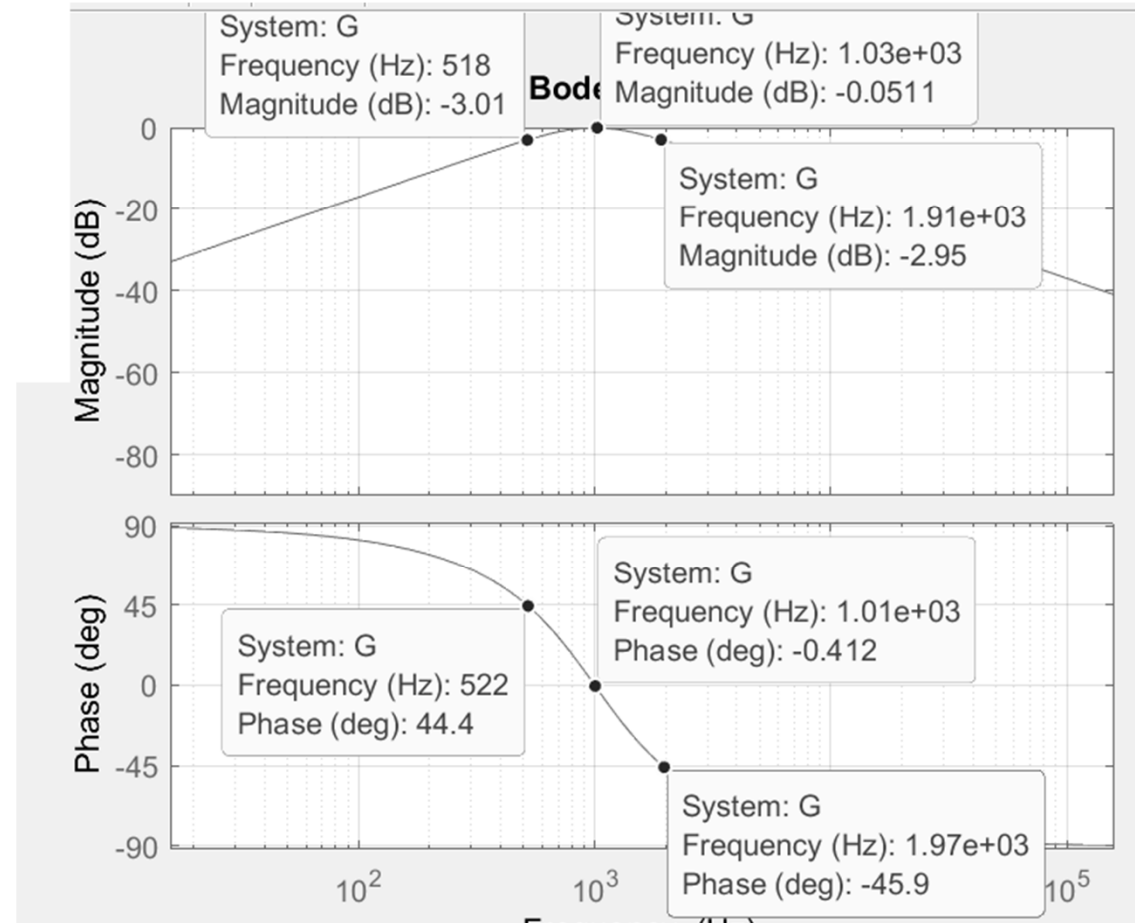
$$\frac{2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




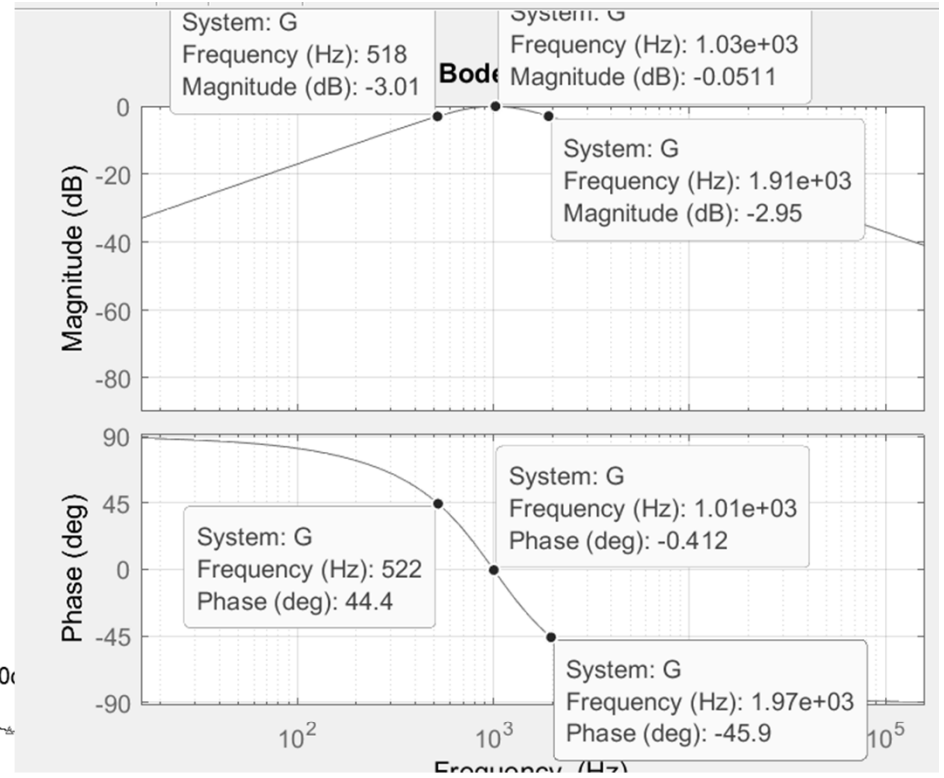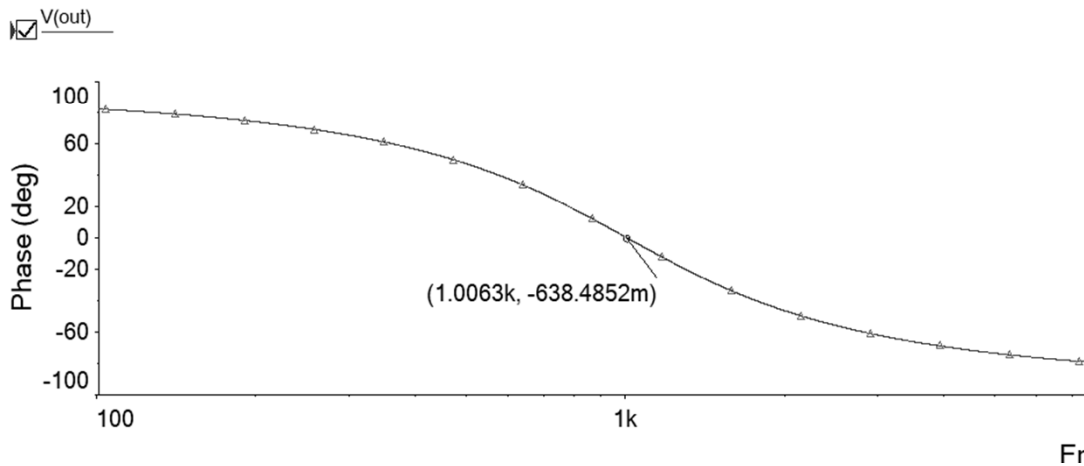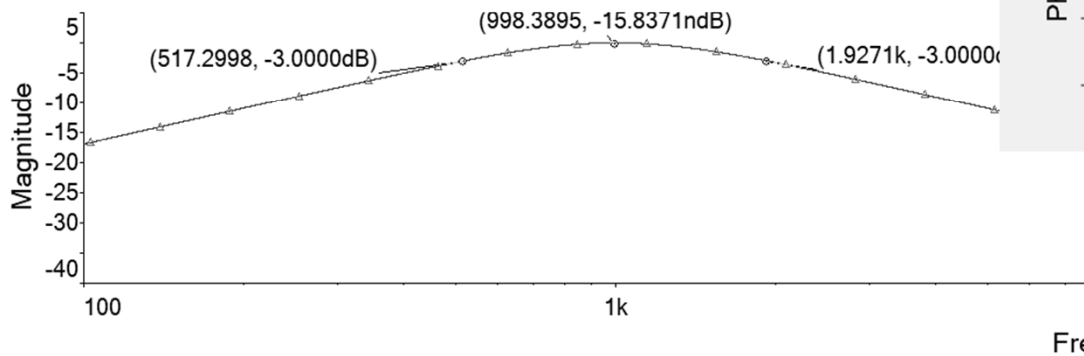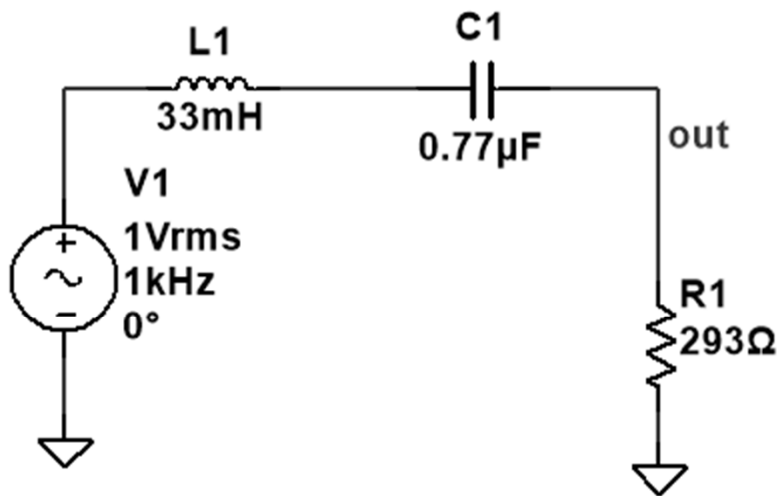

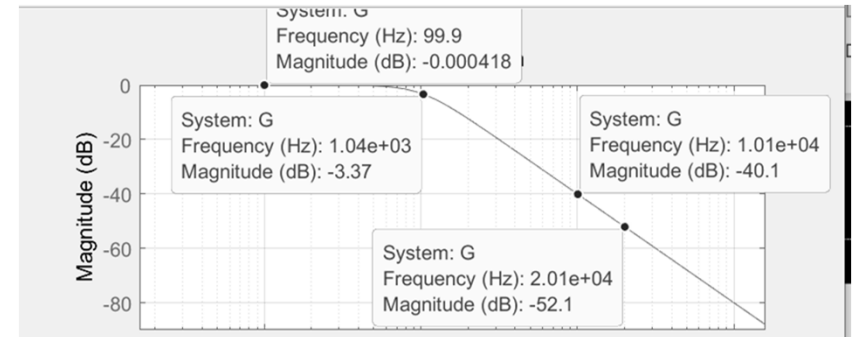
$$\frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


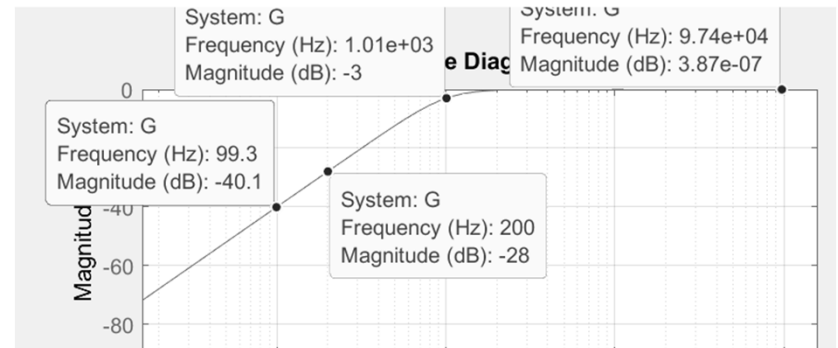
$$\frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


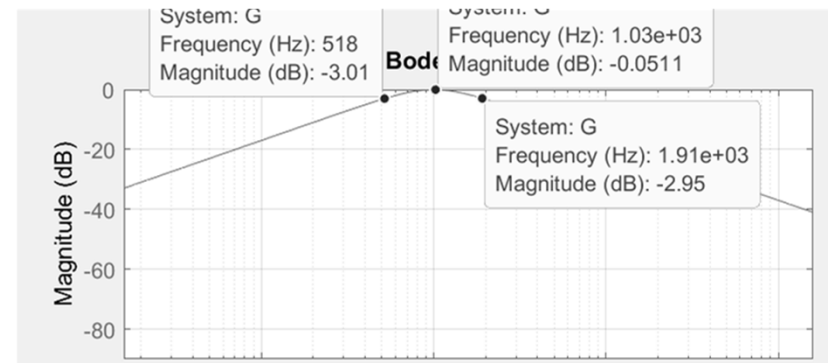
$$\frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




$$\omega_n = \frac{1}{\sqrt{LC}}$$


$$f_o = \frac{1}{2 * \pi \sqrt{LC}}$$

$$\zeta = \frac{1}{2} R \sqrt{\frac{C}{L}}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC}$$

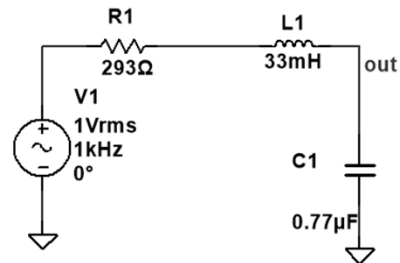

$$s^2 + \frac{R}{L}s + \frac{1}{LC}$$

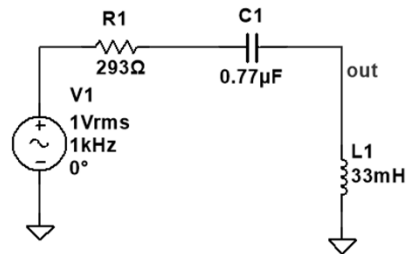

$$s^2 + \frac{R}{L}s + \frac{1}{LC}$$

