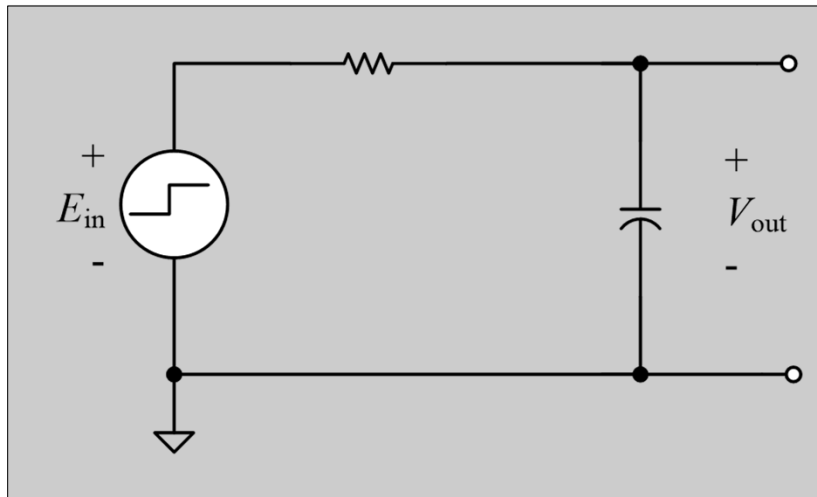


RC Circuit – Transfer Function



$$V_{out}(s) =$$

$$\frac{V_{out}(s)}{E_{in}(s)} =$$


```
clc
clear
s=tf('s')
```

```
R=500;
C=0.5e-6;
tau=R*C
wo=1/tau
fo=wo/(2*pi)
```

```
G=_____
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G,{1e2,1e6},opts);
```

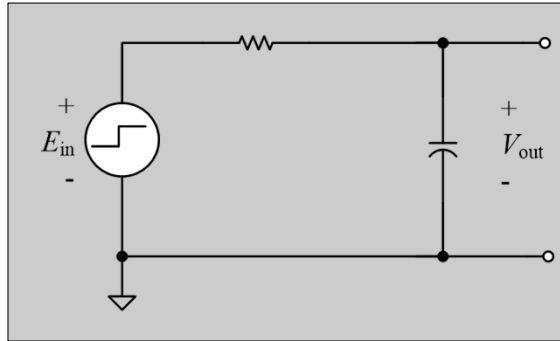

RC Circuit – Frequency Response i.e. Bode' Plot

critical frequency

$$\omega_o = \frac{1}{\tau} \quad \frac{\text{radians}}{\text{second}}$$

$$\omega_o = 2\pi f_o \quad \frac{\text{cycles}}{\text{sec}}$$


$$f_o = \frac{\omega_o}{2\pi}$$

```

clc
clear
s=tf('s')

R=500;
C=0.5e-6;
tau=R*C
wo=1/tau
fo=wo/(2*pi)

```

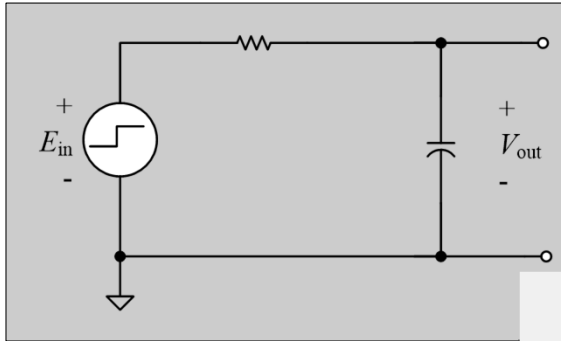

G= _____

```

opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;


```

```

bodeplot(G, {1e2, 1e6}, opts);

```

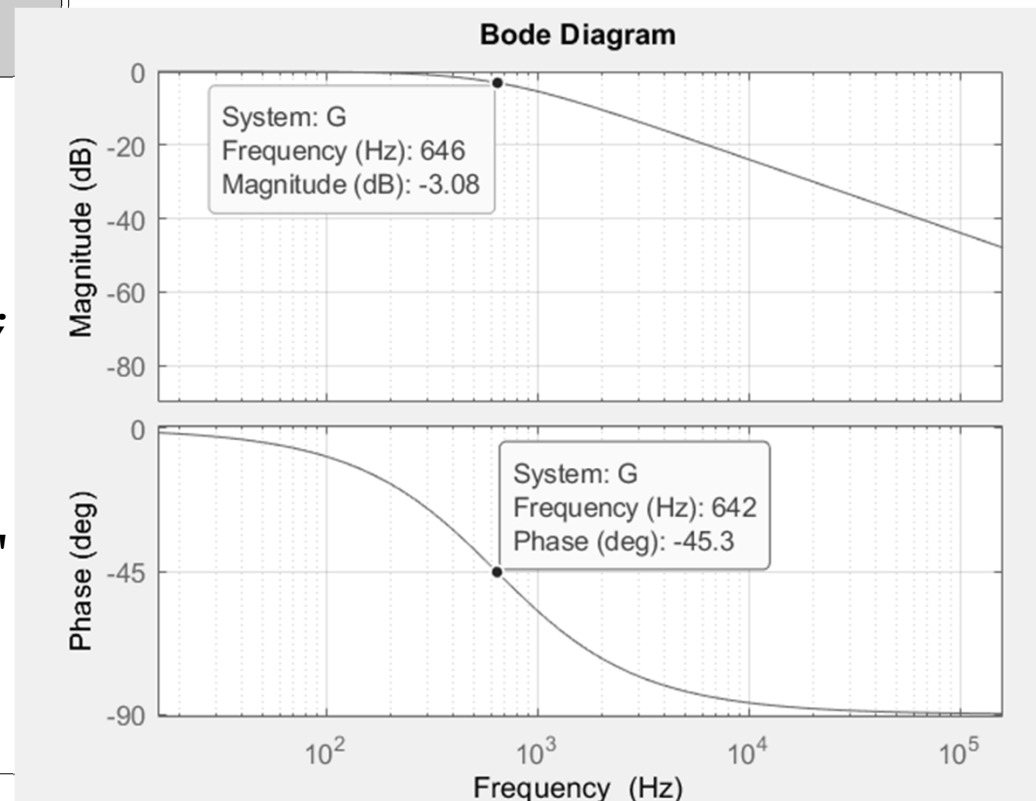RC Circuit – Frequency Response i.e. Bode' Plot





```
clc
clear
s=tf('s')
```

```
R=1000;
C=0.5e-6;
tau=R*C
wo=1/tau
fo=wo/(2*pi)
```


```
G=_____
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G,{1e2,1e6},opts);
```

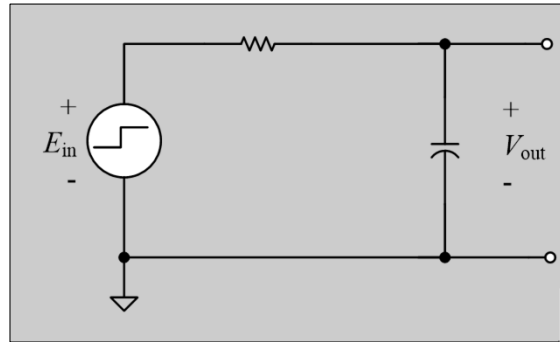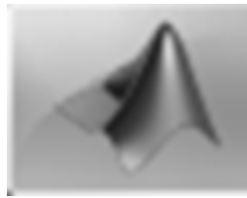


Effect of *doubling* R ??

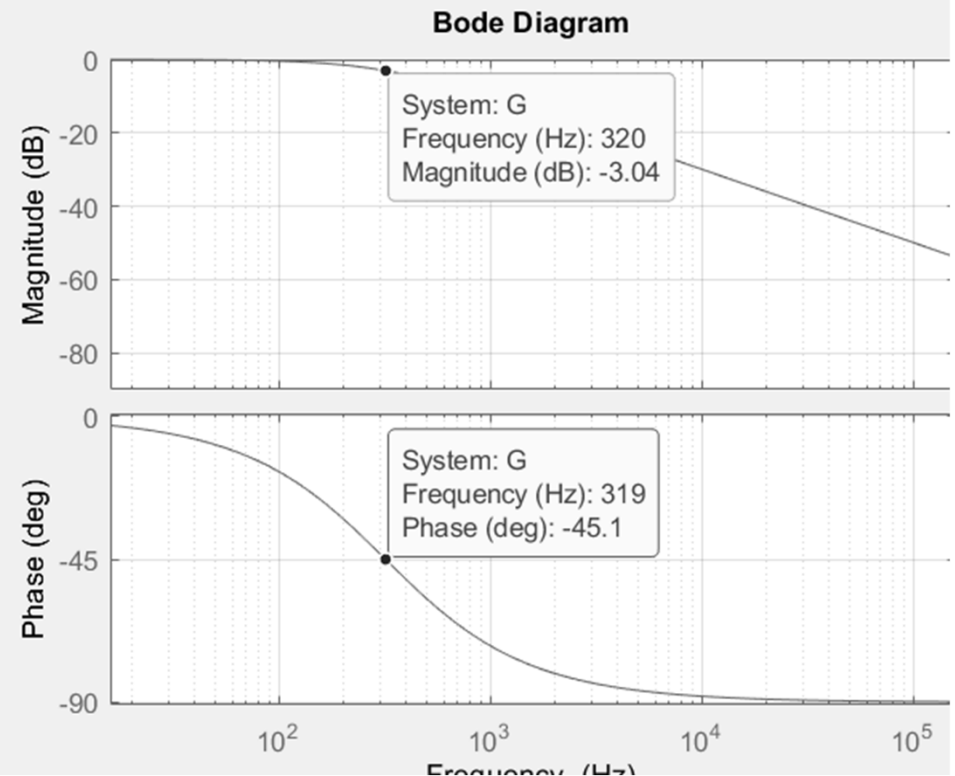

```
clc
clear
s=tf('s')

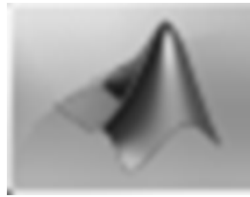R=1000;
C=0.5e-6;
tau=R*C
wo=1/tau
fo=wo/(2*pi)
```



Effect of *reversing* R and C
??

```
G=_____ ;
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;

bodeplot(G,{1e2,1e6},opts);
```

$$s = j\omega$$

$$\frac{V_{out}}{E_{in}} = \frac{1}{Rj\omega C + 1} = \frac{1}{1 + j\omega RC}$$

This is an equation with real and imaginary parts in its denominator. To separate these parts, multiply both the numerator and the denominator by the complex conjugate of the denominator.

$$\frac{V_{out}}{E_{in}} = \frac{1}{1 + j\omega RC} \times \frac{1 - j\omega RC}{1 - j\omega RC}$$

$$= \frac{1 - j\omega RC}{1 - j^2 \omega^2 R^2 C^2}$$

$$= \frac{1 - j\omega RC}{1 + \omega^2 R^2 C^2}$$

$$= \frac{1}{1 + \omega^2 R^2 C^2} - j \frac{\omega RC}{1 + \omega^2 R^2 C^2}$$

$$\frac{V_{out}}{E_{in}} = \text{real} + j \text{imaginary}$$

$$\text{real} = \frac{1}{1 + \omega^2 R^2 C^2} \quad \text{imaginary} = \frac{-\omega RC}{1 + \omega^2 R^2 C^2}$$

$$|\overline{G}| = \text{magnitude} = \sqrt{\text{real}^2 + \text{imaginary}^2}$$

$$= \sqrt{\left(\frac{1}{1 + \omega^2 R^2 C^2}\right)^2 + \left(\frac{\omega RC}{1 + \omega^2 R^2 C^2}\right)^2}$$

$$= \sqrt{\frac{1 + \omega^2 R^2 C^2}{(1 + \omega^2 R^2 C^2)^2}}$$

$$|\overline{G}| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Laplace from s to ω

$$\phi = \text{phase shift} = \arctan\left(\frac{\text{imaginary}}{\text{real}}\right)$$

$$= \arctan\left(\frac{\frac{-\omega RC}{1 + \omega^2 R^2 C^2}}{\frac{1}{1 + \omega^2 R^2 C^2}}\right)$$

$$\phi = -\arctan(\omega RC)$$

Frequency response at a glance

$$G = \frac{A}{\tau s + 1} \Rightarrow s \propto \omega \Rightarrow G \propto \frac{A}{\omega + 1}$$

As $\omega \Rightarrow 0$ $G \Rightarrow A$ As $\omega \Rightarrow \infty$ $G \Rightarrow 0$ Low pass $A_{\omega} = A$

$$G = \frac{A\omega}{\tau s + 1} \Rightarrow s \propto \omega \Rightarrow G \propto \frac{A\omega}{\omega + 1}$$

As $\omega \Rightarrow 0$ $G \Rightarrow \frac{0}{1} = 0$ As $\omega \Rightarrow \infty$ $\frac{\infty}{\infty + 1} = 1$ High pass $A_{\omega} = 1$

$$G = \frac{A}{s^2 + Bs + C} \Rightarrow s \propto \omega \Rightarrow G \propto$$

$$\text{As } \omega \Rightarrow 0 \quad G \Rightarrow \quad \text{As } \omega \Rightarrow \infty \quad G \Rightarrow$$

$$\text{_____ pass } \underline{\underline{A_\omega}} =$$

$$G = \frac{As^2}{s^2 + Bs + C} \Rightarrow s \propto \omega \Rightarrow G \propto$$

$$\text{As } \omega \Rightarrow 0 \quad G \Rightarrow \quad \text{As } \omega \Rightarrow \infty \quad G \Rightarrow$$


$$\text{_____ pass } \underline{\underline{A_\omega}} =$$

$$G = \frac{As}{s^2 + Bs + C} \Rightarrow s \propto \omega \Rightarrow G \propto$$

$$\text{As } \omega \Rightarrow 0 \quad G \Rightarrow \quad \text{As } \omega \Rightarrow \infty \quad G \Rightarrow$$



$$\text{_____ pass } \underline{\underline{A_\omega}} =$$

Multisim – AC Sweep

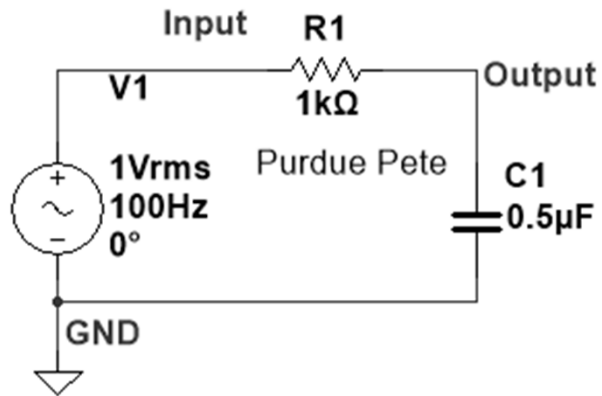

Right click on Output node
Properties/Netname/Show

Simulate/Analysis & Simulations/AC Sweep

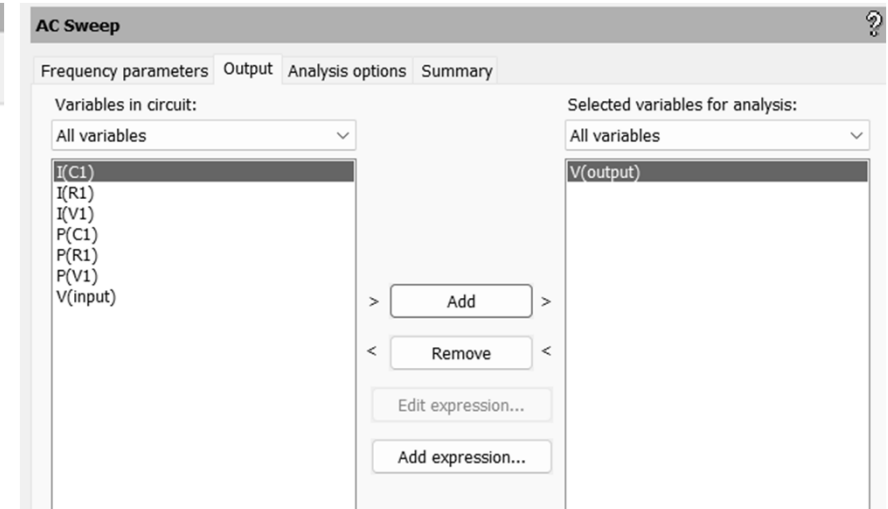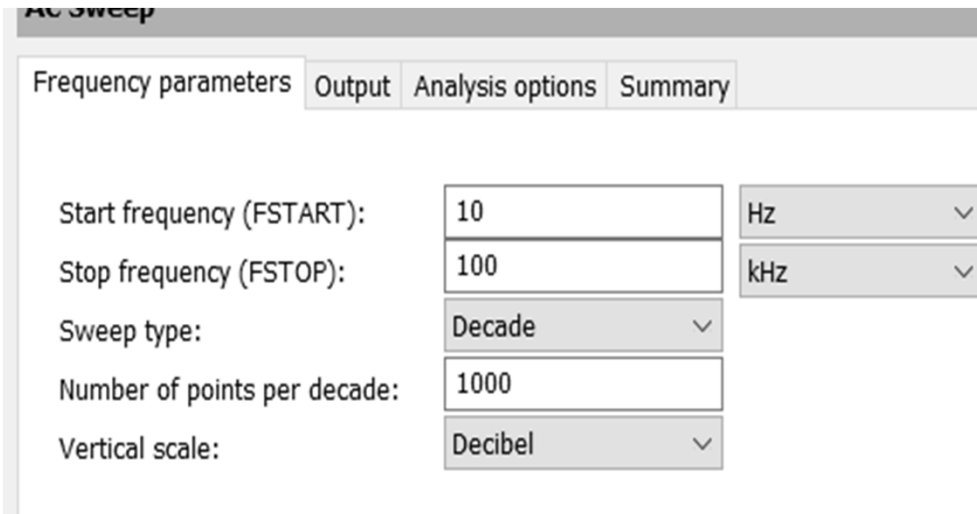

Plots and Cursors - Is f_o right?

