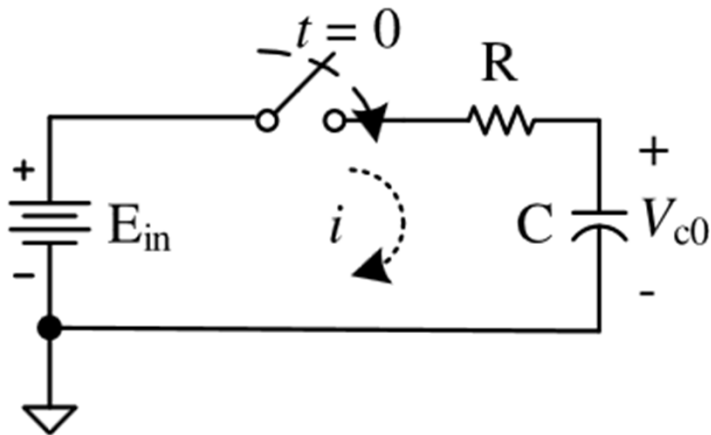


First Order – RC Circuit – Initial Conditions

Table 3-1 Voltage and current relationships

unknown	R	C	L
i	$\frac{v}{R}$	$C \frac{dv}{dt}$	$\frac{1}{L} \int_0^t v dt + I_o$
v	$i \times R$	$\frac{1}{C} \int_0^t i dt + V_o$	$L \frac{di}{dt}$

- $v_C(0) =$ _____
- $v_R(0) =$ _____
- $i(0) =$ _____



- $v_C(\infty) =$ _____
- $v_R(\infty) =$ _____
- $i(\infty) =$ _____

Figure 3-16 RC circuit with a step input

First Order – RC Circuit – KVL Standard Form

Table 3-1 Voltage and current relationships

unknown	R	C	L
i	$\frac{v}{R}$	$C \frac{dv}{dt}$	$\frac{1}{L} \int_0^t v dt + I_o$
v	$i \times R$	$\frac{1}{C} \int_0^t i dt + V_o$	$L \frac{di}{dt}$

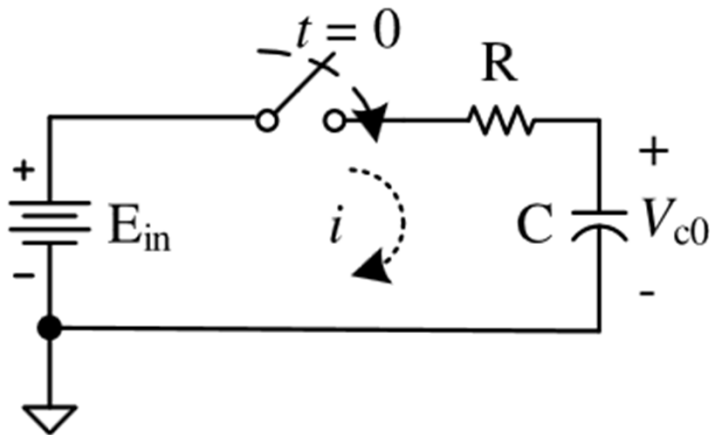



Figure 3-16 RC circuit with a step input

de Solve

$$i' = -\frac{1}{RC}i$$

$$i_{0+} = \frac{V_{R0+}}{R} = \frac{E_{in}}{R}$$

- entry

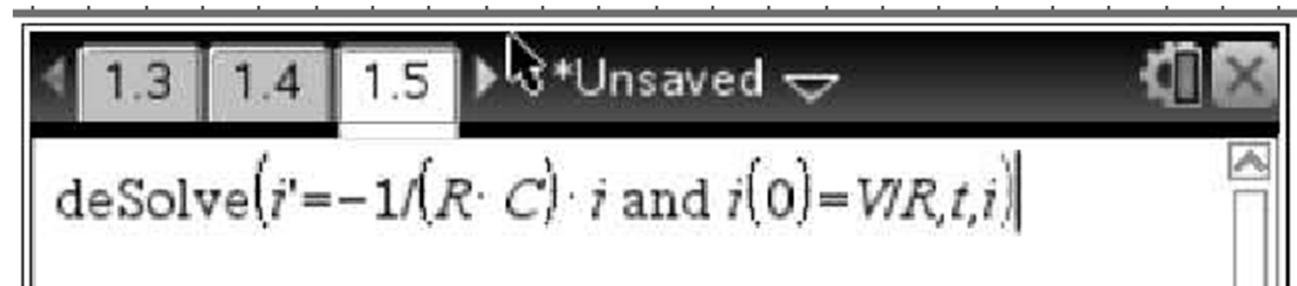

- The prime is on the π menu.
- Spaces before and after **and** are necessary.
- Then enter the initial conditions equation,
- Followed by a comma, the x variable, and the y variable.

V_R ?

v_C ?

Substitute answers into KVL

Table 3-1 Voltage and current relationships			
unknown	R	C	L
i	$\frac{v}{R}$	$C \frac{dv}{dt}$	$\frac{1}{L} \int_0^t v dt + I_o$
v	$i \times R$	$\frac{1}{C} \int_0^t i dt + V_o$	$L \frac{di}{dt}$

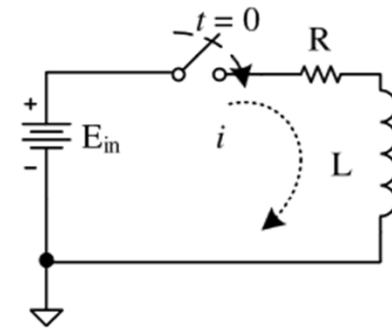


Figure 3-24 RL circuit with a step