


ECET 337
Exam 3
Spring 2025A

Solutions

Name _____

Filter type	Damping (α)	Correction (k_{lp})
Bessel	1.732	0.785
Butterworth	1.414	1.000
3 dB Chebyshev	0.766	1.390

1. Below is the schematic for a filter.

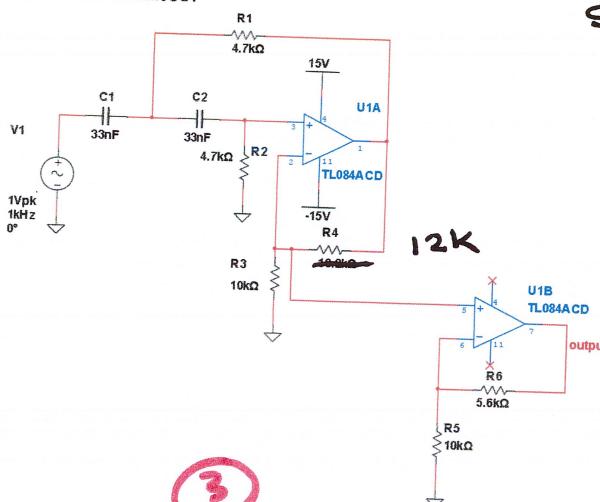

SK HP

- a. [10%] Write the transfer function in terms of A_o , ω_o , α , and s .

$$\frac{V_{out}(s)}{E_{in}(s)} = \frac{A_o \alpha^2}{\alpha^2 + \alpha \omega_o \mu + \omega_o^2}$$

- b. [9%] Calculate the numerical value of each of these parameters

$$A_o = \frac{1.56}{1 + \frac{5.6k\Omega}{10k\Omega}} \quad \textcircled{1} \quad \omega_o = \frac{6.45k\text{ rad/sec}}{4.7k\Omega + 33nF} \quad \textcircled{2} \quad \alpha = \frac{0.80}{1} \quad \textcircled{3}$$

$$3 - A_{HP} = 3 - \left(1 + \frac{12}{10k\Omega} \right) \quad \textcircled{2}$$

- c. [16%] Calculate the following parameters.

1) $V_{out} \text{ RMS } @ 20 \text{ kHz} = \frac{1.56 \text{ V}}{1.1V} \quad 1V + 1.56 \neq 0.707$

2) (circle one) low-pass band-pass

high-pass

3) (circle one) Bessel Butterworth

Chebyshev

4) $f_o = 1.03k\text{ Hz} \quad f_o = \frac{1}{2\pi \times 4.7k \times 33nF}$

5) What happens at f_o ? phase shifted +90°

6) $f_{-3dB} = 741 \text{ Hz} = k_{HP} \times f_o = \frac{1}{1.39} \times 1.03k\text{ Hz}$

7) What happens at f_{-3dB} ? gain dropped by 0.707

8) Roll-off rate = +12 dB/act

or +40 dB/decade

29a

-5

4. Below are the parameters for a filter.

- 1) $f_{-3\text{dB}} = 2\text{k Hz}$
- 2) low pass
- 3) $E_{\text{in DC}} = 1 \text{ V}_{\text{DC}}$ $V_{\text{out DC}} = 1 \text{ V}_{\text{DC}}$
- 4) Butterworth
- 5) order = 2nd

- a. [10%] Write the transfer function in terms of A_o , ω_o , α , and s .

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{A_o \omega_o^2}{s^2 + d \omega_o s + \omega_o^2}$$


- b. [9%] Calculate the numerical value of each of these parameters

$$A_o = \frac{1}{12.57 \text{ k} \frac{\text{rad}}{\text{s}}} \quad \omega_o = 12.57 \text{ k} \frac{\text{rad}}{\text{s}} \quad \alpha = 1.414 =$$

$$\omega_o = 12.57 \times 2\pi f_o = 2\pi \times 2\text{k Hz}$$

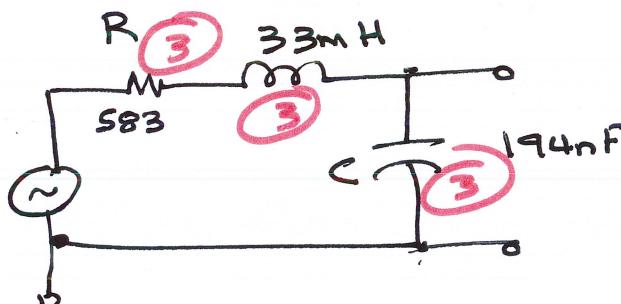- b. [16%] Draw the schematic below using only an inductor, capacitor and resistor.

Choose $L = 33 \text{ mH}$. Show all of the calculations for the value of each component that you add.



$$\omega_o = \frac{1}{\sqrt{LC}} \quad \omega_o^2 = \frac{1}{LC}$$

$$C = \frac{1}{\omega_o^2 L} = \frac{1}{(12.57 \text{ k})^2 \times 33 \text{ mH}} = 194 \text{ nF}$$

$$\xi = \frac{1}{2} R \sqrt{\frac{C}{L}} \quad 2\xi \sqrt{\frac{L}{C}} = R$$

$$R = 2 * 0.707 \sqrt{\frac{33 \text{ mH}}{194 \text{ nF}}} = 583 \Omega$$

3. Below is the transfer function for a filter.

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{-1200 s}{s^2 + 600 s + 40 \times 10^3}$$

- a. [10%] Write the transfer function in terms of A_0 , ω_0 , α , and s .

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{A_0 d \omega_0 s}{s^2 + d \omega_0 s + \omega_0^2}$$

[14%] Calculate the following parameters.

1) Type low-pass

band-pass

high-pass (circle one)

2) $\omega_0 = 200 \text{ rad/sec}$ $\sqrt{40 \times 10^3}$

3) $f_0 = 31.8 \text{ Hz}$ $\omega_0 = 2\pi f_0$

$$f_0 = \frac{200}{2\pi} \text{ rad/sec}$$

4) phase at $f_0 = \pm 180^\circ$ $0^\circ \rightarrow -180^\circ$

5) $\alpha = 3$

$$d\omega_0 = 600 \quad d = 600/200$$


6) $A_0 = -2$

$$A_0 d \omega_0 = -1200 \quad A_0 = \frac{-1200}{3 \times 200}$$

7) Roll-off rate between 1 kHz and 2 kHz = -6 dB/oct

$$-12 \text{ dB} \rightarrow -1$$

- b. [6%] Complete the schematic below. Choose $C = 100 \text{ nF}$. Show all of the calculations for the value of each component that you add. You may or may not use all of the parts. X out those you do not use.

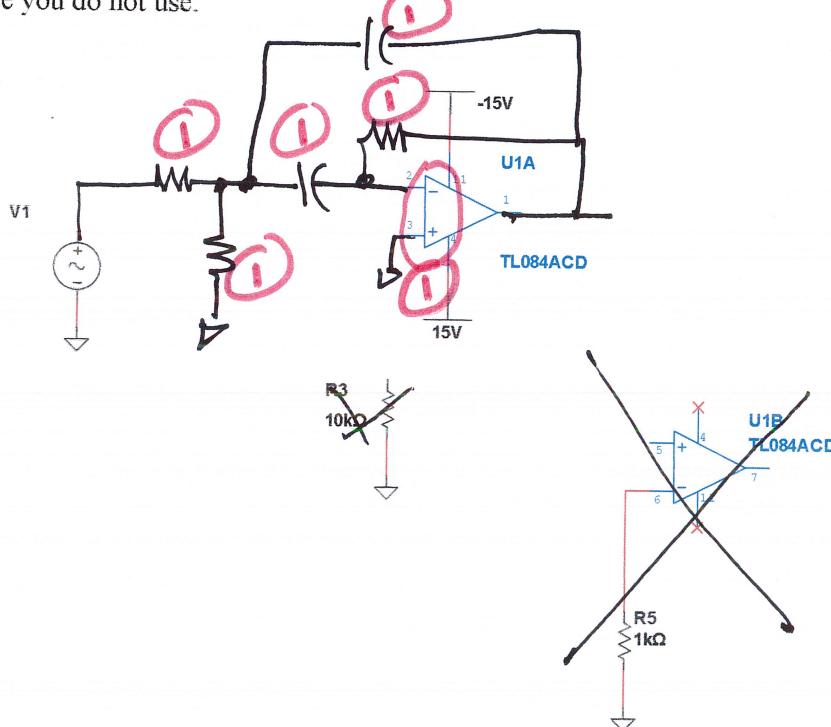


ECET 337
Exam 3
Spring 2025B

Solutions

Name _____

Filter type	Damping (α)	Correction (k_{lp})
Bessel	1.732	0.785
Butterworth	1.414	1.000
3 dB Chebyshev	0.766	1.390

1. Below is the schematic for a filter.

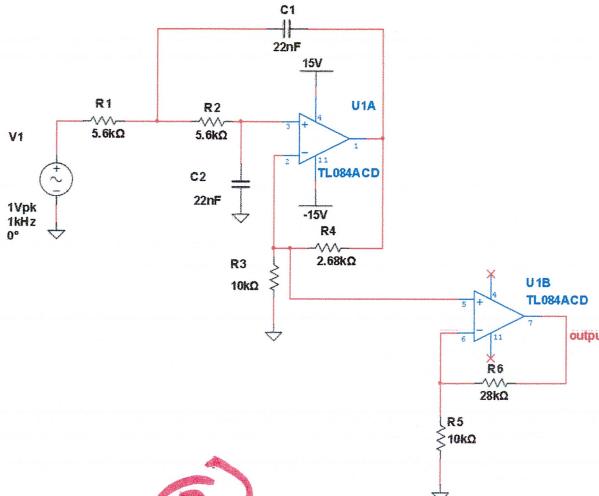

- a. [10%] Write the transfer function in terms of A_o , ω_o , α , and s .

$$\frac{V_{out}(s)}{E_{in}(s)} = \frac{A_o \omega_o^2}{s^2 + \alpha \omega_o s + \omega_o^2}$$

- b. [9%] Calculate the numerical value of each of these parameters

$$A_o = 3.8 \quad \omega_o = \frac{8.12k}{5.6k \cdot 22nF} \quad \alpha = 1.73$$

- c. [16%] Calculate the following parameters.

1) $V_{out} @ DC = 3.8V_{DC} = A_o * 1V_{DC}$

2) (circle one) low-pass band-pass high-pass

3) (circle one) Bessel Butterworth Chebyshev

4) $f_o = 1.29kH2 \approx \omega_o = 2\pi f_o \quad f_o = \omega_o / 2\pi$

5) What happens at f_o ? phase shifted -90°

6) $f_{-3dB} = 1kH2 = k_{LP} * f_o = 0.785 * 1.29kH2$

7) What happens at f_{-3dB} ? Gain drops $-3dB$ below A_o (0.707 * A_o)

8) Roll-off rate = $-12dB/dec$

or
 $-40 dB/decade$

$$A_{INT} = 1 + \frac{2.68k}{10k}$$

$$= 1.268$$

$$d = 3 - 1.268$$

2

2. Below are the parameters for a filter.

- 1) $f_{-3\text{dB}} = 440 \text{ Hz}$
- 2) high pass
- =
- 3) $E_{\text{in}} = 1 \text{ V}_{\text{RMS}}$ $V_{\text{out}} @ 50\text{kHz} = 1 \text{ V}_{\text{RMS}}$
- 4) Butterworth
- 5) order = 2nd

a. [10%] Write the transfer function in terms of A_o , ω_o , α , and s .

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{A_o s^2}{s^2 + 2\omega_o s + \omega_o^2}$$


b. [9%] Calculate the numerical value of each of these parameters

$$A_o = \frac{1}{3} \quad \omega_o = 2.74k \text{ rad/sec} \quad \alpha = 1.414$$

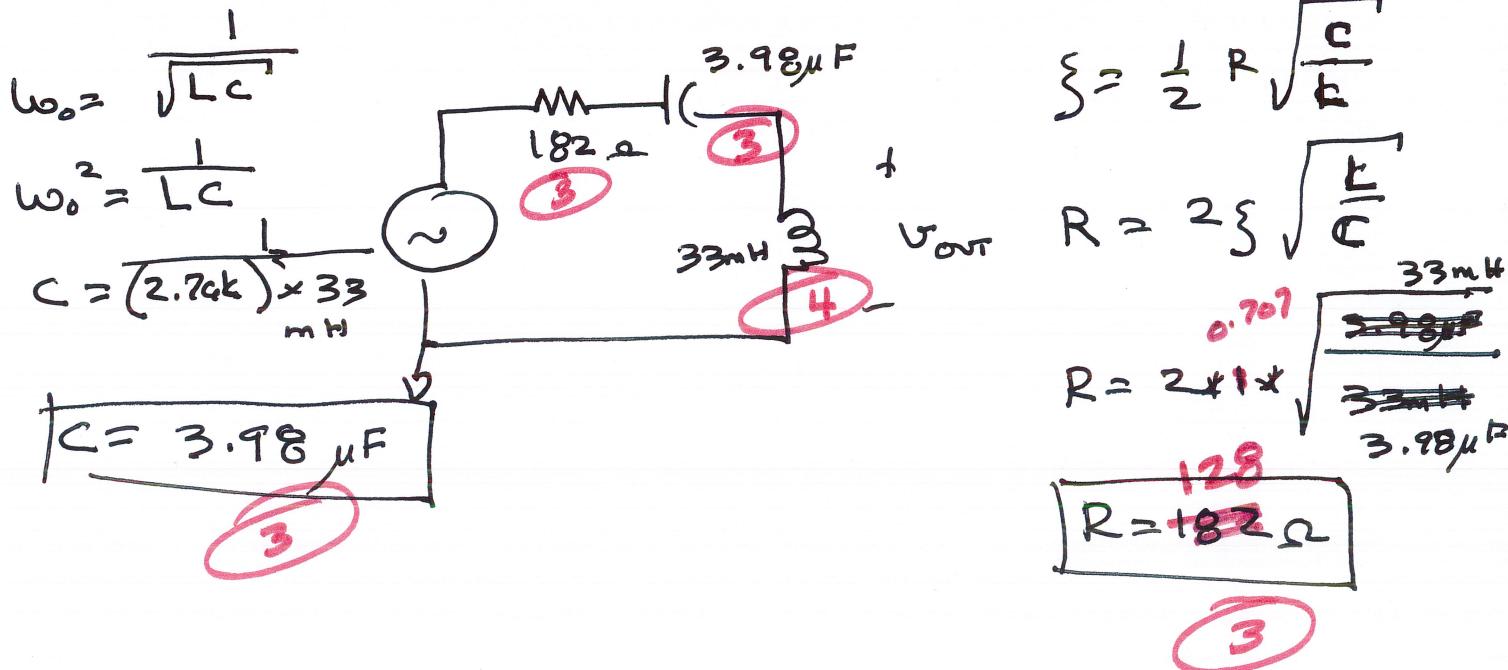b. [16%] Draw the schematic below using only an inductor, capacitor and resistor.

Choose $L = 33 \text{ mH}$. Show all of the calculations for the value of each component that you add.

$$\begin{cases} f_0 = f_{-3\text{dB}} \\ \omega_o = 2\pi f_0 = 2\pi \times 440 \text{ Hz} \end{cases} \quad (\text{Butterworth})$$



3. Below is the transfer function for a filter.

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{-700 s}{s^2 + 130 s + 160 \times 10^3}$$

- a. [10%] Write the transfer function in terms of A_0 , ω_0 , α , and s .

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} = \frac{A_0 \alpha \omega_0 s}{s^2 + \alpha \omega_0 s + \omega_0^2}$$

- [14%] Calculate the following parameters.

1) Type low-pass

band-pass

high-pass (circle one)

2) $\omega_0 = 400 \text{ rad/sec}$

$\sqrt{160 \times 10^3}$

3) $f_0 = 64.42$ $\omega_0 = 2\pi f_0$

$f_0 = 400 / 2\pi =$

4) phase at $f_0 = \pm 180^\circ$

5) $\alpha = 0.325$ $\alpha \omega_0 = 130$ $\alpha = 130 / 400 = 0.325$

6) $A_0 = 5.38$ $A_0 \alpha \omega_0 = -700$ $A_0 = -700 / 130$

7) Roll-off rate between 20 Hz and 40 Hz = $+6 \text{ dB/dec}$

- b. [6%] Complete the schematic below. Calculate *no* component values. You may or may not use all of the parts. X out those you do not use.

