

Put your calculator in the *Exact* mode.

1. Given the time domain equation:

$$f(t) = 18 * t$$

a. [5%] Write the integral definition of its Laplace transform.

$$F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt \Big|_{s>0} = \int_0^{\infty} 18xt e^{-st} dt \Big|_{s>0}$$

- b. [15%] Complete the integral operation, either manually or using your calculator to find  $F(s)$ . If you complete the integration manually, show *all* appropriate steps. If you use your calculator, write below the *exact* information entered.

Do *not* bother to convert the answer to standard form.

$$\frac{18}{s^2}$$

Put your calculator in the *Approximate* mode.

- c. [10%] Using the Laplace Transform tables, also find  $f(t)$  for  $F(s) = \frac{18}{s(s+5)(s+9)}$

$$f(t) = \frac{A}{s(a+b)} \Rightarrow \frac{A}{ab} \left( \frac{ae^{-bt} - be^{-at}}{b-a} \right)$$

Table line number = 20 b

$$\begin{aligned} A &= 18 \\ a &= 5 \\ b &= 9 \end{aligned}$$

$$f(t) = 0.4 \left( 1 + \frac{5e^{-5t} - 9e^{-9t}}{4} \right)$$

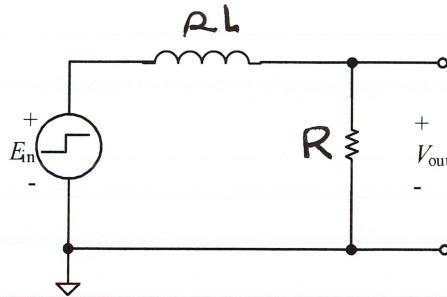


Figure 1 Schematic for Problem 2

2. [10%] a. Derive the equation for the *transfer function* in terms of  $s$  for the circuit above, with symbols,  $L$ ,  $R$ , &  $s$ , not values.

$$\frac{R}{sL + R} \cdot \frac{V_{out}}{E_{in}} = \frac{1}{sL + R} \quad \approx = \frac{L}{R}$$

Put the answer in the *standard form* found in the Tables.

$$\frac{V_{out}}{E_{in}} = \frac{1}{s\tau + 1}$$

- [4%] b. Write the Laplace equation for  $E_{in} = 18 \text{ V}$ , a *step*.

$$E_{in}(s) = \frac{18}{s} \quad \text{either}$$

- [4%] c. Write the Laplace equation for the output voltage in response to the step.

$$V_{out}(s) = \frac{18}{s} \cdot \frac{1}{(s\tau + 1)} = \frac{18}{s(s\tau + 1)}$$


- [4%] d. Determine the *time domain* equation for the output with symbols.

$$V_{out}(t) = 18 \left( 1 - e^{-t/\tau} \right) \quad \text{Table line \# } 17a$$

- [8%] e. For  $R = 4.7 \text{ k}\Omega$  and  $L = 33 \text{ mH}$ , calculate

$$\text{Peak amplitude} = 18 \text{ V} \quad \text{time constant} = \frac{L}{R} = \frac{33 \text{ mH}}{4.7 \text{ k}\Omega} = 7.02 \text{ msec}$$

Sketch the output waveshape

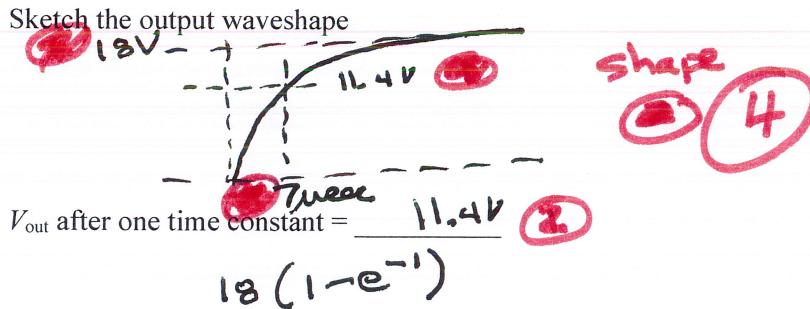

$$A \omega_n^2$$

3. [6%] a. Given the transfer function:  $\frac{12 \times 10^9}{s^2 + 65 \times 10^3 s + 3 \times 10^9}$  for a set of R, L, and C

Calculate:  $\omega_n = 254.8 \text{ rad/s}$   $K_{A_0} = 4$   $\xi = 0.6$

$$\omega_n^2 = 3 \times 10^9$$

$$\omega = \sqrt{3 \times 10^9}$$

$$A = 4$$

$$2\zeta\omega_n = 65 \times 10^3$$

$$\zeta = \frac{65 \times 10^3}{2 \times 54.8 \text{ rad/s}}$$

- b. [6%] If  $A_0$ , only, decreases, what happens to the following responses?

Answer: Increase, no change, decrease

(3)

1) final height in response to a step input decreases

2) ringing NC

(3)

- c. [8%] If  $\xi$ , only, is cut in half, what would happen to each of the following responses?

Answer: Increase, no change, decrease

(4)

1) final height in response to a step input NC

2) ringing increases

(4)

- e. [10%] Identify the type of damping that describes each of the following characteristics.

Answer over or critical or under

100

| Characteristics                     | damping         |
|-------------------------------------|-----------------|
| 1. $\xi = 1$                        | <u>critical</u> |
| 2. $\xi > 1$                        | <u>over</u>     |
| 3. $\xi < 1$                        | <u>under</u>    |
| 4. fastest without overshooting     | <u>critical</u> |
| 5. overshoots                       | <u>under</u>    |
| 6. smallest 5% settling time        | <u>under</u>    |
| 7. sluggish                         | <u>over</u>     |
| 8. two equal, real roots            | <u>critical</u> |
| 9. different real roots             | <u>over</u>     |
| 10. two complex roots <del>NC</del> | <u>under</u>    |

4. [10%] Answer the following for the circuit to the right.

- a) Does this: (choose one)

pass DC and block pulses or  
pass pulses and block DC

(3)

- b) Which component(s) set the resonant (critical) frequency?  
(circle in the schematic)


(2)

- c) Does changing R affect the damping?  
Yes or No (circle one)

(2)

- d) What is the circuit's order?  
1<sup>st</sup> 2<sup>nd</sup> 3<sup>rd</sup> (circle one)

(3)

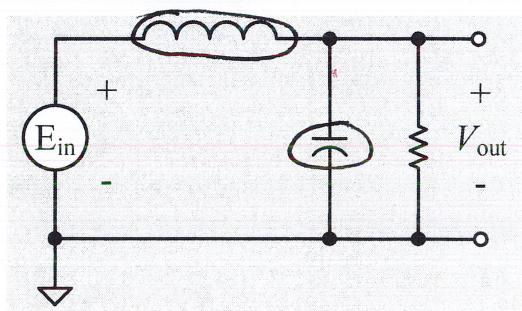

ECET 337  
Exam 2B  
Spring 2025

Solutions  
Name \_\_\_\_\_

Put your calculator in the *Exact* mode.

1. Given the time domain equation:

$$f(t) = 12 * t + 3$$

- a. [5%] Write the integral definition of it's Laplace transform.

$$F(s) = \int_0^\infty f(t) e^{-st} dt \Big|_{s>0}$$

- b. [15%] Complete the integral operation, either manually or using your calculator to find  $F(s)$ . If you complete the integration manually, show *all* appropriate steps. If you use your calculator, write below the *exact* information entered.

Do *not* bother to convert the answer to standard form.

$$\int_0^\infty (12*t + 3) * e^{-st} dt \Big|_{s>0} = 3(12)$$

$$\frac{3(\rho+4)}{\rho^2} \quad 3$$

Put your calculator in the *Approximate* mode.

- c. [10%] Using the Laplace Transform tables, also find  $f(t)$  for  $F(s) = \frac{12}{s(s+3)(s+7)}$

$$f(t) = \frac{6.571}{s} \left( 1 + \frac{3e^{-7t}}{4} - 7e^{-3t} \right)$$

Table line number = 20 b 3

$$\frac{A}{s(s+a)(s+b)} \Rightarrow \frac{A}{ab} \left( 1 + \frac{ae^{-bt} - be^{-at}}{b-a} \right)$$

$$\begin{aligned} A &= 12 \\ a &= 3 \\ b &= 7 \end{aligned}$$

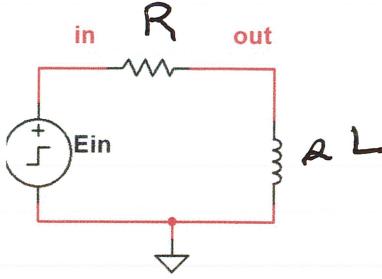


Figure 1 Schematic for Problem 2

2. [10%] a. Derive the equation for the *transfer function* in terms of  $s$  for the circuit above, with symbols,  $L$ ,  $R$ , &  $s$ , not values.

$$\frac{V_{out}}{E_{in}} = \frac{\frac{1}{R} s L}{R + sL} \quad \frac{1}{R} = \frac{\frac{L}{R} s}{\frac{L}{R} s + 1} \quad \tau = \frac{L}{R}$$

Put the answer in the *standard form* found in the Tables.

$$\frac{V_{out}}{E_{in}} = \frac{\frac{L}{R} s}{\frac{L}{R} s + 1} = \frac{\tau s}{\tau s + 1} \quad (1)$$

- [4%] b. Write the Laplace equation for  $E_{in} = 12 V$ , a *step*.

$$E_{in}(s) = \frac{12}{R} \quad (2)$$

- [4%] c. Write the Laplace equation for the output voltage in response to the step.

$$V_{out}(s) = \frac{\frac{L}{R} \tau s}{\tau s + 1} = \frac{12 s}{(s + 1)} \quad (2)$$

- [4%] d. Determine the *time domain* equation for the output with symbols.

$$V_{out}(t) = \frac{12 e^{-t/\tau}}{2} \quad (2)$$

Table line # 13a

- [8%] e. For  $R = 2.2 \text{ k}\Omega$  and  $L = 56 \text{ mH}$ , calculate

$$\text{Peak amplitude} = 12V \quad (1)$$

$$\text{time constant} = \frac{25.5 \mu s}{2.2 k\Omega}$$

$$\frac{L}{R} = \frac{56 \text{ mH}}{2.2 \text{ k}\Omega}$$

Sketch the output waveshape

*shape*  
4

$$V_{out} \text{ after one time constant} = 4.4V \quad (2)$$

$$12V (e^{-1}) = 4.4V$$

$$\left. \begin{array}{l} (1) \\ \frac{A}{s + 1} \rightarrow \frac{A}{s} e^{-t/\tau} \\ A = 12 \tau \\ V_{out} = \frac{12 \tau}{s} e^{-t/\tau} \\ = 12 e^{-t/\tau} \end{array} \right\}$$

3. [6%] a. Given the transfer function:  $\frac{15 \times 10^9}{s^2 + 56 \times 10^3 s + 8 \times 10^9}$  for a set of R, L, and C

Calculate:  $\omega_n = \sqrt{\frac{15 \times 10^9}{8 \times 10^9}} = 89.4 \text{ rad/s}$  (2)

 $\omega_n^2 = 8 \times 10^9$  (2)
 $A_o = \frac{1.88}{15 \times 10^9} = 1.2 \times 10^{-9}$  (2)
 $\xi = \frac{0.3}{\sqrt{15 \times 10^9}} = 0.3 \times 10^{-3}$  (2)
 $2\xi\omega_n = 56 \times 10^3$ 
 $\zeta = \frac{56 \times 10^3}{2 \times 89.4 \times 10^9} = 0.3 \times 10^{-3}$  (2)

- b. [6%] If  $A_o$ , only, increases, what happens to the following responses?

Answer: Increase, no change, decrease

1) ringing NC (3)

2) final height in response to a step increase (3)

- c. [8%] If  $\xi$ , only, is increased by 3, what would happen to each of the following responses?

Answer: Increase, no change, decrease

1) ringing decreases (4)

2) final height in response to a step NC (4)

- e. [10%] Identify the type of damping that describes each of the following characteristics.

Answer over or critical or under

1ea

| Characteristics               | damping |
|-------------------------------|---------|
| 1. $\xi > 1$                  | O       |
| 2. $\xi = 1$                  | C       |
| 3. $\xi < 1$                  | U       |
| 4. sluggish                   | O       |
| 5. fastest with no overshoots | C       |
| 6. smallest 5% settling time  | U       |
| 7. overshoots                 | U       |
| 8. different, real roots      | O       |
| 9. two complex roots          | U       |
| 10. equal, real roots         | C       |

4. [10%] Answer the following for the circuit to the right.

- a) What is the circuit's order?

1<sup>st</sup>    2<sup>nd</sup>    3<sup>rd</sup> (circle one) (3)

- b) Which component(s) set the resonant (critical) frequency?  
(circle in the schematic)

2

- c) Does changing R affect the damping?

Yes or No (circle one) 2

- d) Does this: (choose one)

pass pulses and block DC or  
pass DC and block pulses 3

