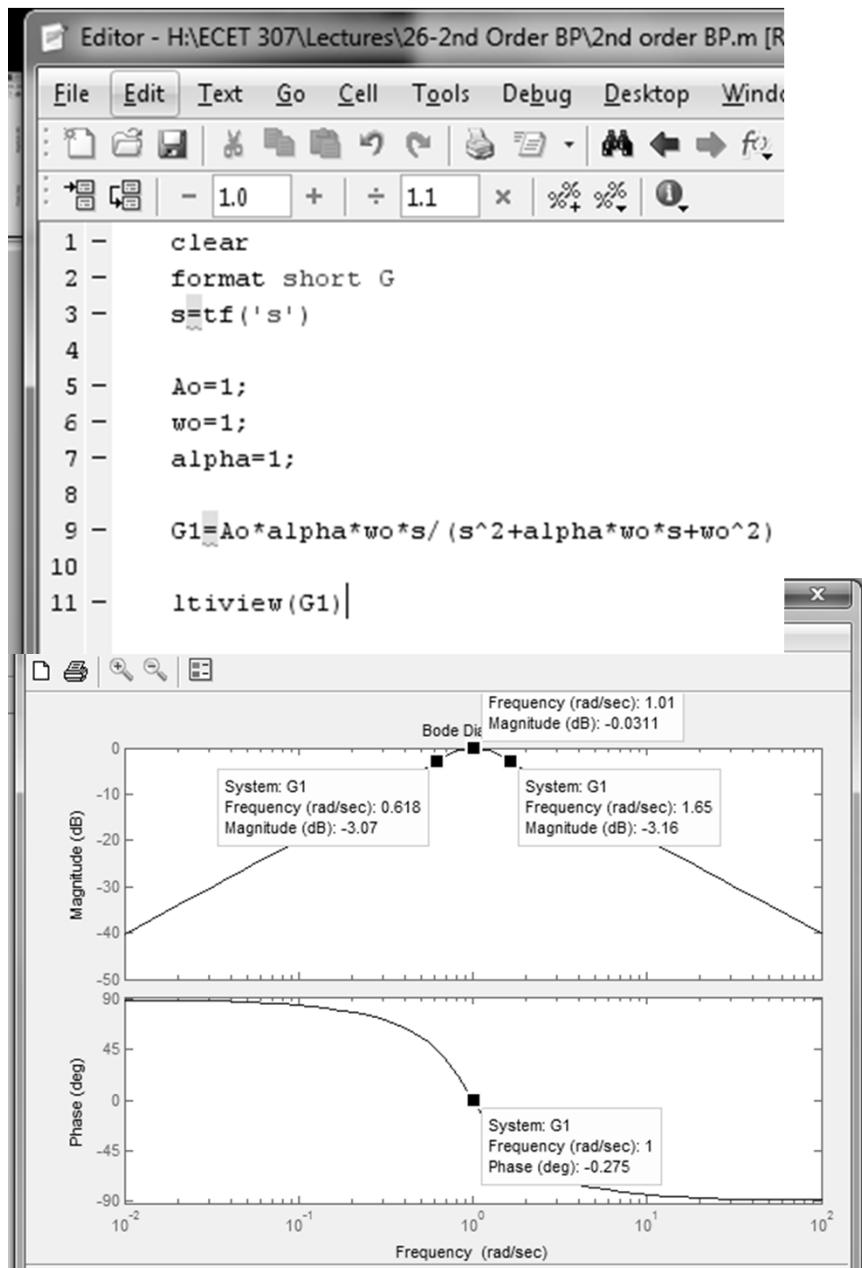


Second Order Bandpass Filters




- $G = \frac{A_o \alpha \omega_o s}{s^2 + \alpha \omega_o s + \omega_o^2}$
- A_o
- f_o magnitude phase
- f_{high} f_{low} Δf
- $f_o = \underline{\hspace{10em}}$

- $Q = \underline{\hspace{10em}}$
- $\alpha = \underline{\hspace{10em}}$

Second Order Bandpass Multi-feedback

$$G = \frac{A_o \alpha \omega_o s}{s^2 + \alpha \omega_o s + \omega_o^2}$$

$$1 \leq Q \leq 10$$

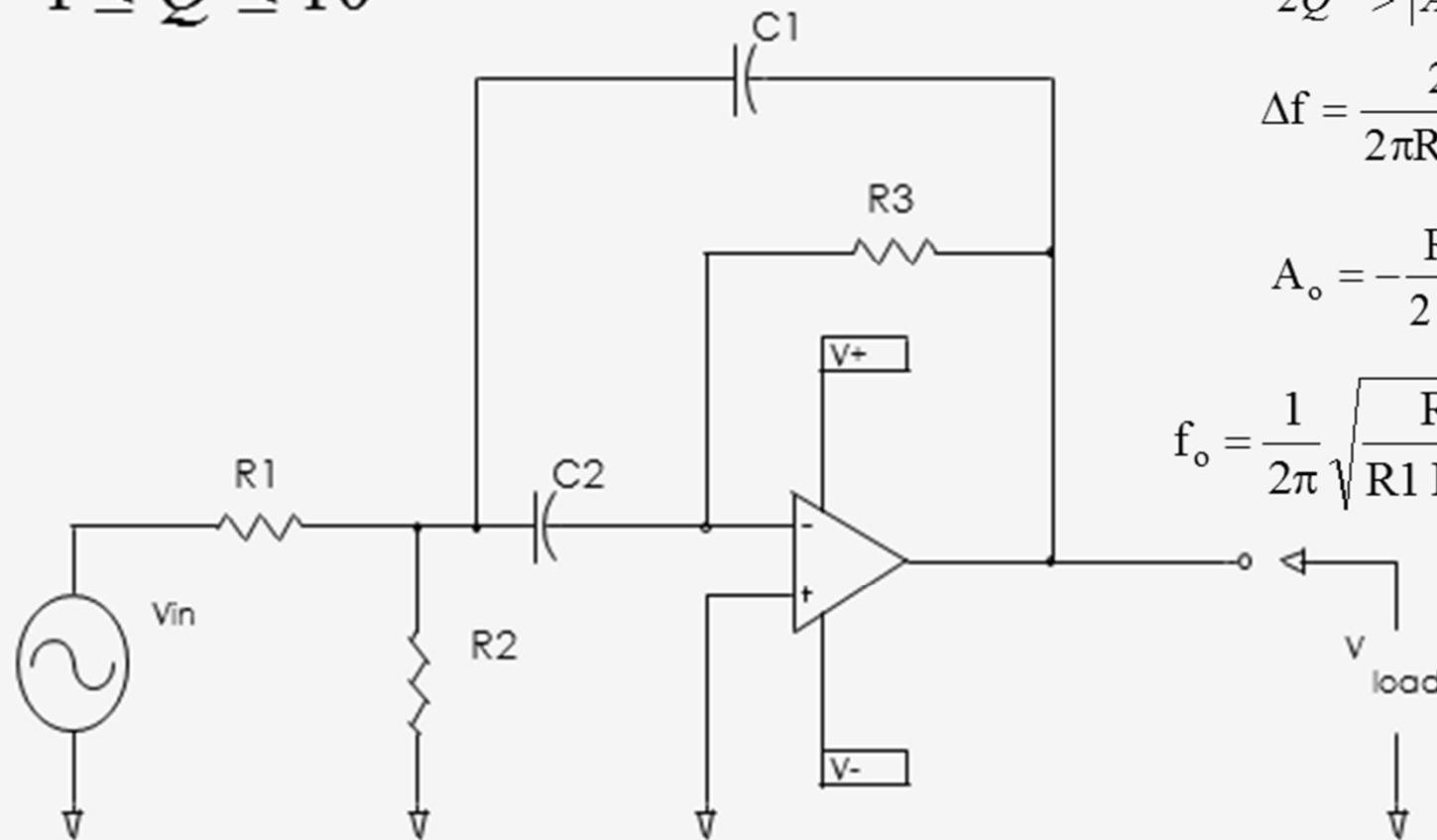


$$2Q^2 > |A_o|$$

$$\Delta f = \frac{2}{2\pi R_3 C}$$

$$A_o = -\frac{R_3}{2 R_1}$$
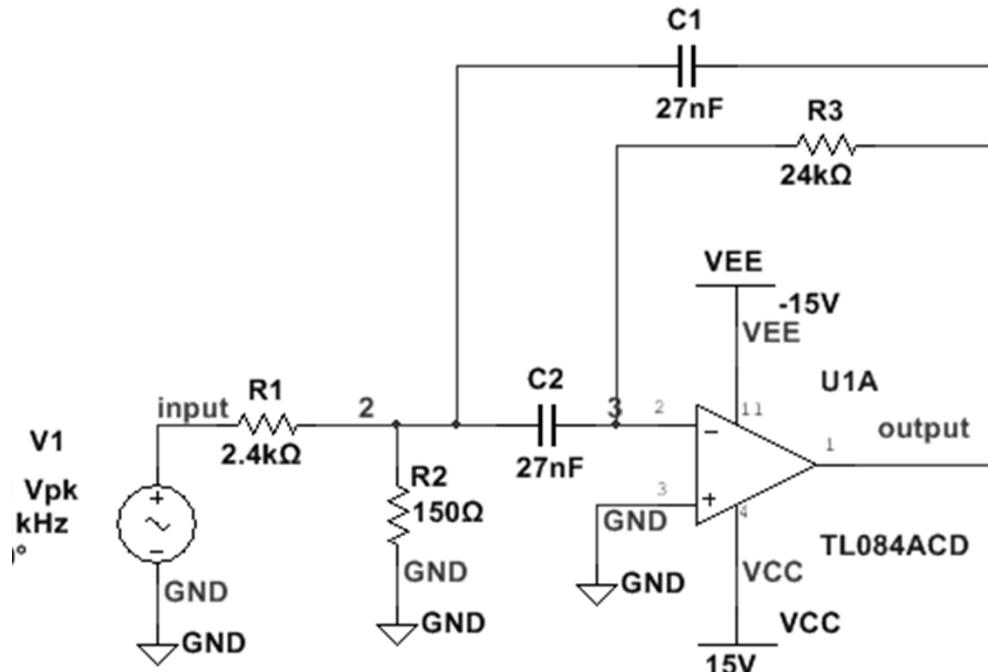
$$f_o = \frac{1}{2\pi} \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}}$$



Analysis Example

$$G = \frac{A_o \alpha \omega_o s}{s^2 + \alpha \omega_o s + \omega_o^2}$$




$$A_o =$$

$$\omega_o =$$


$$Q =$$

$$\alpha =$$

Analysis Example

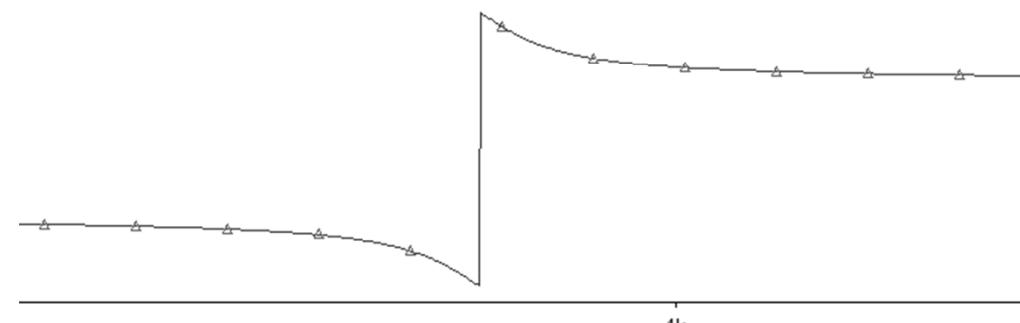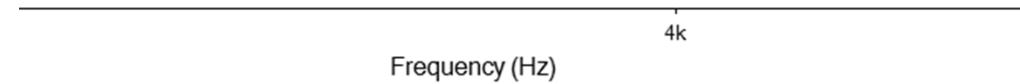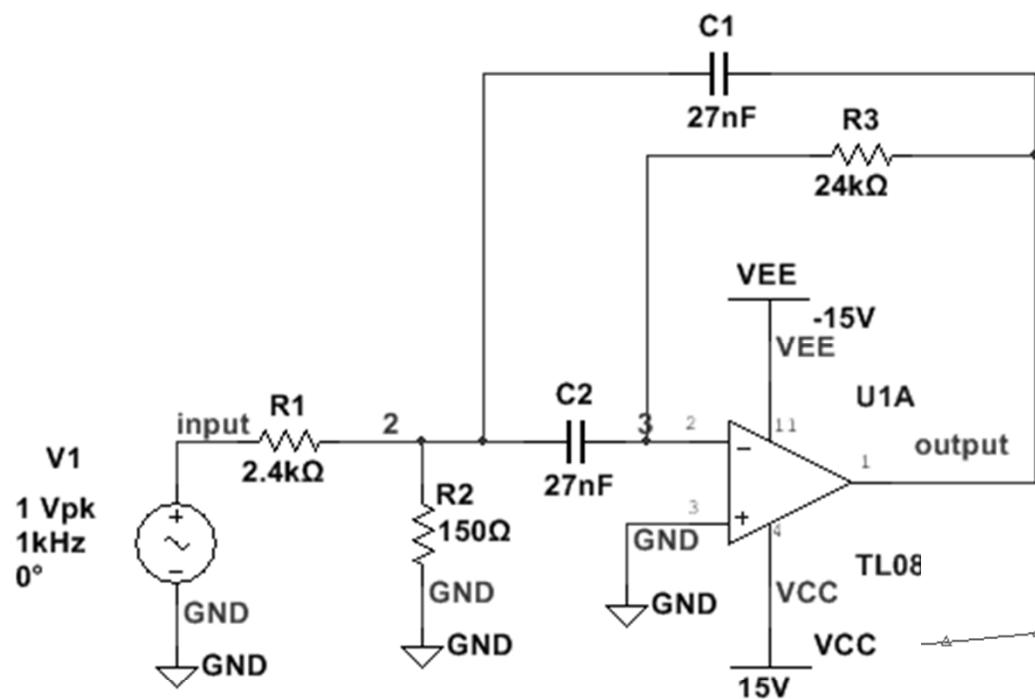

Design Example - MATLAB Check

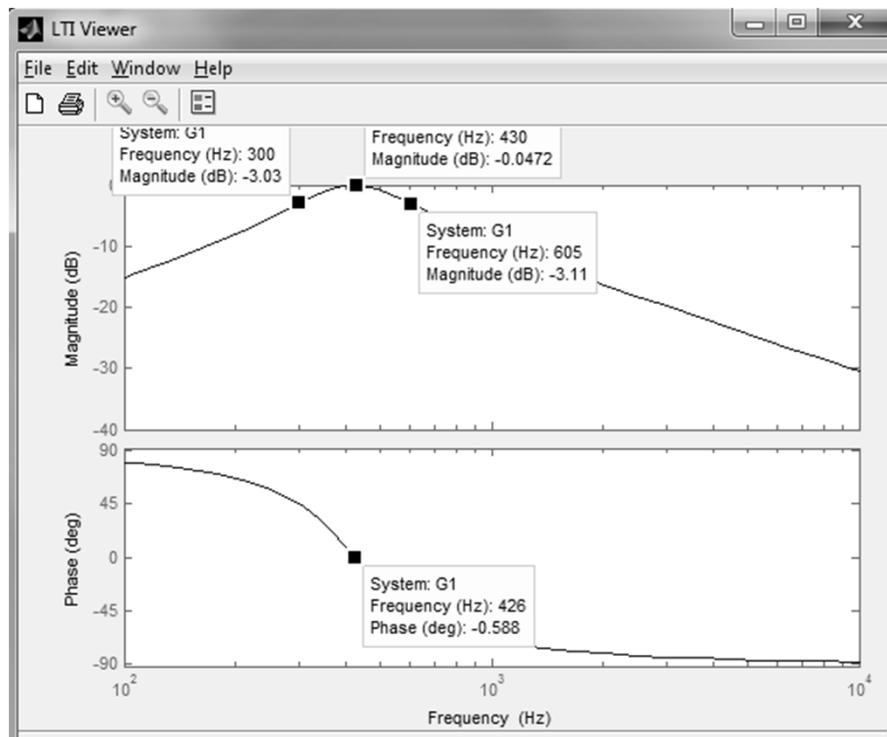

$$\bullet \quad G = \frac{A_o \alpha \omega_o s}{s^2 + \alpha \omega_o s + \omega_o^2}$$

$$f_{\text{high}} = 600 \text{ Hz}$$

$$f_{\text{low}} = 300 \text{ Hz}$$

$$A_o = 0 \text{ dB} = 1$$


$$f_0 = \underline{\hspace{2cm}}$$

$$\omega_0 = \underline{\hspace{2cm}}$$

$$Q = \underline{\hspace{2cm}}$$

$$\alpha = \underline{\hspace{2cm}}$$

Design Example

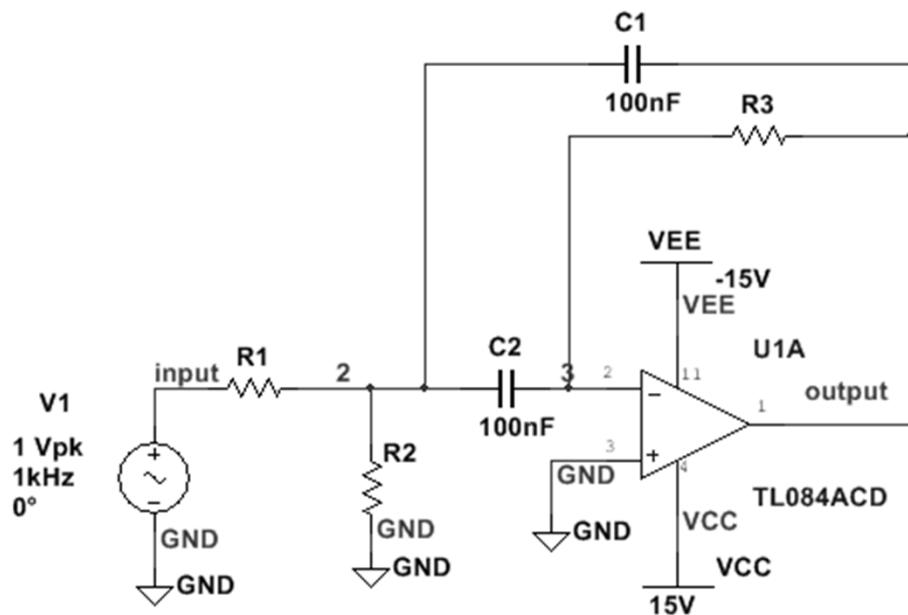

$$\Delta f =$$

$$f_o =$$

$$A_o =$$

$$\Delta f = \frac{2}{2\pi R_3 C}$$

Pick $C = \text{_____}$ (low audio)

$$R_3 = \frac{2}{2\pi \Delta f C}$$

$$A_o = -\frac{R_3}{2R_1}$$

$$R_1 =$$

After some algebra

$$R_2 = \frac{R_1}{4\pi^2 R_1 R_3 f_o^2 C^2 - 1} =$$