

# 1

## Analog Fundamentals

### Introduction

Linear electrical and electronic systems are made of resistors, capacitors, inductors, and op amps. These analog systems can be analyzed and designed with a few fundamental laws; Ohm's law, Kirchhoff's laws, and the voltage divider law. Once you understand the behavior of these few components, and can apply these laws, you will be able to handle the majority of analog systems.

### Objectives

Upon completion of this chapter, you will be able to analyze and design:

- Unloaded and loaded voltage dividers.
- Op amp circuits, including voltage followers, noninverting and inverting and difference amplifiers, and the inverting summer.
- A Thevenin's equivalent circuit for a complex system.
- Simple AC circuits using phasors.

## 1.1 Basic Principles


### Voltage Divider

Ohm's Law defines the relationship among the *voltage* (pressure), *current* (flow), and *resistance* (friction) in an electrical circuit.

#### Ohm's Law

$$V = I \times R \qquad I = \frac{V}{R} \qquad R = \frac{V}{I}$$

The units for  $V$  is **V, volts**;  $I$  is **A, amperes** or **amps**  $R$  is  **$\Omega$ , ohms**

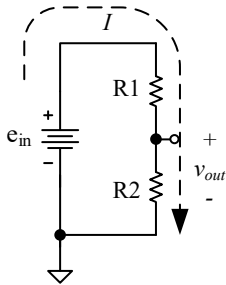

**Figure 1-1** Resistors in series to form a *voltage divider*

Placing two resistors end-to-end, in series, causes the total opposition to add, shown in Figure 1-1.

$$R_{\text{total}} = R1 + R2$$

The voltage divider, shown in Figure 1, is used to reduce the input voltage  $e_{\text{in}}$  to a lower (more usable) level,  $v_{\text{out}}$ . The input voltage  $e_{\text{in}}$  is applied across  $R_{\text{total}}$ , producing a current  $I_{\text{total}}$ .

$$I_{\text{total}} = \frac{e_{\text{in}}}{R_{\text{total}}}$$

This current flows through  $R1$ , then  $R2$ . So,  $I_{R2} = I_{\text{total}}$

$$v_{\text{out}} = v_{R2} = I_{R2} \times R2$$

$$v_{\text{out}} = I_{\text{total}} \times R2 = \frac{e_{\text{in}} \times R2}{R_{\text{total}}}$$

$$v_{\text{out}} = \frac{e_{\text{in}} \times R2}{R1 + R2}$$

or

$$\frac{v_{\text{out}}}{e_{\text{in}}} = \frac{R2}{R1 + R2}$$

#### Voltage Divider Law

## Op Amp Voltage Follower

One of the most common **linear** op amp circuits (one that uses negative feedback) is the voltage follower. Before beginning the analysis of this circuit, however, you must recall two facts about the op amp itself. These are illustrated in Figure 2.

First, since the input impedance is very high, the **signal** current that flows into either input terminal (- or +) is negligibly small.


$$i_{INV} \approx i_{NI} \approx 0$$

Second, the open loop gain,  $v_{out}/v_{in}$ , is extremely large. This means that for any reasonably sized output (any output in the linear region, not  $\pm V_{SAT}$ ),  $v_{in}$  must be negligibly small.


$$v_{in} \approx 0$$

The two inputs leads are at virtually the same potential. You certainly will never be able to measure any significant potential difference between the two inputs during linear operation.

Schematics for a voltage follower are given in Figure 1-3.

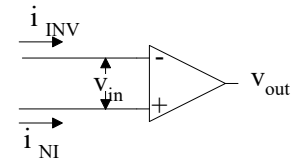

**Figure 1-2** Fundamental op amp characteristics

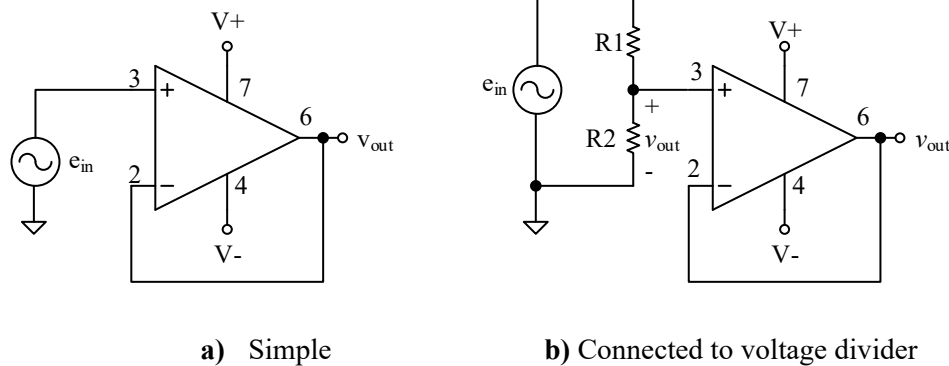

**Figure 1-3** Voltage follower

There is no difference between the two inputs. This means that since the noninverting input is at the source potential, so is the inverting input. However, the inverting input is tied **directly** to the output. The output voltage equals the voltage at the noninverting input, which is the input

**voltage follower**

$$i_{in} = 0$$

$$v_{out} = v_{in}$$


$$\text{gain} = 1$$

voltage. So the output voltage equals the input voltage, giving a gain of 1.


Remember, no significant current flows into the input of the op amp. So, this circuit will draw *no* current from  $e_{in}$ . More importantly, if a voltage divider (Figure 1-3b) with  $R_1$  and  $R_2$  was connected between  $e_{in}$  and the op amp, *none* of  $I_{R2}$  would flow into the op amp. The voltage across  $R_2$  would *not* change. It is said that the op amp (Figure 1-3a) does not **load down** the voltage divider (Figure 1-3b).
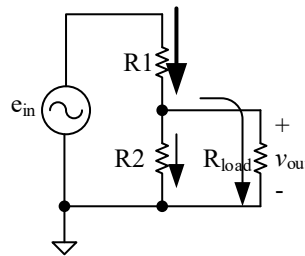
## The Effect of Loading and Buffering

Placing a load (a resistor or something else to use the output voltage) across the output of a voltage divider lowers that voltage. The act of taking energy out of a circuit lowers the energy available. That is *loading*. This is shown in Figure 1-4a.



a) Loaded voltage divider

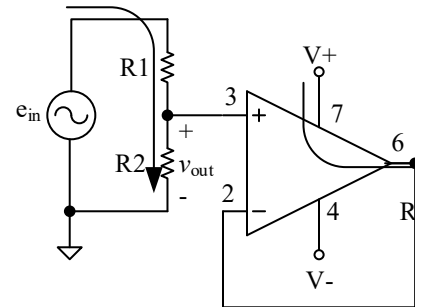

b) Op amp buffer

**Figure 1-4** Loading and buffering a voltage divider

Without the load resistor, *all* of the current that flows through  $R_1$  then flows through  $R_2$ , producing  $v_{out}$ . However, connecting  $R_{load}$  in parallel with  $R_2$  means that some of the current from  $R_1$  now is diverted to  $R_{load}$ . This lowers the current available to  $R_2$  and that lowers  $v_{out}$ .

However, placing a voltage follower (buffer) between the output of the voltage divider and the load prevents this loading. In Figure 1-4b, no current flows into the input of the op amp. So, all of the current from  $R_1$  flows through  $R_2$ , just as it did without the load connected. The voltage follower passes  $v_{out}$  to its output, where  $R_{load}$  is connected. The current for  $R_{load}$  now comes from the power supplies, through the op amp's output pin.

**Example 1-1**

- a. Given  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $e_{\text{in}} = 3 \text{ V}$ , calculate  $v_{\text{out}}$  with no load
- b. Calculate the effect of connecting  $R_{\text{load}} = 7 \text{ k}\Omega$ .

**Solution**

a.

$$v_{\text{out}} = \frac{3 \text{ V} \times 10 \text{ k}\Omega}{5 \text{ k}\Omega + 10 \text{ k}\Omega} = 2 \text{ V}$$


b.

Remember parallel circuits? Connecting  $R_{\text{load}}$  in parallel with  $R_2$  produces a lower resistance.

$$R_{\text{parallel}} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_{\text{load}}}} = \frac{1}{\frac{1}{10 \text{ k}\Omega} + \frac{1}{7 \text{ k}\Omega}} = 4.1 \text{ k}\Omega$$

$$v_{\text{out}} = \frac{3 \text{ V} \times 4.11 \text{ k}\Omega}{5 \text{ k}\Omega + 4.11 \text{ k}\Omega} = 1.35 \text{ V}$$

This is a 35% reduction (loading down) of  $v_{\text{out}}$ . Using the voltage follower of Figure 1-4b will prevent this error.

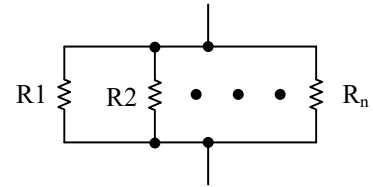**Resistors in Parallel****Figure 1-5** Resistors in parallel

$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}$$


$$R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n}}$$

or

$$R_{\text{parallel}} = (R_1^{-1} + R_2^{-1} + \cdots + R_n^{-1})^{-1}$$

**Noninverting Amplifier**

The voltage follower uses 100% negative feedback. But, as a result, it produced an output voltage no larger than its input. To produce a larger output, you must *reduce* the amount of negative feedback. This is done by the voltage divider made of  $R_f$  and  $R_i$  in Figure 1-6.

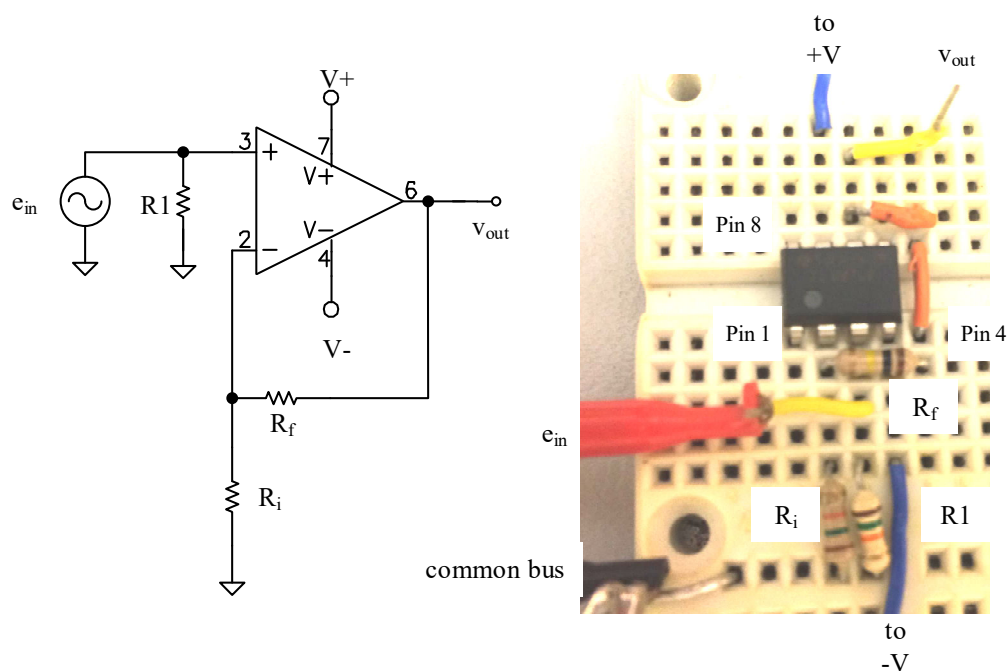

**Figure 1-6** Noninverting amplifier

The gain,  $A_v$  is

### Noninverting Amplifier Gain

$$A_v = \frac{v_{out}}{e_{in}} = 1 + \frac{R_f}{R_i}$$

The voltage gain can be derived by recalling that there is virtually no difference between the two inputs of the op amp (during linear operation with negative feedback).

$$v_{R_i} = e_{in}$$

$$i_{R_i} = \frac{v_{R_i}}{R_i} = \frac{e_{in}}{R_i}$$

Since no significant current flows into the inputs of an op amp, the current through  $R_i$  is also the current through  $R_f$ .

$$i_{R_i} = i_{R_f}$$

The voltage dropped by this current across  $R_f$  is

$$\begin{aligned} v_{R_f} &= i_{R_f} \times R_f \\ &= \frac{e_{in}}{R_i} \times R_f \end{aligned}$$

The output voltage is the voltage across  $R_i$  plus the voltage across  $R_f$ .


$$\begin{aligned} v_{out} &= v_{R_i} + v_{R_f} \\ &= e_{in} + \frac{e_{in}}{R_i} R_f \\ &= e_{in} \left( 1 + \frac{R_f}{R_i} \right) \end{aligned}$$

Since the gain is the output voltage divided by the input voltage,

$$A_v = \frac{v_{out}}{e_{in}} = 1 + \frac{R_f}{R_i}$$

The resistor  $R_1$  has two functions. First it is an input pull-down resistor, providing a path from ground for the nA of *bias* current that must flow into the input of the op amp for it to work correctly. If the input is left open, then this tiny amount of current (that is usually ignored) cannot properly bias the input transistors into their linear region. They turn off, sending the op amp's output to the rail, i.e. the maximum positive or negative voltage available from the supplies.

Secondly, the impedance that  $e_{in}$  sees looking into the noninverting terminal of the op amp is in the  $G\Omega$ . Though this is so large as to often be considered an open, it does vary from IC to IC, and with operating conditions. Resistor  $R_1$  sets that impedance to a defined, stable, predictable value.

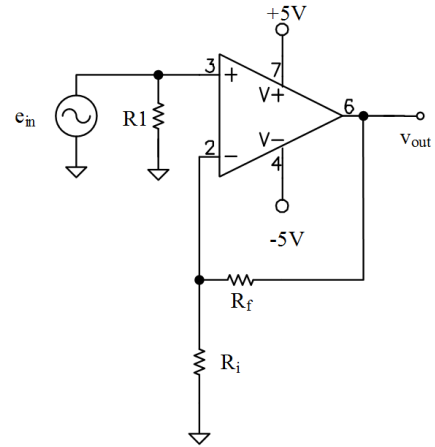

**Figure 1-6** Noninverting amplifier


### Noninverting Amp input Impedance

with  $R_1$ :  
 $Z_{in} = R_1$

without  $R_1$ :  
 $Z_{in} = G\Omega$

## Inverting Amplifier

The circuit shown in Figure 1-7 is an *inverting* amplifier. It is inverting because  $e_{in}$  is, eventually, connected to the inverting input rather than the noninverting input (as it is in the noninverting amplifier in Figure 1-6). *Negative* feedback is needed to assure linear operation, an amplifier. In Figure 1-7, this is provided from the output, through  $R_f$  to the inverting input. That is just how negative feedback is provided for the noninverting amplifier in Figure 1-6 too.

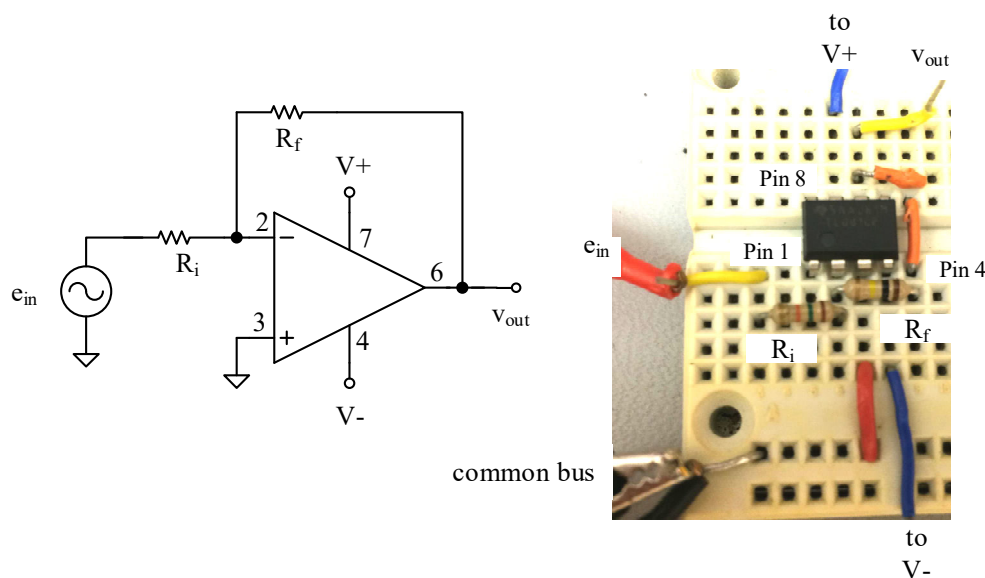

**Figure 1-7** Inverting amplifier

The inverting input is at

**virtual ground.**

**Inverting Amp  
input Impedance**

$$Z_{in} = R_i$$

This negative feedback drives the output voltage to whatever potential is necessary to assure that there is no significant difference between the inverting input and the noninverting input. Since the noninverting input is connected directly to ground, the inverting input voltage is also at (nearly, *virtually*) ground. This is significantly different from the noninverting amplifier, and dictates its operation.

This means that between the input source,  $e_{in}$ , and ground (or virtual ground) is  $R_i$ . That resistor sets the input impedance. This is a significant consideration when analyzing or designing an inverting amplifier with an op amp.



Figure 1-8 shows the voltages and currents around the inverting amplifier. Because of negative feedback, the inverting input pin is driven to virtual ground, 0 V. This puts the entire input voltage across  $R_i$

$$V_{Ri} = e_{in}$$

$$I_{Ri} = \frac{V_{Ri}}{R_i} = \frac{e_{in}}{R_i}$$

The current that flows into the input pin of the op amp is so small that it can be ignored. Summing the currents at that input pin gives

$$I_{Ri} = I_{\text{input pin}} + I_{Rf}$$

$$I_{\text{input pin}} = 0$$

$$I_{Ri} = I_{Rf}$$

$$I_{Ri} = \frac{e_{in}}{R_i} = I_{Rf}$$

The voltage across  $R_f$ ,  $V_{Rf}$ , is

$$V_{Rf} = I_{Rf} \times R_f$$


$$V_{Rf} = \frac{e_{in}}{R_i} R_f$$

Look carefully at the direction of  $I_{Rf}$  and the polarity of the output voltage. Current can only flow left-to-right through  $R_f$  if the output voltage is negative with respect to the left end of  $R_f$ , virtual ground.

$$V_{out} = -V_{Rf}$$

$$V_{out} = -\frac{e_{in}}{R_i} R_f = -\frac{R_f}{R_i} e_{in}$$

$$A_v = \frac{V_{out}}{e_{in}} = -\frac{R_f}{R_i}$$

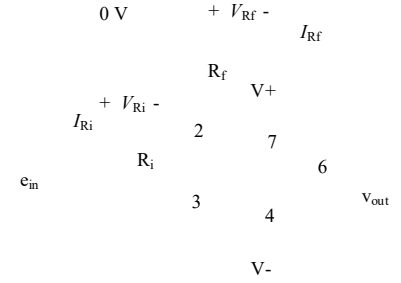


**Figure 1-8** Inverting amp gain derivation

**Inverting amplifier gain**

## Inverting Summer

Several voltage sources can be combined by connecting each, through its own input resistor to the virtual ground of the inverting amplifier, creating an *inverting summer*. This is shown in Figure 1-8.

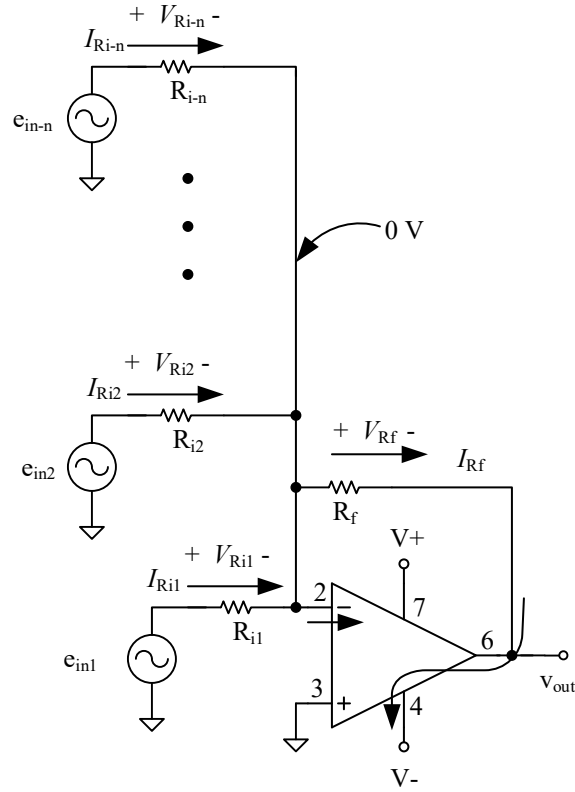

**Figure 1-8** Inverting summer schematic

Each source sends its current into the virtual ground node where they combine to create the current through the feedback resistor.

$$I_{Ri1} = \frac{V_{Ri1}}{R_{i1}} = \frac{e_{in1}}{R_{i1}} \quad I_{Ri2} = \frac{V_{Ri2}}{R_{i2}} = \frac{e_{in2}}{R_{i2}} \quad I_{Ri-n} = \frac{V_{Ri-n}}{R_{i-n}} = \frac{e_{in-n}}{R_{i-n}}$$

$$I_{Rf} = I_{R1} + I_{R2} + \cdots + I_{R-n}$$

$$I_{Rf} = \frac{e_{in1}}{R_{i1}} + \frac{e_{in2}}{R_{i2}} + \cdots + \frac{e_{in-n}}{R_{i-n}}$$

That current produces the output voltage.

$$V_{out} = -I_{Rf} \times R_f$$

$$V_{out} = -\left(\frac{e_{in1}}{R_{i1}} + \frac{e_{in2}}{R_{i2}} + \cdots + \frac{e_{in-n}}{R_{i-n}}\right) R_f$$

$$V_{out} = -\left(\frac{R_f}{R_{i1}} e_{in1} + \frac{R_f}{R_{i2}} e_{in2} + \cdots + \frac{R_f}{R_{i-n}} e_{in-n}\right)$$

**Inverting summer output equation**

Each input source has its own gain, set by its input resistor and by the feedback resistor. Changing  $R_{i-n}$  changes the contribution that source has on the mix of signals. Changing  $R_f$  changes the overall gain without altering the proportion that each separate input contributes.

Remember, each input resistor is connected to virtual ground. So it sets the input impedance that its source experiences, and the current its source must provide.

### Example 1-2

Design an audio mixer to combine a voice, a guitar, and a drum. Each input must have an:

- impedance of at least 10 k $\Omega$ .
- adjustable gain (mix) 0.5 to 50.

### Solution


Refer to Figure 1-8. Make each  $R_i$  with a fixed resistor in series with a rheostat.

$$R_{i-fixed} = 10 \text{ k}\Omega$$

Even when the rheostat is set to 0  $\Omega$ , the input impedance is 10 k $\Omega$ .

Each signal's gain is set by
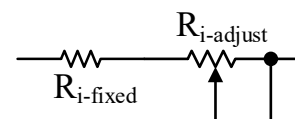
$$A_{v-n} = \frac{V_{out}}{e_{in-n}} = -\frac{R_f}{R_{i-n}}$$



The smaller  $R_{i-n}$ , the larger the gain. So when the rheostat is set to  $0\ \Omega$  the gain will be at its maximum, 50.

$$R_f = A_{v-n} \times R_{i-n} = 50 \times 10\ \text{k}\Omega = \mathbf{500\ \text{k}\Omega}$$

The smallest gain comes when  $R_{i-n}$  is at its largest.

$$A_{v-n} = \frac{V_{\text{out}}}{e_{\text{in-n}}} = -\frac{R_f}{R_{i-n}} = \frac{R_f}{R_{i-\text{fixed}} + R_{i-\text{adjust}}}$$

$$R_{i-\text{fixed}} + R_{i-\text{adjust}} = \frac{R_f}{A_{v-n\ \text{min}}}$$

$$R_{i-\text{adjust}} = \frac{R_f}{A_{v-n\ \text{min}}} - R_{i-\text{fixed}}$$

$$R_{i-\text{adjust}} = \frac{500\ \text{k}\Omega}{0.5} - 10\ \text{k}\Omega$$

$$R_{i-\text{adjust}} = 990\ \text{k}\Omega$$

Select  $R_{i-\text{adjust}} = \mathbf{1\ \text{M}\Omega}$ .

---

## Difference Amplifier: Fundamentals

The inverting amplifier can be combined with the noninverting amplifier to create a circuit with several very useful characteristics. Its schematic is shown in Figure 1-9.

Proper operation requires that

$$R_{i1} = R_{i2} = R_i$$

$$R_{f1} = R_{f2} = R_f$$

This matching should be as perfect as possible, 1% or closer.

Assuming a perfect match, the output voltage is

Signals can be **amplified**.

$$v_{\text{out}} = \frac{R_f}{R_i} (e_{\text{in1}} - e_{\text{in2}})$$