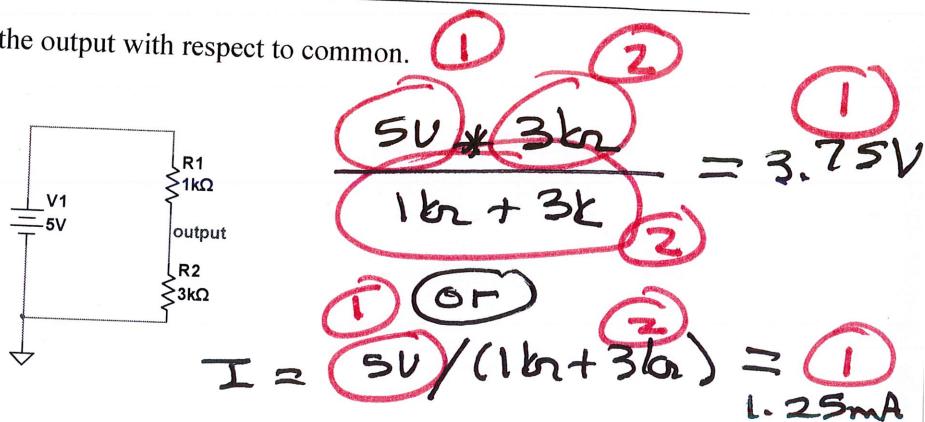


Show all off your work. No work => no credit.  
Include units properly in all calculations and answers. No units => no credit.


1.

- a. [6%] Calculate the voltage at the output with respect to common.



$$V_{output} = 3.75V$$

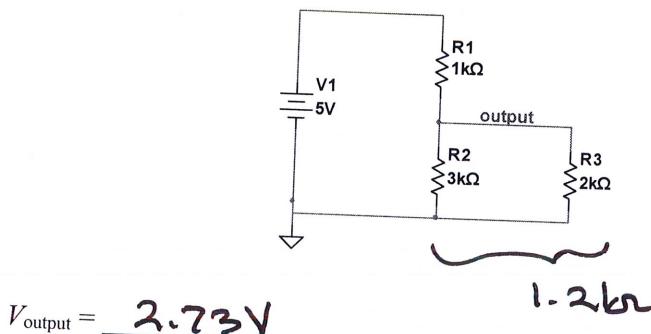- b. [9%] Calculate the voltage at the output with respect to common.





$$R_{23} = \left( (3k\Omega)^{-1} + (2k\Omega)^{-1} \right)^{-1} = 1.2k\Omega$$

$$V_{output} = \frac{5V * 1.2k\Omega}{1k\Omega + 1.2k\Omega} = 2.73V$$

Answers below are an EXAMPLE of a correct solution. Other solutions may also be right

## 2. Impedance Combination

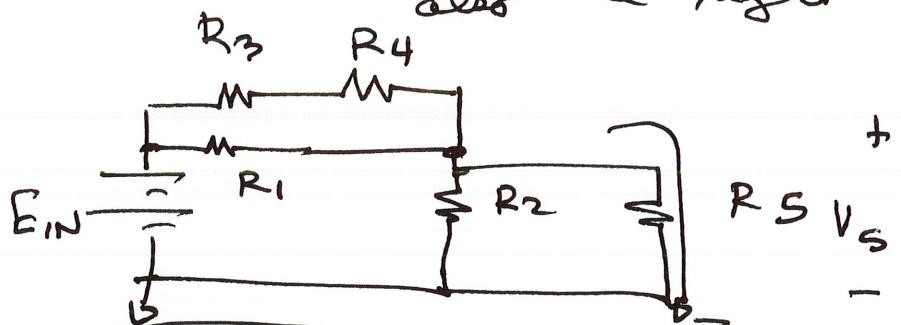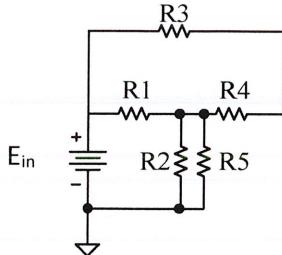


[25%] Complete a plan to calculate the current through  $R_5$ . Place the equations in the right order, using the nomenclature developed for solving a circuit using impedance combination. Enter your equations, in the correct order, in the numbered cells below.

Indicate the correct equations. Do not say  $R_{ab} = R_a//R_b$  if  $R_a$  is in parallel with  $R_b$ . Instead, provide the correct equation to actually calculate  $R_{ab}$  given the values of  $R_a$  and  $R_b$ .

Redraw the schematic as often as necessary to clearly explain your plan.

Be sure to indicate current directions on the schematic, and voltage drops with + - or - + across the affected component.

1	$R_{25} = (R_2^{-1} + R_5^{-1})^{-1}$	14
2	$R_{34} = R_3 + R_4$	15
3	$R_{134} = (R_{34}^{-1} + R_1^{-1})^{-1}$	16
4	$V_{25} = \frac{E_{in}}{R_{134} + R_{25}}$	17
5	$V_s = V_{25}$	18
6	$I_{R5} = V_s / R_5$	19
7		20
8		21
9		22
10		23
11		24
12		25
13		26

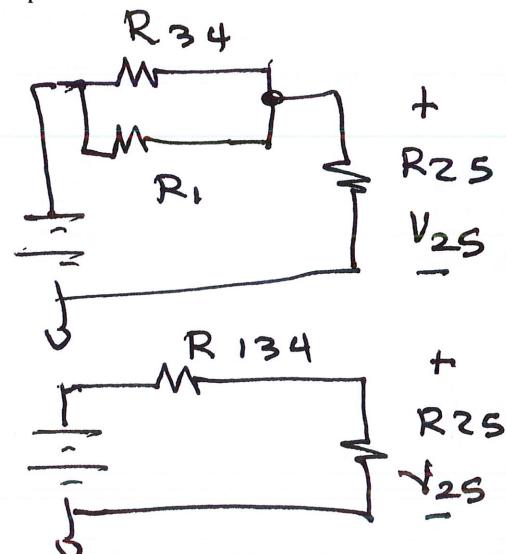

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_0^t 5i \, dt$$

CAP

$$i = \frac{1}{L} \int_0^t v \, dt$$


$$v = L \frac{di}{dt}$$

INDUCTOR

Put your calculator in the **Exact mode under Document Settings**

### 3. Capacitors and Inductors in the Time Domain

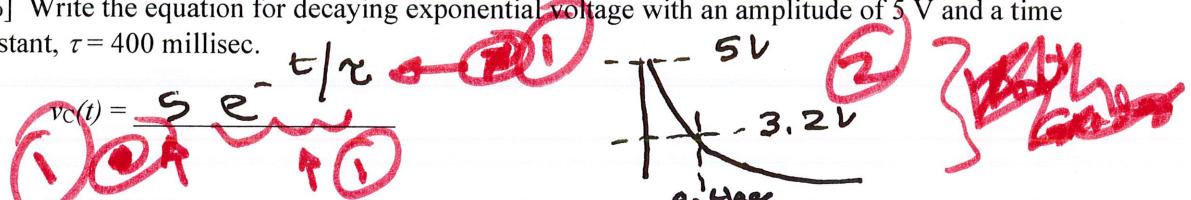- a. [5%] Write the equation for decaying exponential voltage with an amplitude of 5 V and a time constant,  $\tau = 400$  msec.



- b. [10%] Write the equation for the current through a  $2 \mu F$  capacitor with waveform from question 3.a. applied across it.

Begin by recording below the differential or integral relationship of  $i_C$  and  $v_C$  in terms of  $i_C$ ,  $C$ , and  $v_C$ .

$$\boxed{5} i_C = C \frac{dv_C}{dt} = \frac{2\mu}{5} \frac{d}{dt} (5e^{-t/\tau})$$

Solve this equation.  $i_C = \frac{-e^{-t/0.4}}{4000}$

Write this equation in **standard form**.  $i_C = -2 \mu e^{-t/0.4}$

- c. [5%] Write the equation for a voltage *ramp* that begins at 0 V and rises 5 V in 0.6 seconds.


$$v(t) = \frac{8.33}{0.6} t \quad \frac{5}{0.6} t = 8.33 t$$

- d. [10%] Write the equation for the current through a 300 mH inductor which has the voltage ramp from step c driven into it.


Begin by recording below the differential or integral relationship of  $i_L$  and  $v_L$  in terms of  $i_L$ ,  $L$ , and  $v_L$ .

$$\boxed{5} i_L = \frac{1}{300m} \int_0^t 8.33 t \, dt = \frac{833}{60} t^2$$

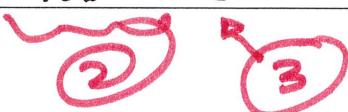Solve this equation.  $i_L = \frac{13.88 t^2}{2}$


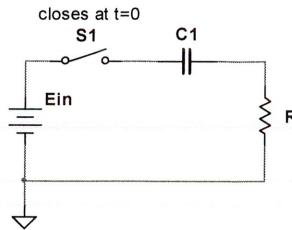
#### 4. RC Circuit solution with Differential Equations



- a. [5%] Use Kirchhoff's voltage law to write an equation that sums the voltages around the loop.

$$E_{in} = V_C + V_R$$

- b. [7%] Use Ohm's law and the relationship of voltage and current for a capacitor to convert that voltage equation to a first order differential equation with current, (and its derivative) as the independent variable.

Put your final answer in the form needed to use **deSolve** on the calculator.

$$\begin{aligned} E_{in} &= \frac{1}{C} \int_0^t i \, dt + i R \\ 0 &= \frac{1}{C} i + i' R \end{aligned}$$

$$i' = -\frac{1}{RC} i$$

- c. [6%] What are:

$$i(\infty) = \frac{0}{2} \quad i(0^+) = \frac{E_{in}}{R} \quad \tau = \frac{RC}{2}$$

- d. [12%] Solve the differential equation. Write the exact entry into your calculator, the solution for  $i(t)$  given by the calculator. Then put this equation in standard form.

Calculator entry  $\text{deSolve}(i' = \frac{-1}{r+c} * i \text{ and } i(0) = \frac{e}{r}, t, i)$

Calculator answer  $\frac{E_{in} e^{-t/(C+R)}}{R}$

Standard form  $i(t) = \frac{E_{in}}{R} e^{-t/RC}$

$v_R(t) = E_{in} e^{-\frac{t}{RC}}$

ECET 337  
Exam 1B  
Spring 2025


Solution

Name \_\_\_\_\_

Show *all* off your work. No work => no credit.  
Include units properly in all calculations and answers. No units => no credit.

1.

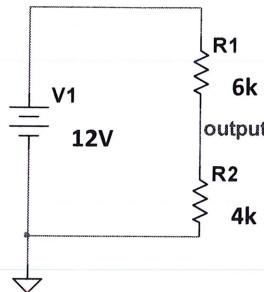- a. [6%] Calculate the voltage at the output with respect to common.



$$V_{\text{out}} = \frac{12V * 4k\Omega}{6k\Omega + 4k\Omega} \quad \textcircled{1}$$

$$= 4.8V \quad \textcircled{2}$$

(OR)

$$I = 12V / (4k\Omega + 6k\Omega)$$


$$I = 1.2mA$$

$$V = 1.2mA * 4k\Omega =$$

$$= 4.8V$$

$$V_{\text{output}} = 4.8V$$

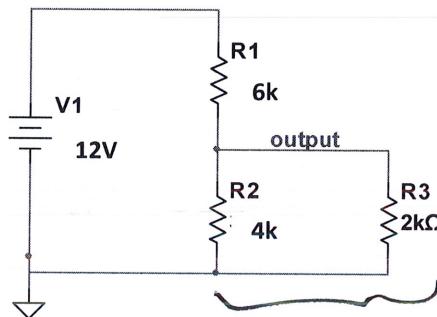- b. [9%] Calculate the voltage at the output with respect to common.



$$R_{23} = \left( \frac{1}{4k\Omega} + \frac{1}{2k\Omega} \right)^{-1}$$

$$= 1.33k\Omega \quad \textcircled{3}$$


$$V_{\text{output}} = 2.177V$$

$$V_{\text{out}} = \frac{12V * 1.33k\Omega}{6k\Omega + 1.33k\Omega} \quad \textcircled{1}$$

$$= 2.177V \quad \textcircled{2}$$

$$= 2.177V \quad \textcircled{1}$$

## 2. Impedance Combination

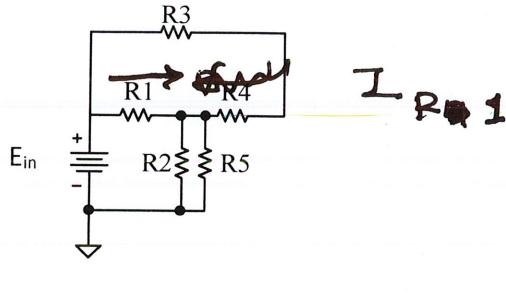

$R_1$


[25%] Complete a plan to calculate the current through  ~~$R_1$~~ . Place the equations in the right order, using the nomenclature developed for solving a circuit using impedance combination. Enter your equations, in the *correct order*, in the numbered cells below.

Indicate the correct equations. Do *not* say  $R_{ab} = R_a/R_b$  if  $R_a$  is in parallel with  $R_b$ . Instead, provide the correct equation to actually calculate  $R_{ab}$  given the values of  $R_a$  and  $R_b$ .

Redraw the schematic as often as necessary to clearly explain your plan.

Be sure to indicate current directions on the schematic, and voltage drops with + - or - + across the affected component.

1	$R_{34} = R_3 + R_4$
2	$R_{25} = R_2^{-1} + R_5^{-1}$
3	$R_{134} = R_1 + R_{34}$
4	$R_{134} = (R_1^{-1} + R_{34}^{-1})^{-1}$
5	$V_{134} = E_{in} R_{134} / (R_{134} + R_{25})$
6	$V_{R_1} = V_{134}$
7	$I_{R_1} = V_{R_1} / R_1$
8	
9	
10	
11	
12	
13	

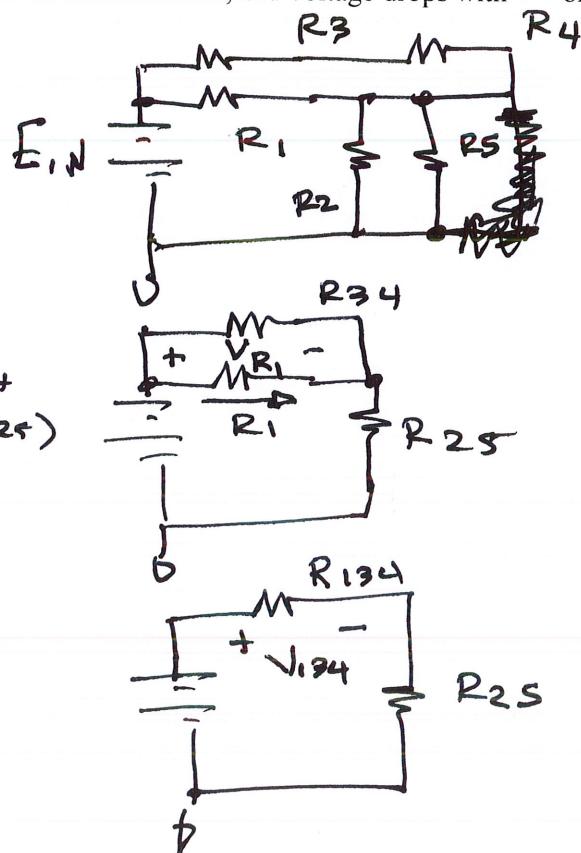

$$i = C \frac{dv}{dt}$$


**Put your calculator in the *Exact* mode under Document Settings**

### 3. Capacitors and Inductors in the Time Domain

- a. [5%] Write the equation *rising* exponential voltage with an amplitude of 6 V and a time constant,  $\tau = 200$  millsec.

$$v_C(t) = C(1 - e^{-t/\tau})$$

(1) 

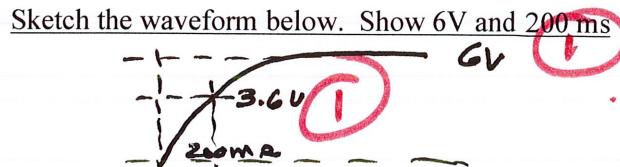

- b. [10%] Write the equation for the current through a  $5 \mu F$  capacitor with waveform from question 3.a. applied across it.

Begin by recording below the differential or integral relationship of  $i_C$  and  $v_C$  in terms of  $i_C$ ,  $C$ , and  $v_C$ .

$$i = C \frac{dv}{dt} = 5 \mu \frac{d}{dt} (1 - e^{-t/0.2})$$

(5)

$$\frac{5}{40000} e^{-st}$$

Solve this equation.  $i_C = \frac{5}{40000}$

Write this equation in *standard* form.  $i_C = \frac{150}{25 \mu} e^{-t/0.2}$  (5)

- c. [5%] Write the equation for a voltage *ramp* that begins at 0 V and rises 12 V in 2 seconds.

$$v(t) = \frac{12}{2} t \quad \frac{12}{2} t = 6t$$

(2) 


- d. [10%] Write the equation for the current through a 700 mH inductor which has the voltage ramp from step c driven into it.

Begin by recording below the differential or integral relationship of  $i_L$  and  $v_L$  in terms of  $i_L$ ,  $L$ , and  $v_L$ .


$$i = \frac{1}{L} \int_0^t v dt = \frac{1}{0.7} \int_0^t 6t dt$$

(5)

Solve this equation.  $i_L = \frac{\frac{30}{7}}{2} t^2 = 4.29 t^2$

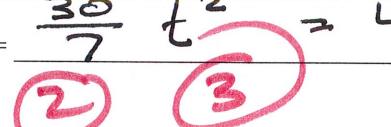(2) 
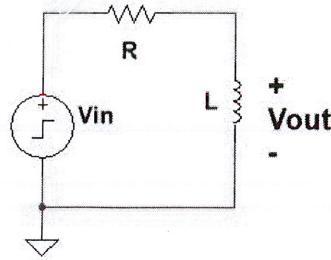
#### 4. RL Circuit solution with Differential Equations



- a. [5%] Use Kirchhoff's voltage law to write an equation that sums the voltages around the loop.

$$V_{in} = V_R + V_L$$

- b. [7%] Use Ohm's law and the relationship of voltage and current for an inductor to convert that voltage equation to a first order differential equation with current, (and its derivative) as the independent variable.

Put your final answer in the form needed to use **deSolve** on the calculator.

$$\begin{aligned} V_{in} &= iR + L \frac{di}{dt} \\ \frac{V_{in}}{L} - i \frac{R}{L} &= i' \end{aligned}$$

$$i' = -\frac{R}{L}i + \frac{V_{in}}{L}$$

- c. [6%] What are:

$$i(\infty) = \frac{V_{in}}{R} \quad i(0^+) = 0 \quad \tau = \frac{L}{R}$$

- d. [12%] Solve the differential equation. Write the exact entry into your calculator, the solution for  $i(t)$  given by the calculator. Then put this equation in standard form.

Calculator entry  $\text{deSolve}(i' = -\frac{R}{L}i + \frac{V_{in}}{L} \text{ and } i(0) = 0, t, i)$

Calculator answer  $\frac{V_{in}}{R} - \frac{e^{-\frac{Rt}{L}}}{R} \times V_{in}$

Standard form  $i(t) = \frac{V_{in}}{R} (1 - e^{-t/\tau})$   $\tau = L/R$

$v_R(t) = V_{in} (1 - e^{-t/\tau})$   $\tau = L/R$