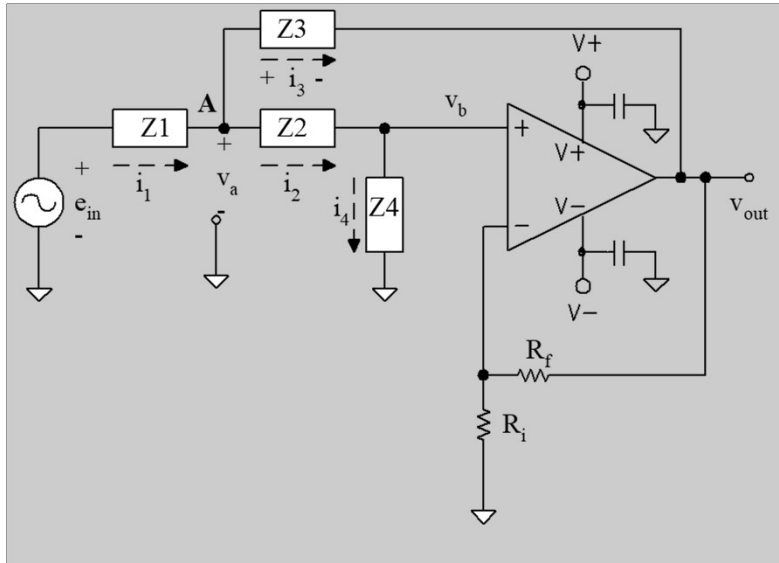


Second Order LP Butterworth Filters

- Transfer Function $G = \frac{A_o \omega_o^2}{s^2 + 2\xi \omega_o s + \omega_o^2}$
- Characteristics
 - _____
 - $\xi =$ _____
 - Damping _____
 - f_o (-90 deg shift) _____ f_{-3dB}
 - _____ dB/decade or _____ dB/octave roll off
- MATLAB

$$V_{out} = A_o V_b$$

Second Order L



$$V_{out} = A_o V_b$$

$$A_o = 1 + \frac{R_f}{R_i}$$

Purdue University

So

$$V_b = \frac{V_{out}}{A_o}$$

Assuming that no current flows into the op amp,

$$i_4 = \frac{V_b}{Z_4}$$

$$i_2 = i_4 = \frac{V_b}{Z_4}$$

At node A,

$$V_a = i_4 (Z_2 + Z_4)$$

$$\text{Combining these yields } V_a = \frac{V_b}{Z_4} (Z_2 + Z_4)$$

Current into the filter, i_1 , is the difference in potential across Z_1 divided by Z_1 .

$$i_1 = \frac{e_{in} - V_a}{Z_1} = \frac{e_{in}}{Z_1} - \frac{V_a}{Z_1}$$

$$\text{Substitute for } V_a: i_1 = \frac{e_{in}}{Z_1} - \frac{V_b (Z_2 + Z_4)}{Z_1 Z_4}$$

The current through the feedback impedance, i_3 , can be calculated by summing the currents at node A.

$$i_3 = i_1 - i_2$$

Combine the equations for i_1 and i_2 .

$$i_3 = \frac{e_{in}}{Z_1} - \frac{V_b (Z_2 + Z_4)}{Z_1 Z_4} - \frac{V_b}{Z_4}$$

Summing the loop from node A, Z_3 , and the output yields

$$V_a - i_3 Z_3 - V_{out} = 0$$

$$V_{out} = V_a - i_3 Z_3$$


Substitute for i_3 .

$$V_{out} = \frac{V_b}{Z_4} (Z_2 + Z_4) - \left[\frac{e_{in}}{Z_1} - \frac{V_b (Z_2 + Z_4)}{Z_1 Z_4} - \frac{V_b}{Z_4} \right] Z_3$$

Combine this with the initial relationship for the input to output voltages of the op amp.

$$V_{out} = A_o V_b$$

Second Order LP

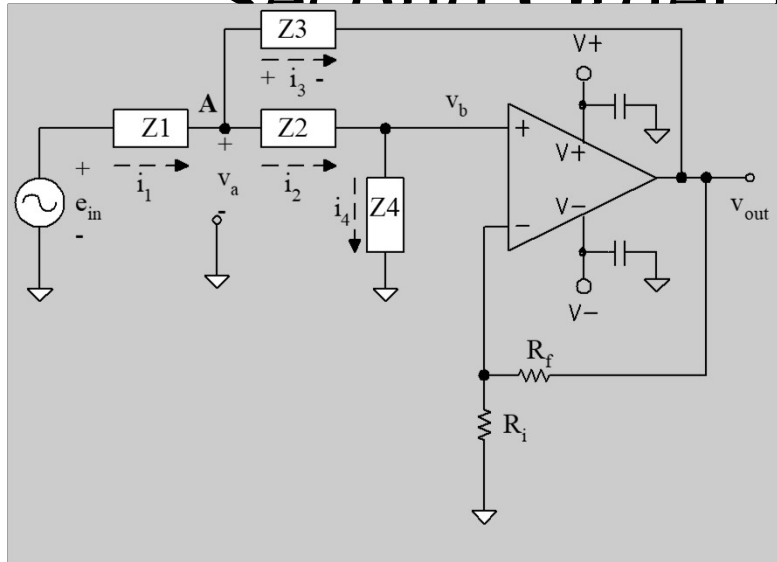

$$A_{int} = 1 + \frac{R_f}{R_i}$$

$$\omega_o^2 = \frac{1}{R^2 C^2}$$

$$\omega_o = \frac{1}{RC}$$

$$f_o = \frac{1}{2\pi RC}$$

$$\alpha \omega_o = \frac{3 - A_o}{RC}$$

Purd

$$\alpha = 3 - A_{int}$$

$$V_{out} = \frac{V_b}{Z4} (Z2 + Z4) - \left[\frac{e_{in}}{Z1} - \frac{V_b(Z2 + Z4)}{Z1Z4} - \frac{V_b}{Z4} \right] Z3$$

$$\frac{V_{out}}{e_{in}} = \frac{A_o Z3 Z4}{Z1 Z2 + Z2 Z3 + Z3 Z4 + Z1 Z3 + Z1 Z4 (1 - A_o)}$$

$$\begin{aligned} \frac{V_{out}}{E_{in}} &= \frac{\frac{A_o}{C^2 s^2}}{R^2 + \frac{R}{Cs} + \frac{1}{C^2 s^2} + \frac{R}{Cs} + \frac{R}{Cs} (1 - A_o)} \\ &= \frac{\frac{A_o}{C^2 s^2}}{\frac{R^2 C^2 s^2 + RCs + 1 + RCs + RCs(1 - A_o)}{C^2 s^2}} \\ &= \frac{A_o}{R^2 C^2 s^2 + 2RCs + RCs(1 - A_o) + 1} \\ \frac{V_{out}}{E_{in}} &= \frac{A_o}{R^2 C^2 s^2 + RC[2 + (1 - A_o)]s + 1} \end{aligned}$$

The quadratic in the denominator is more easily solved if the coefficient of s^2 is 1. Dividing numerator and denominator by $R^2 C^2$, you obtain

$$\frac{V_{out}}{E_{in}} = \frac{\frac{A_o}{R^2 C^2}}{s^2 + \left(\frac{3 - A_o}{RC} \right) s + \frac{1}{R^2 C^2}}$$

Second-order systems have been studied extensively. Mechanical and chemical as well as electrical second-order systems behave similarly. One transfer function is

$$\frac{A_o \omega_o^2}{s^2 + \alpha \omega_o s + \omega_o^2}$$

where

Sallen Key Implementation

$$G = \frac{A_o \omega_o^2}{s^2 + 2\xi \omega_o s + \omega_o^2}$$

$$f_o = \underline{\hspace{2cm}}$$


$$\alpha = \underline{\hspace{2cm}}$$


$$A_{int} = \underline{\hspace{2cm}}$$

$$\text{Sets } \underline{\hspace{2cm}}$$

U1B ???

Multisim Demo

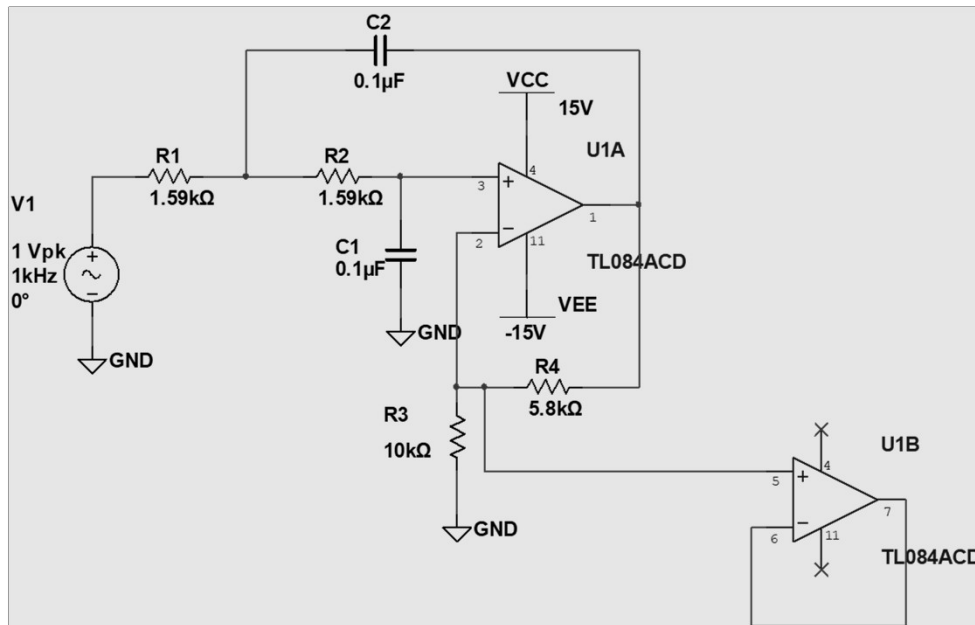

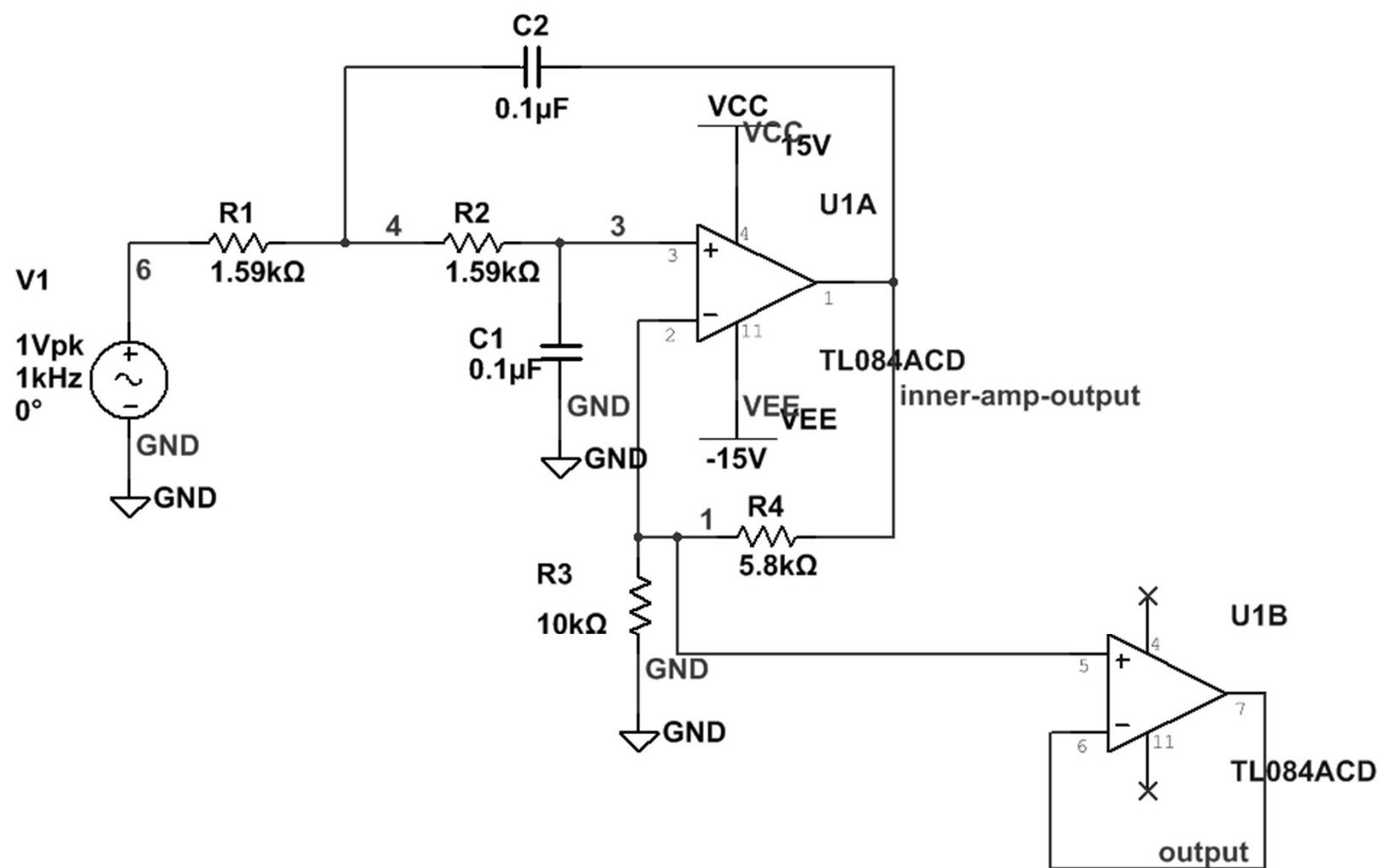

Active Analysis:

Interactive Simulation

DC Operating Point

AC Sweep

Transient

DC Sweep

Single Frequency AC

Parameter Sweep

Noise

Monte Carlo

Fourier

AC Sweep

Frequency parameters

Output

Analysis options

Summary

Start frequency (FSTART):

10

Hz

Stop frequency (FSTOP):

100

kHz

Sweep type:

Decade

Number of points per decade:

1000

Vertical scale:

Decibel

2ndOrderLP AC Sweep

