

Filter Types and Order


- Change ξ changes the response *type*.
 - Bessel, Butterworth, Chebyshev
 - Transfer function, Matlab, Circuit, Multisim
- Low Pass \Rightarrow High Pass
 - Transfer function, Matlab, Circuit, Multisim

Multistages \Rightarrow Higher order \Rightarrow better roll-off

- Coefficient corrections
- Transfer function, Matlab, Circuit, Multisim

Changing the Damping

Filter Type	Damping (α)	Correction (k_{lp})
Bessel	1.732	0.785
Butterworth	1.414	1.000
3dB Chebyshev	0.766	1.390

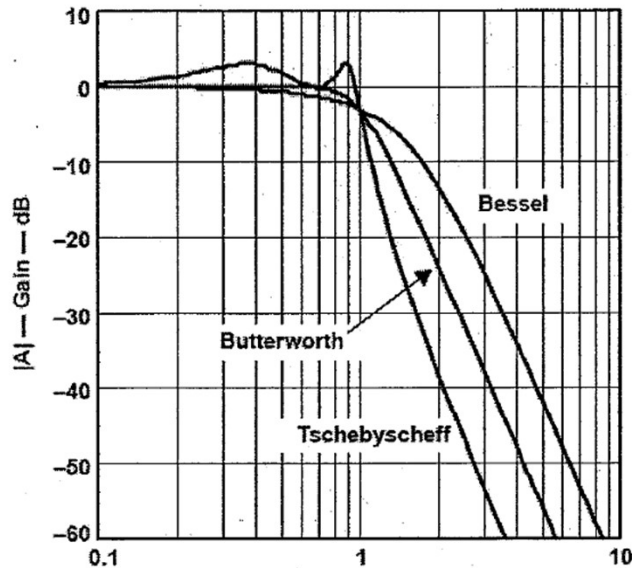

Transfer function

$$G = \frac{A_o \omega_0^2}{s^2 + 2\xi \omega_0 s + \omega_0^2}$$

Bessel Characteristics

Flat in the pass band:

Slower *early* roll-off

$$\xi = 0.866$$

Nearly critically damped

Practically *no* overshoot

Good for filtering digital signals

$$f_{-3dB} = k_{lp} * f_o = 0.785 * f_o \quad \text{early}$$

MATLAB

```
clear
format short G
s=tf('s')
```



```
Ao=1;
wo=1;
zeta=0.866;
```

```
G=Ao*wo^2/(s^2+2*zeta*wo*s+wo^2)
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G,{1e-1,1e1},opts);
```

Bessel - MATLAB

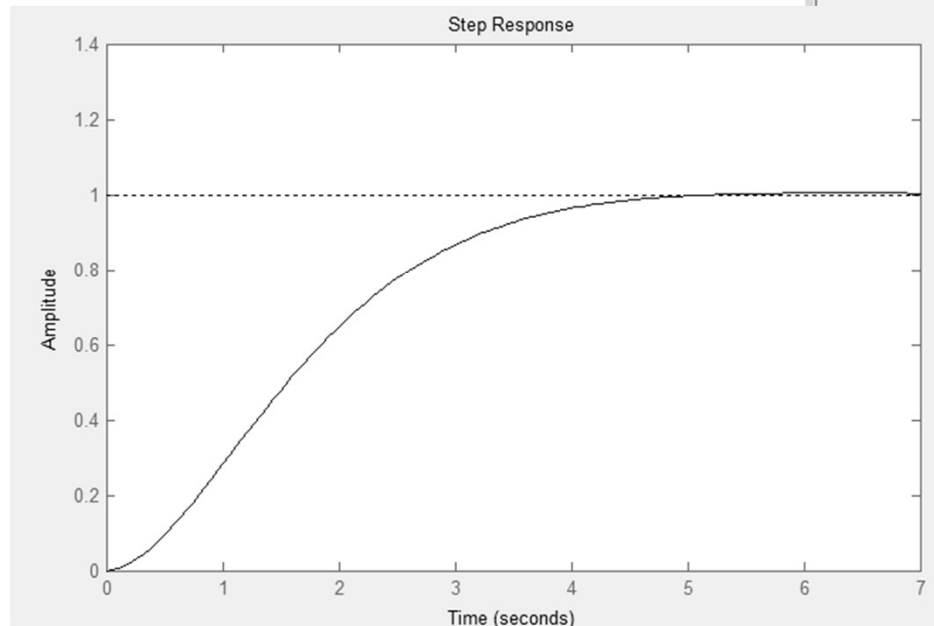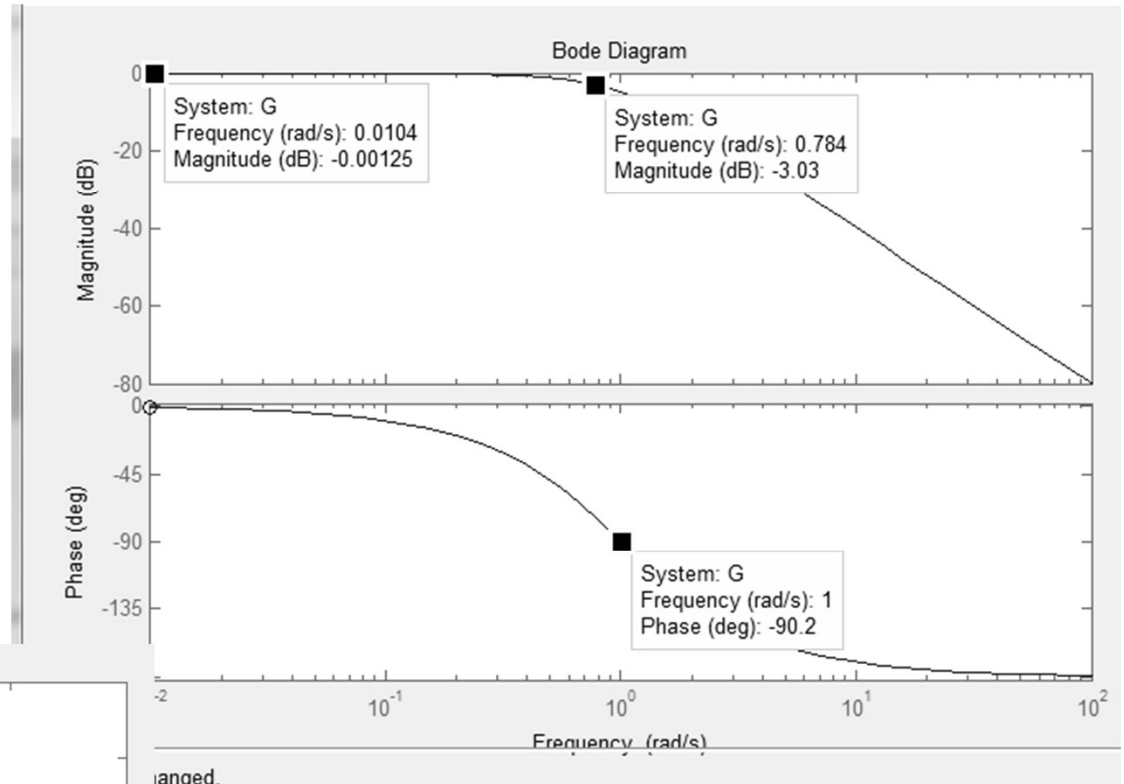

Bessel - Sallen Key Implementation

$$G = \frac{A_o \omega_o^2}{s^2 + 2\xi \omega_o s + \omega_o^2}$$

$$f_o = 1/(2\pi RC)$$

$$\alpha = 2\xi = 2 * 0.866 = 1.732$$

$$= 3 - A_{int}$$


$$A_{int} = 1 + R_f/R_i$$

$$A_{int} = 3 - 1.732$$

$$= 1.268$$


Set damping

Multisim Demo

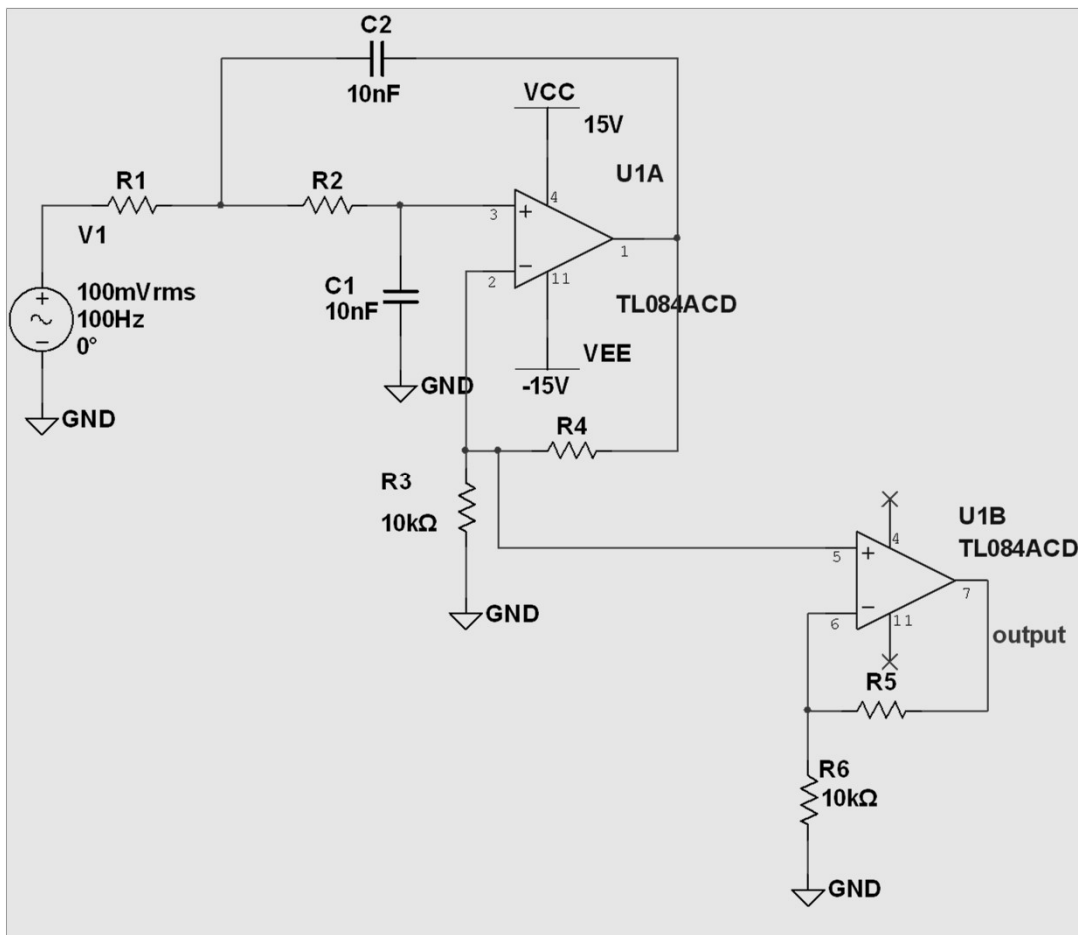


Bessel - Sallen Key Implementation

AC Analysis

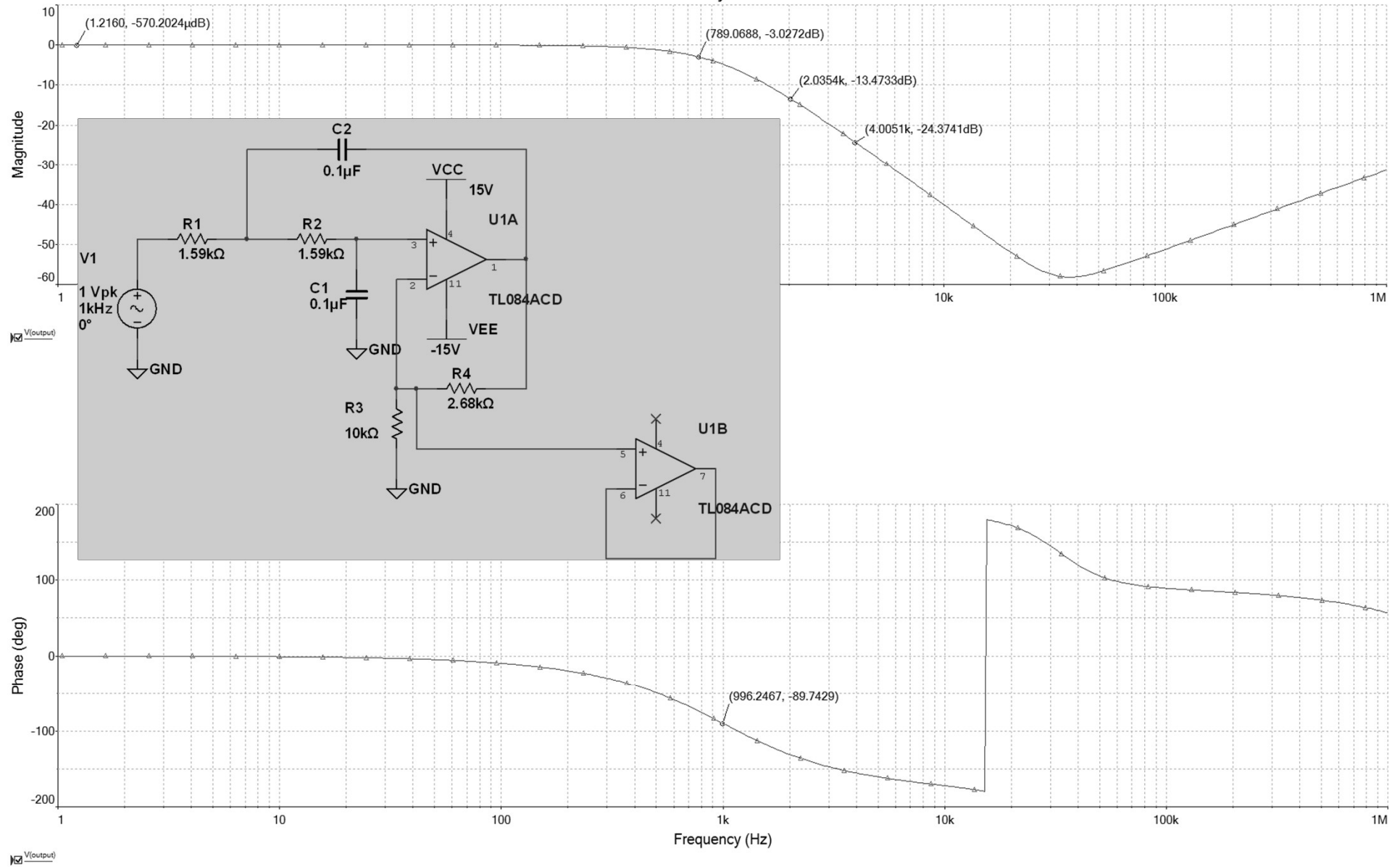


Second Order HP Chebyshev Filters

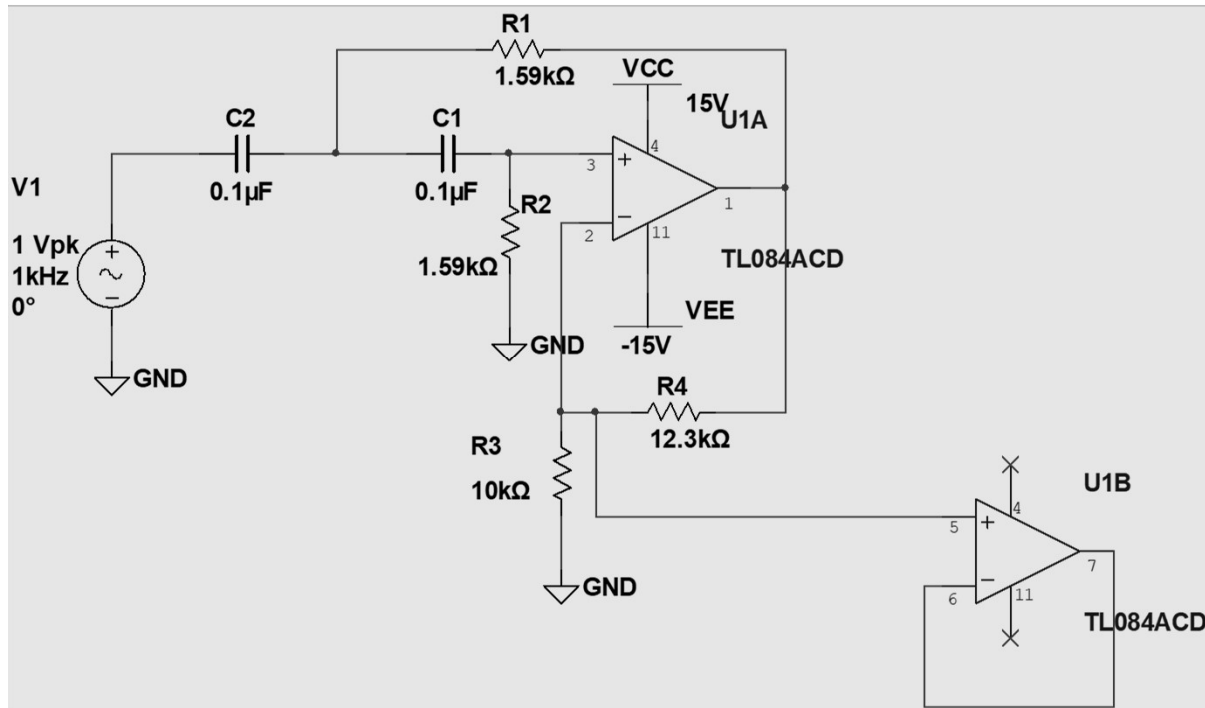

- $$G = \frac{A_o s^2}{s^2 + 2\xi\omega_o s + \omega_o^2}$$

- Multisim

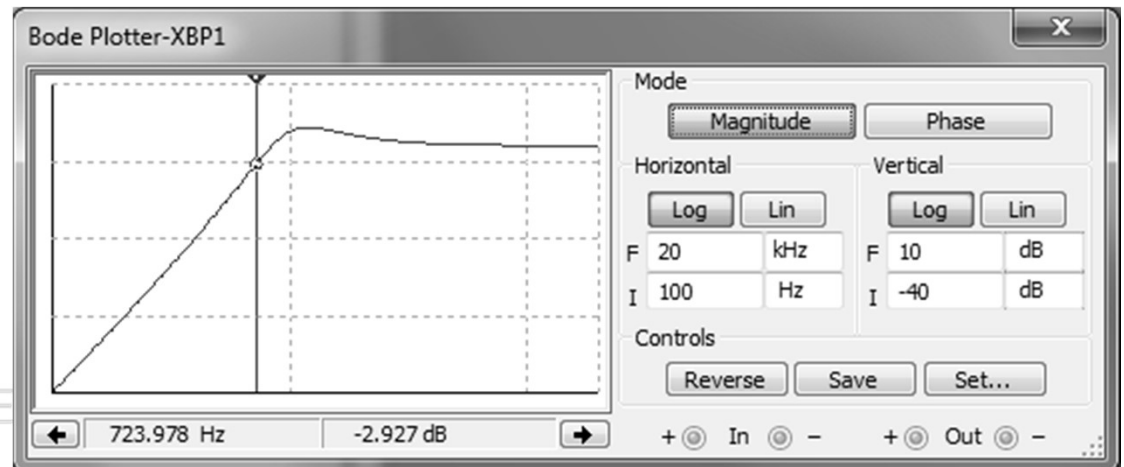

Second Order HP Chebyshev Filters

$$f_{-3\text{dBLP}} = k_{lp} * f_o$$

$$k_{HP} = 1/k_{lp}$$

$$f_{-3\text{dBHP}} = k_{HP} * f_o$$

```
clear
format short G
s=tf('s')
```

```
Ao=1;
fo=1;
wol=2*pi*fo;
zetal=0.383;
|
```


```
G=(Ao*s^2/(s^2+2*zetal*wol*s+wol^2))
```

```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G, {1e-1, 1e2}, opts);
```

$$G = \frac{A_o s^2}{s^2 + 2\xi\omega_o s + \omega_o^2}$$

- MALAB

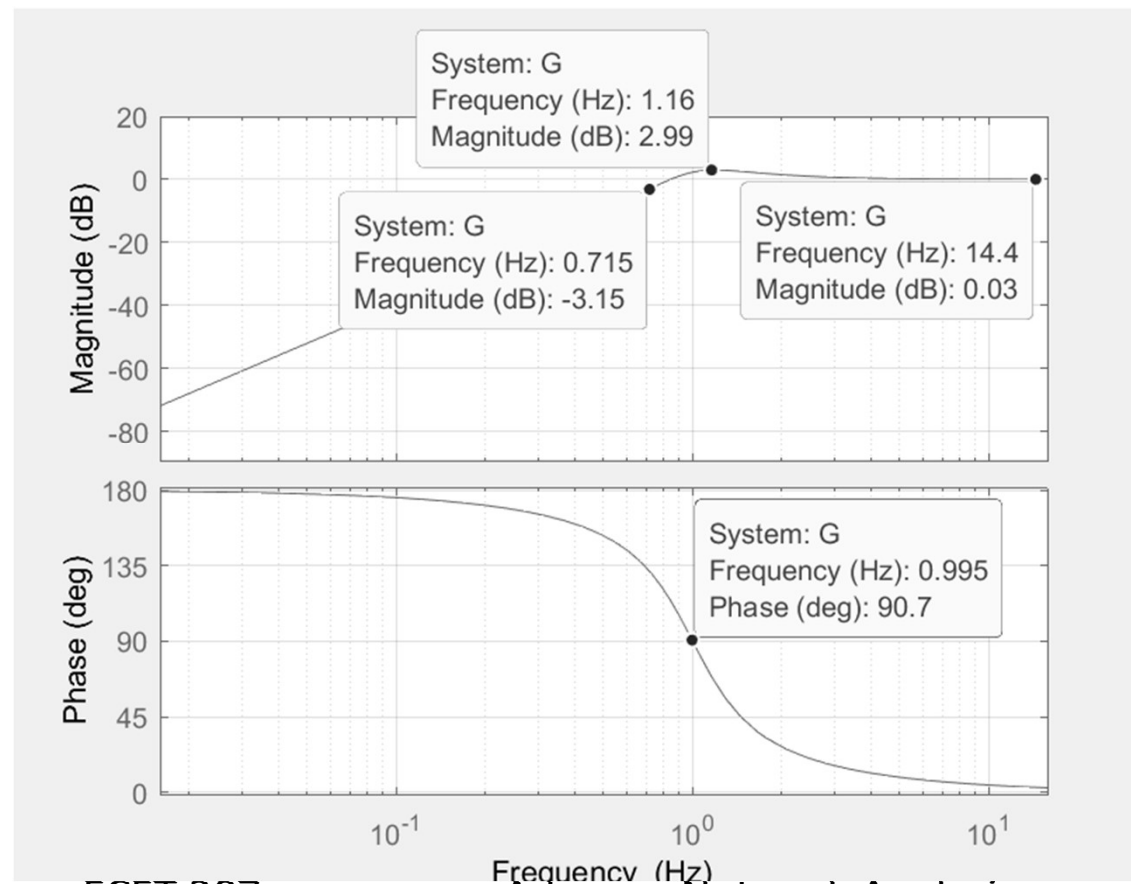

Higher Order

- Adjust each stage RC and A_{int} Corrections $\alpha = 2\xi = 3 - A_{\text{int}}$
 $A_{\text{int}} = 1 + R_f/R_i$ $f_{-3\text{dB}} = k_{\text{LP1}} f_o$ $f_{-3\text{dB}} = k_{\text{LP2}} * f_o$

Filter Order	Section		Bessel	Butterworth	3dB Cheby
2	2	α	1.732	1.414	0.766
		k_{lp}	0.785	1.000	1.390
3	1	α	-	-	-
		k_{lp}	0.753	1.000	3.591
	2	α	1.447	1.000	0.326
		k_{lp}	0.687	1.000	1.172
4	2	α	1.916	1.848	0.929
		k_{lp}	0.696	1.000	2.349
	2	α	1.242	0.765	0.179
		k_{lp}	0.621	1.000	1.095
5	1	α	-	-	-
		k_{lp}	0.665	1.000	5.762
	2	α	1.775	1.618	0.468
		k_{lp}	0.641	1.000	1.670
	2	α	1.091	0.618	0.113
		k_{lp}	0.569	1.000	1.061
6	2	α	1.959	1.932	0.958
		k_{lp}	0.621	1.000	3.412
	2	α	1.636	1.414	0.289
		k_{lp}	0.590	1.000	1.408
	2	α	0.977	0.518	0.078
		k_{lp}	0.523	1.000	1.042

3rd Order LP Bessel

Filter Order	Section		Bessel
2	2	α	1.732
		k_{lp}	0.785
3	1	α	-
		k_{lp}	0.753
	2	α	1.447
		k_{lp}	0.687

$$\omega_o = \frac{1}{\tau}$$

$$f_{3dB} = k_{lp} \times f_o \quad f_o = \frac{f_{3dB}}{k_{LP}}$$

$$G = \frac{1}{\tau_1 s + 1} \times \frac{A_o \omega_{o2}}{s^2 + \alpha_2 \omega_{o2} s + \omega_{o2}^2}$$

```
clear
format short G
s=tf('s')
```

```
AdB=8;
Ao=10^(AdB/20);
f3dB=1e3;
kLP1=0.753;
kLP2=0.687;
a2=1.447;
```

```
fo1=f3dB/kLP1;
wo1=2*pi*fo1;
tau1=1/wo1;
```

```
fo2=f3dB/kLP2;
wo2=2*pi*fo2;
```

```
G=(1/(tau1*s+1))*(Ao*wo2^2/(s^2+a2
*wo2*s+wo2^2))
```


```
opts = bodeoptions('cstprefs');
opts.FreqUnits = 'Hz';
opts.grid = 'on';
opts.PhaseWrapping = 'on';
opts.MagLowerLimMode = 'manual';
opts.MagLowerLim = -90;
```

```
bodeplot(G,{1e2,100e3},opts);
```

$$\omega_o = \frac{1}{\tau}$$

$$f_{3dB} = k_{lp} \times f_o \quad f_o = \frac{f_{3dB}}{k_{LP}}$$
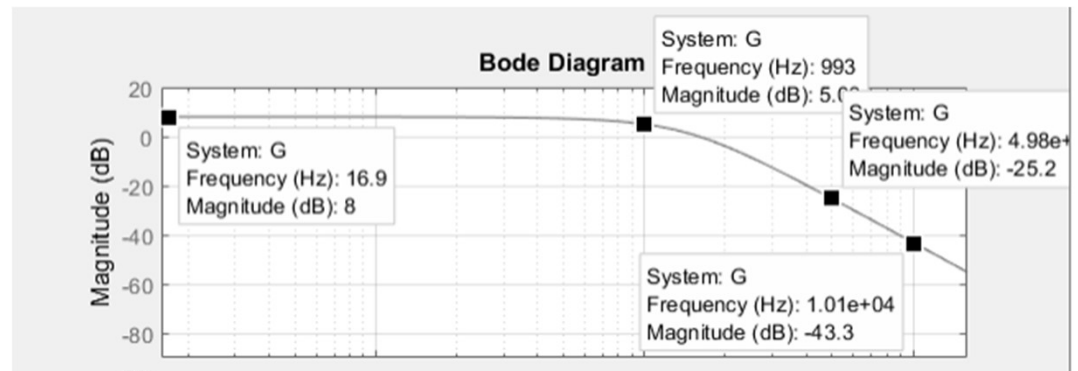
$$G = \frac{1}{\tau_1 s + 1} \times \frac{A_o \omega_{o2}}{s^2 + \alpha_2 \omega_{o2} s + \omega_{o2}^2}$$




Sallen-Key Configuration

$$f_{3dB} = k_{lp} \times f_o = \frac{k_{LP1}}{2\pi R_1 C}$$

$$R_1 = \frac{k_{LP1}}{2\pi f_{3dB} C}$$
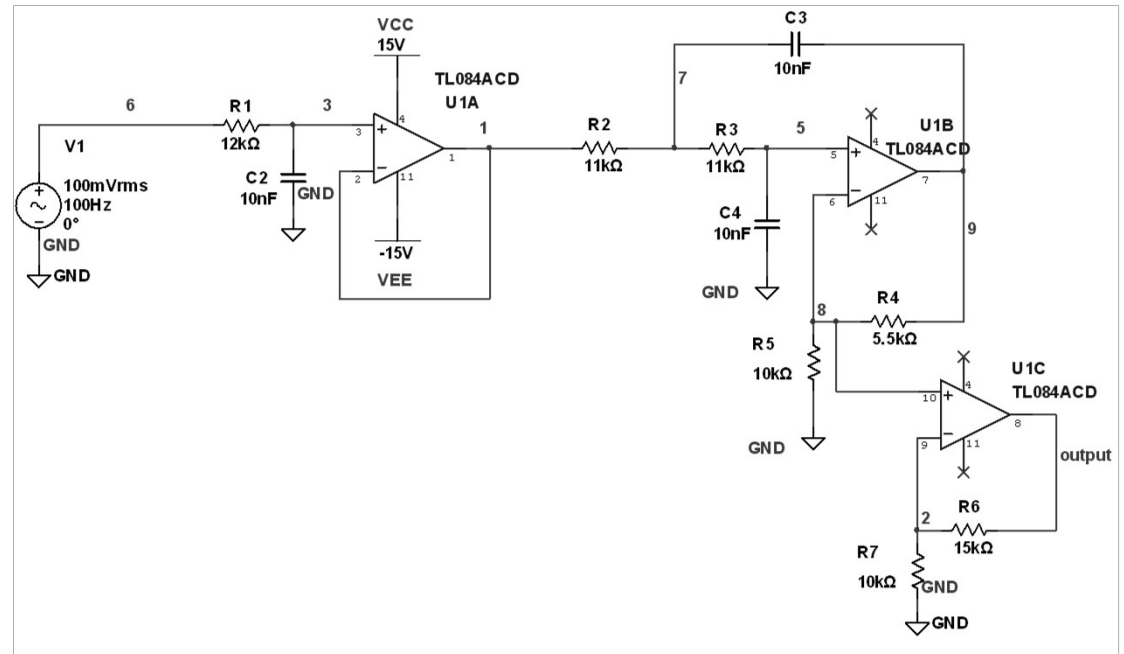
$$R_2 = R_3 = \frac{k_{LP2}}{2\pi f_{3dB} C}$$



$$A_{int} = 3 - \alpha = 3 - 1.447 = 1.553$$

$$A_o = 2.5 = 1 + \frac{R_6}{7}$$

$$A_{int} = 1.553 = 1 + \frac{R_4}{R_5}$$

$$R_7 = 10 \text{ k}\Omega \quad R_6 = 15 \text{ k}\Omega$$

$$R_4 = 10 \text{ k}\Omega \quad R_5 = 5.5 \text{ k}\Omega$$

