
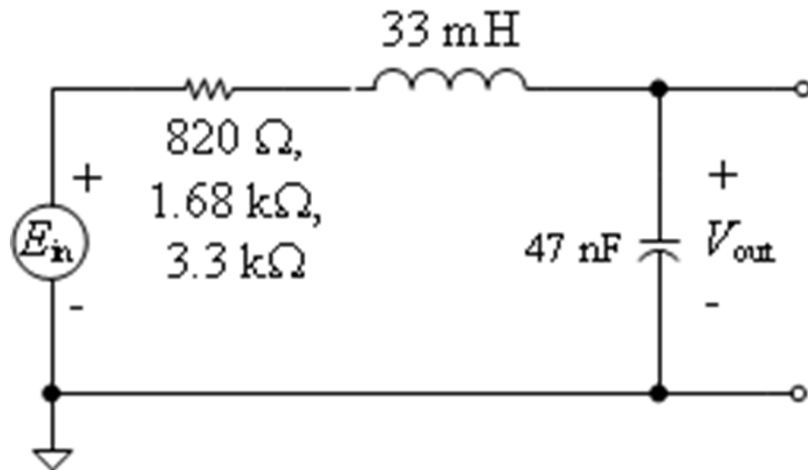


Laplace Second Order – Series RLC

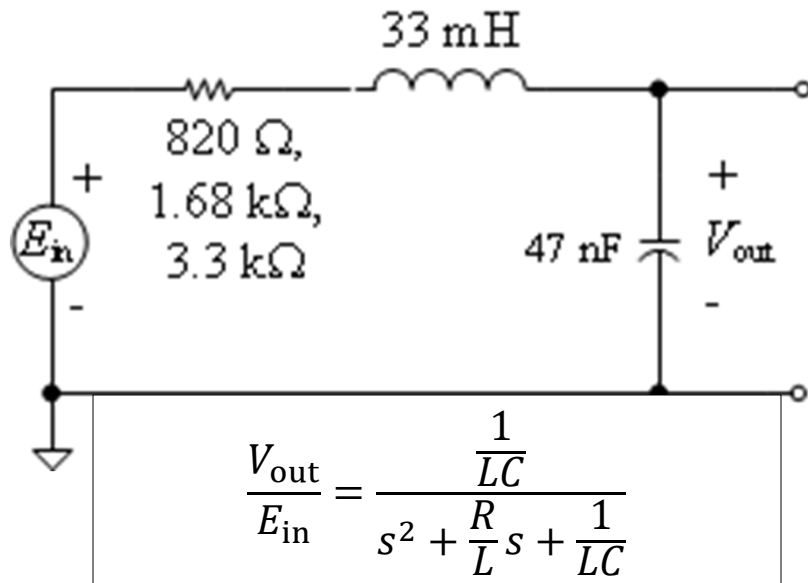

1. Add the Laplace impedances.
2. Find the transfer function.

Laplace Second Order – Series RLC



Real
Overdamped

Equal
Critically damped

Complex
Under damped

Quadratic equation roots


$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$Ax^2 + Bx + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$A = 1 \quad B = 2\zeta\omega_n \quad C = \omega_n^2$$

Laplace Second Order – Series RLC

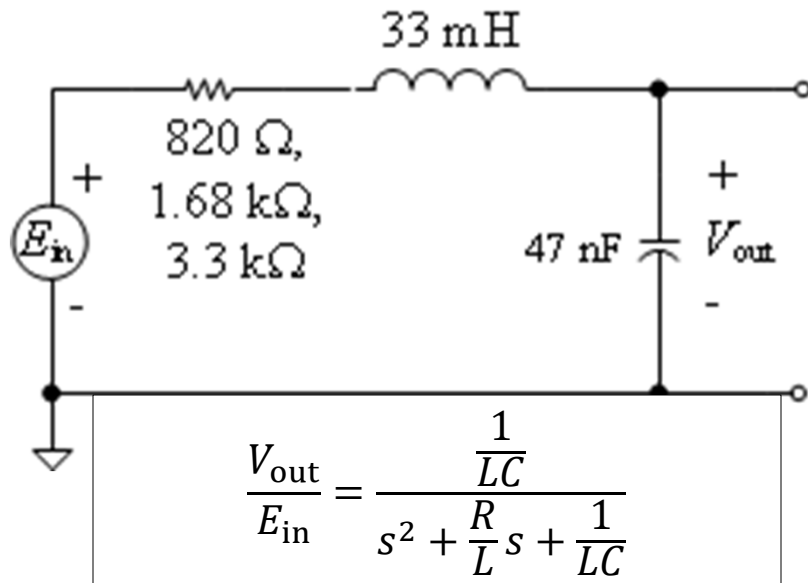

Real
Overdamped

Equal
Critically damped

Complex
Under damped

Quadratic equation roots


$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$Ax^2 + Bx + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$A = 1 \quad B = 2\zeta\omega_n \quad C = \omega_n^2$$

Which R => which damping?

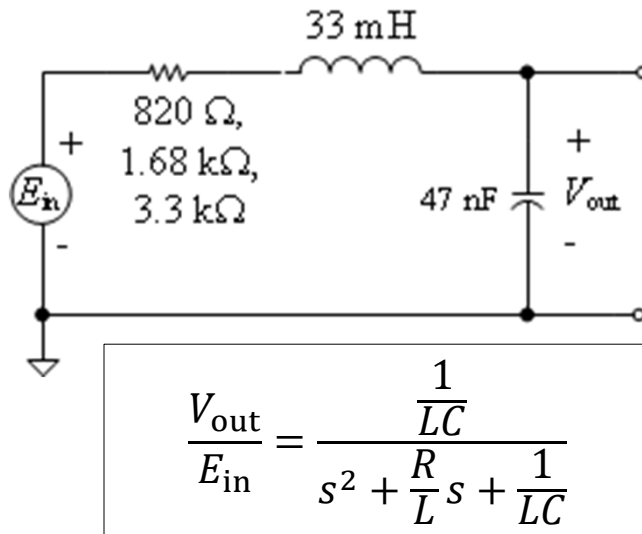

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$Ax^2 + Bx + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

820 Ω

_____ damped


1.68 kΩ

_____ damped

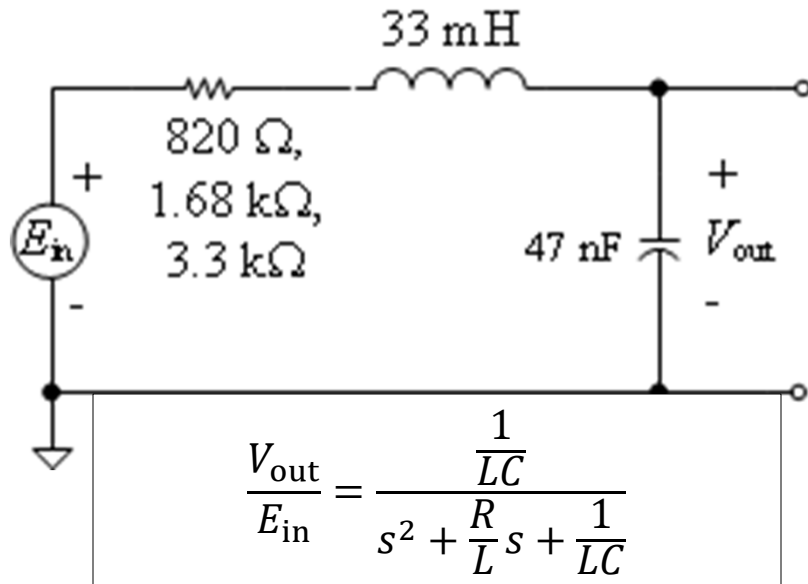3.3 kΩ

_____ damped


Write the time domain equation for $V_{\text{out}}(t)$
Overdamped



$$\frac{A}{s(s+a)(s+b)} \rightarrow \frac{A}{ab} \left(1 + \frac{ae^{-bt} - be^{-at}}{b-a} \right)$$

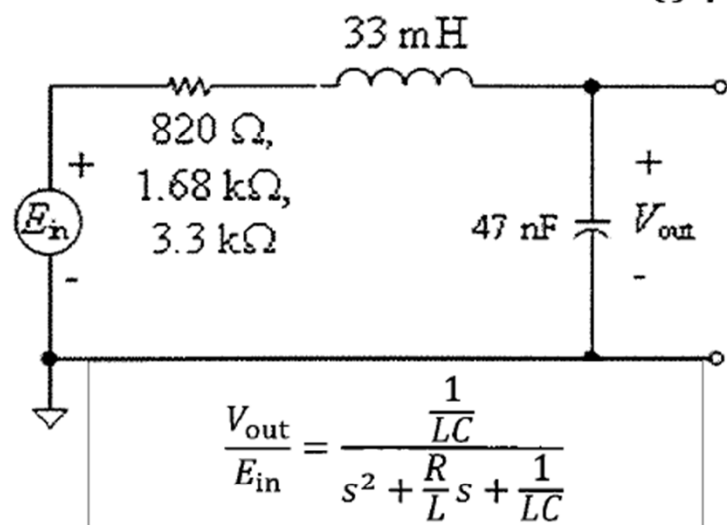(5)

Write the time domain equation for $V_{out}(t)$
Overdamped



$$= \frac{1}{s^2 + \frac{3.3k\Omega}{33mH}s + \frac{1}{33mH * 47nF}}$$

$$= \frac{645m}{s^2 + 100k s + 645m}$$

$$A=1 \quad B=100k \quad C=645m$$

$$\frac{A}{s(s+a)(s+b)} \rightarrow \frac{A}{ab} \left(1 + \frac{ae^{-bt} - be^{-at}}{b-a} \right)$$

$$\chi = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$\chi = \frac{-100k \pm \sqrt{(100k)^2 - 4 * 645m}}{2}$$

$$\chi = -50k \pm 43k = -7k, -93k$$


$$(s + 7k)(s + 93k)$$

$$V_{out} = \frac{1V}{s} * \frac{645m}{(s+7k)(s+93k)}$$

$$V_{out} = \frac{645m}{7k * 93k} \left(1 + \frac{7ke^{-93kt} - 93ke^{-7kt}}{93k - 7k} \right)$$

$$= 0.991 \left(1 + 0.081e^{-t/11\mu s} - 1.08e^{-t/143\mu s} \right)$$

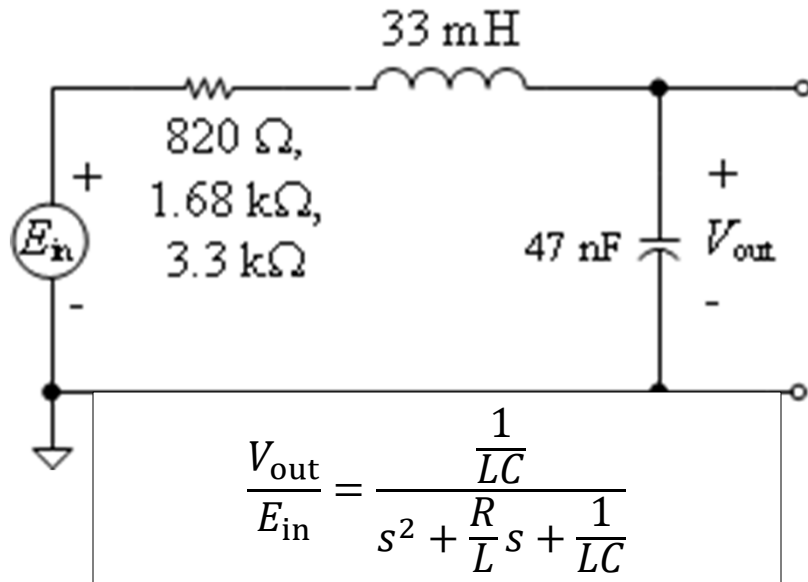
Write the time domain equation for $V_{\text{out}}(t)$
Critically damped



$$\frac{A}{s(s + \alpha)^2} \rightarrow \frac{A}{a^2} [1 - (1 + at)e^{-at}]$$

6

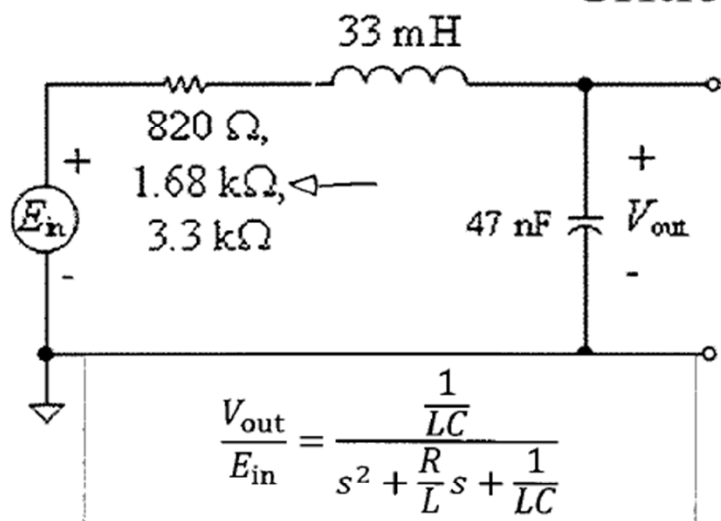Write the time domain equation for $V_{out}(t)$
Critically damped



$$\frac{V_{out}}{E_{in}} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$= \frac{645 \text{ M}}{s^2 + 50.9 \text{ k } s + 645 \text{ M}}$$

$A = 1 \quad B = 50.9 \text{ k} \quad C = 645 \text{ M}$

$$\frac{A}{s(s + \alpha)^2} \rightarrow \frac{A}{a^2} [1 - (1 + at)e^{-at}]$$

$$\chi = \frac{-B \pm \sqrt{B^2 - 4AC}}{2}$$

$$\chi = \frac{-50.9 \text{ k} \pm \sqrt{(50.9 \text{ k})^2 - 4(645 \text{ M})}}{2}$$


$$\chi \approx -25.5 \text{ k} \pm 0 \leftarrow \text{almost with standard components}$$

$$V_{out} = \frac{1}{A} \times \frac{645 \text{ M}}{(s + 25.5 \text{ k})^2}$$

$$V = \frac{645 \text{ M}}{(25.5 \text{ k})^2} \left[1 - (1 + 25.5 \text{ k } t) e^{-25.5 \text{ k } t} \right]$$

$$V = 0.992 \left[1 - (1 + 25.5 \text{ k } t) e^{-t/39 \mu\text{s}} \right]$$

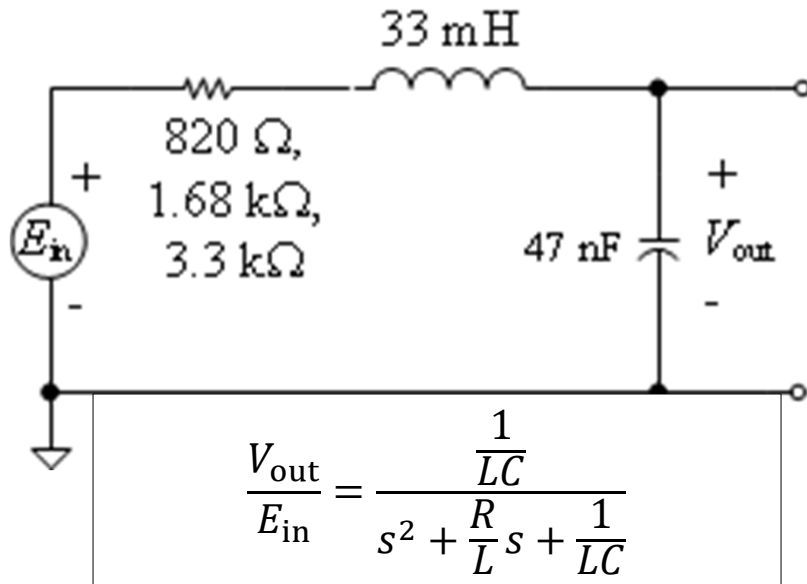Write the time domain equation for $V_{\text{out}}(t)$
Underdamped




22.

$$\frac{A\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$$

$$A \left[1 + \frac{e^{-\zeta\omega_n t}}{\sqrt{1-\zeta^2}} \sin(\omega_n \sqrt{1-\zeta^2} t - \psi) \right]$$

where $\psi = \tan^{-1} \frac{\sqrt{1-\zeta^2}}{-\zeta}$ ($0 < \psi < \pi$)

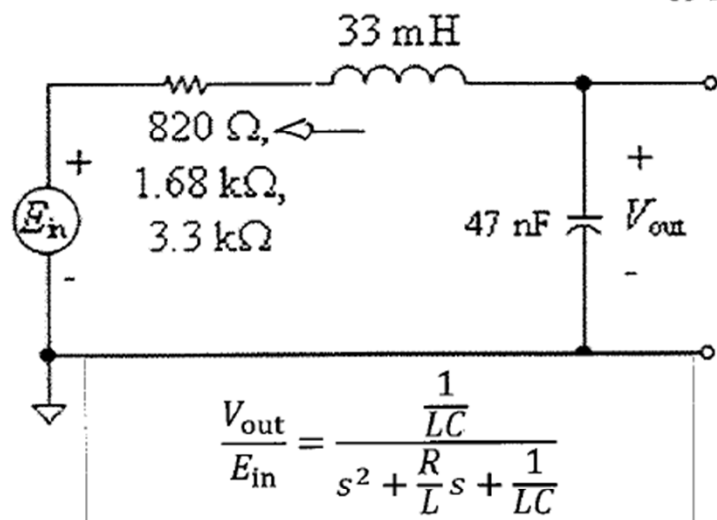Write the time domain equation for $V_{out}(t)$
Underdamped



$$\frac{V_{out}}{E_{in}} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$= \frac{645M}{s^2 + 24.8k s + 645M}$$

$$\omega_n^2 = 645M$$

$$\omega_n = 25.4 K$$

$$A\omega_n^2 = 645M$$

$$A = 1$$

$$2\zeta\omega_n = 24.8k$$

$$\zeta = \frac{24.8k}{2 \times 25.4k}$$

$$\zeta = 0.49$$

$$22. \quad \frac{A\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$$

$$A \left[1 + \frac{e^{-\zeta\omega_n t}}{\sqrt{1-\zeta^2}} \sin(\omega_n \sqrt{1-\zeta^2} t - \psi) \right]$$

where $\psi = \tan^{-1} \frac{\sqrt{1-\zeta^2}}{-\zeta}$ ($0 < \psi < \pi$)

$$v = 1 \left[1 + \frac{e^{-0.49 \times 25.4k t}}{\sqrt{1-0.49^2}} \sin(25.4k \sqrt{1-0.49^2} t - \psi) \right]$$

$$= 1 + 1.147 e^{-12.4k t} \sin(22.1k t - \psi)$$

$$= 1 + 1.147 e^{-t/81\mu sec} \sin(2\pi \times 3.5k Hz t - \psi)$$


eventually $v_{out} = E_{in}$

eventually dies out ($\omega \sim 40\mu sec$)

oscillation with
decaying amplitude
with 286 μsec period







MATLAB calculated responses
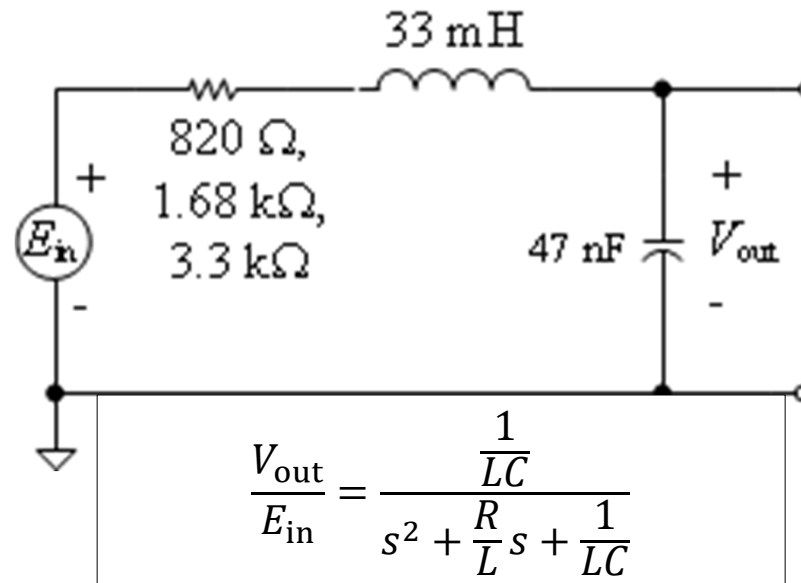
$$\frac{V_{out}}{E_{in}} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$









```

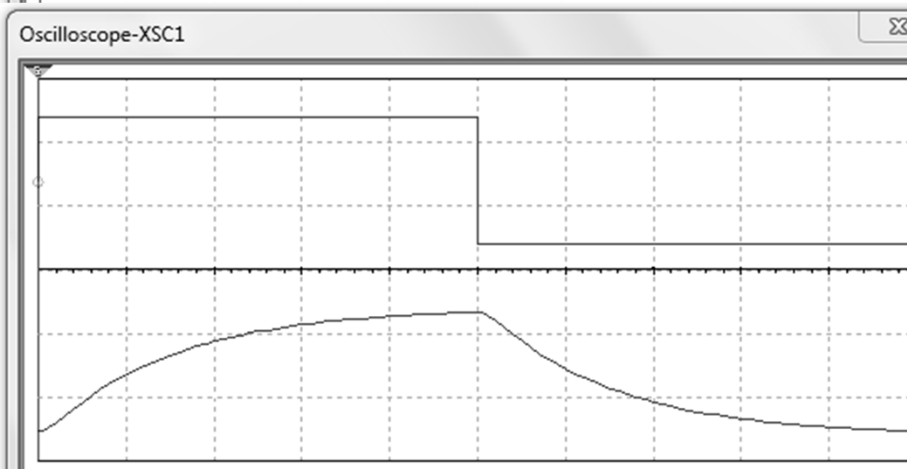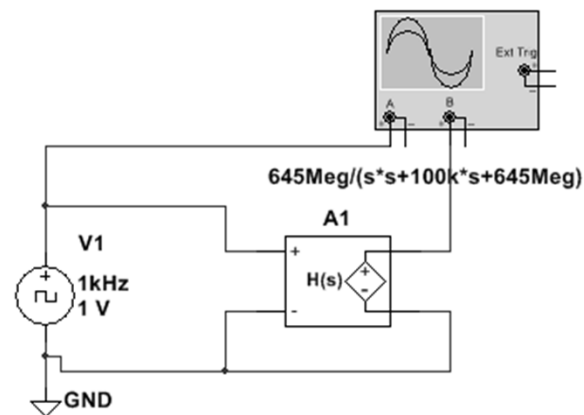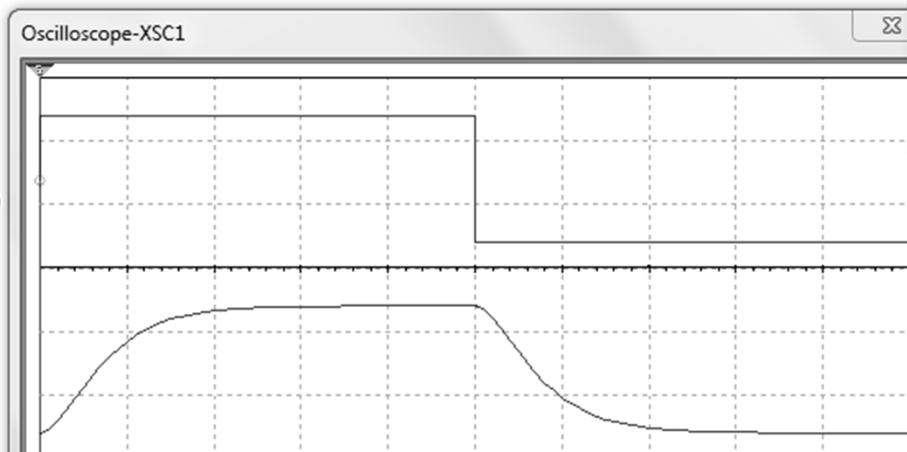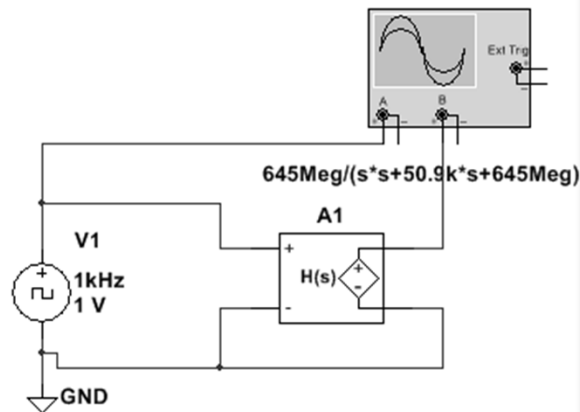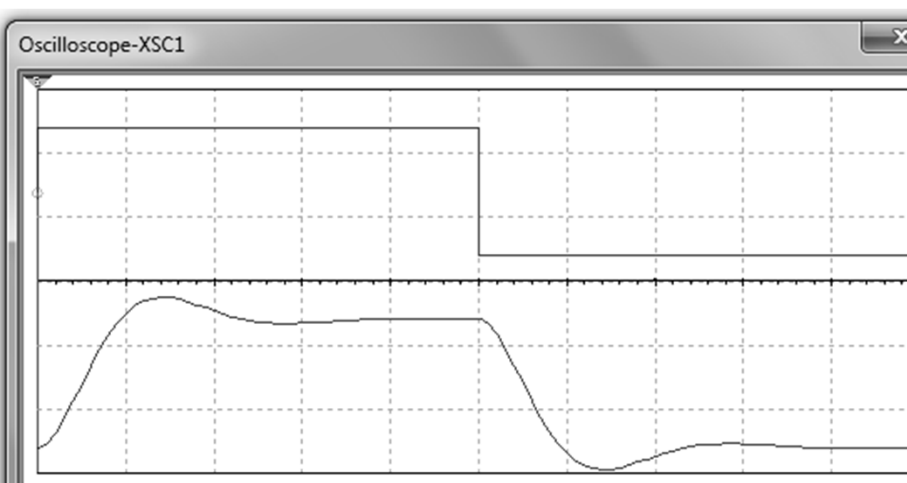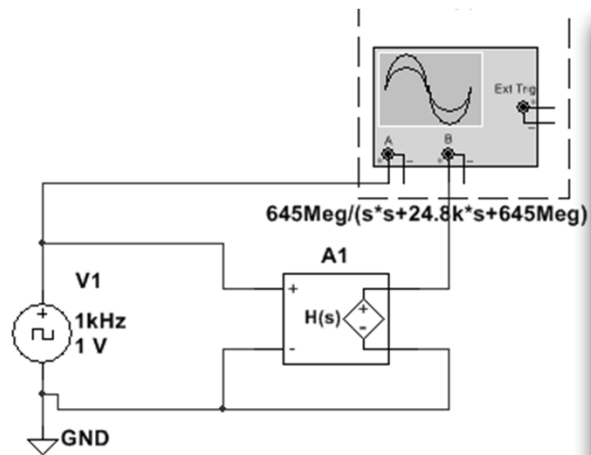clc
clear
s=tf('s')
R1=3.3e3;
R2=1.68e3;
R3=820;
L=33e-3;
C=47e-9;
G_over=(1/L*C)/(s^2+(R1/L)*s+(1/(L*C)))
G_critical=(1/L*C)/(s^2+(R2/L)*s+(1/(L*C)))
G_under=(1/L*C)/(s^2+(R3/L)*s+(1/(L*C)))
ltiview(G_over,G_critical,G_under)
    
```



Processing

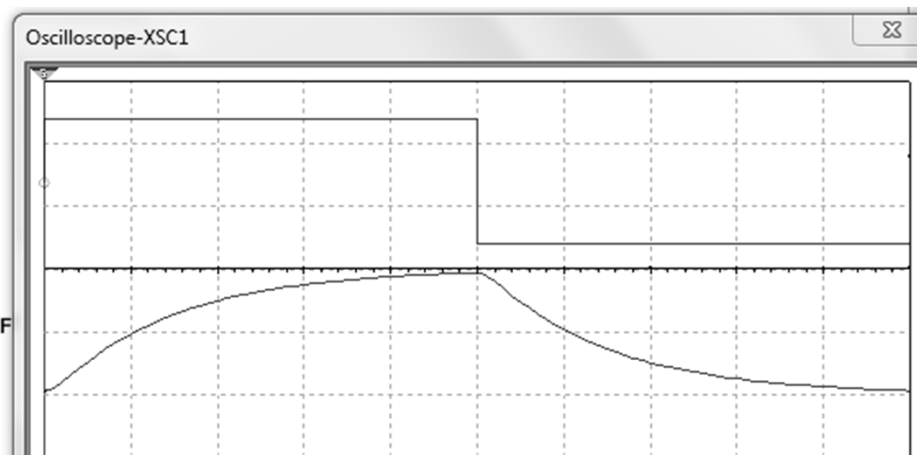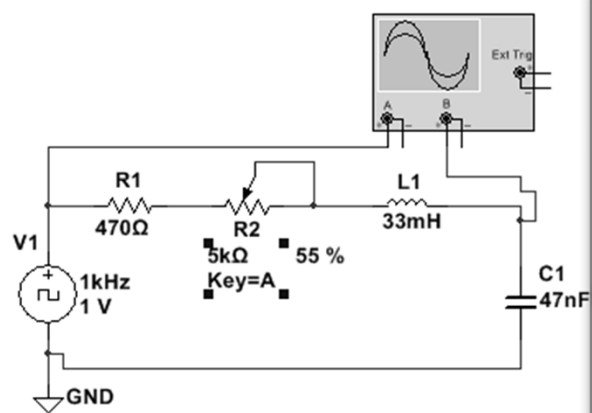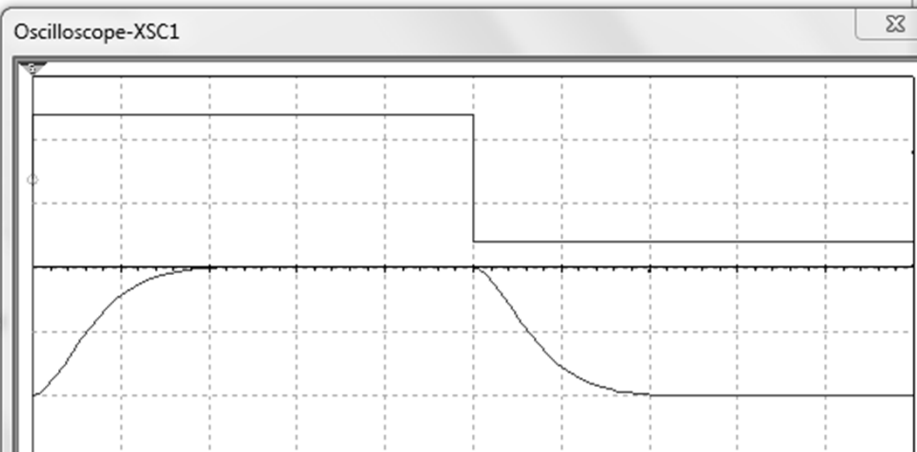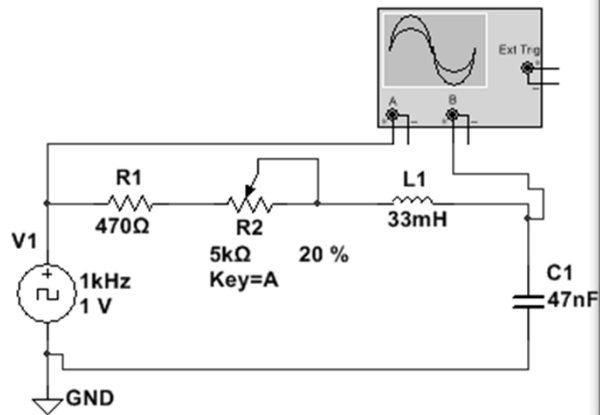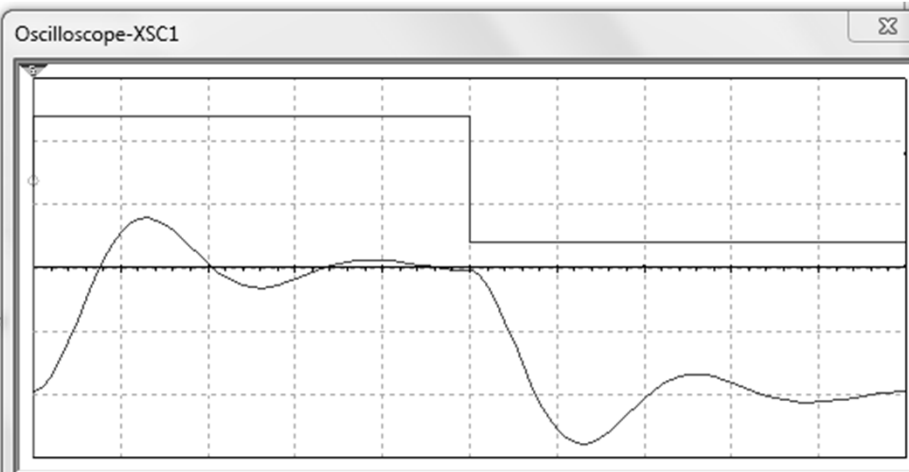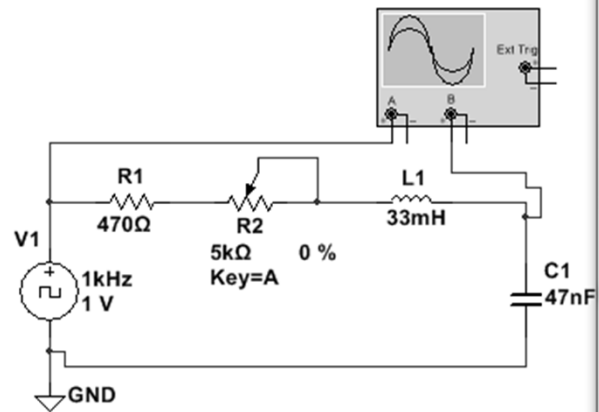

F

rocessing