

**Figure 3-10** Capacitance, charge, electrostatic field, and voltage

## 3.2 Capacitance in the Time Domain

Capacitance exists anytime there are two parallel conductors separated by an insulator. Often, this is an intentional component, two plates separated by a film insulator and packaged with an external lead connecting to each plate. This is shown in Figure 3-10. But, any two associated conductors form a capacitance, such as the two traces on the top and bottom of a printed circuit board.

Each electron that arrives at the lower plate forces an electron to leave the upper plate, leaving an equal positive charge there. This charge,  $Q$ , creates an electrostatic field, shown by the arrows between the plates, storing energy and producing a resulting potential difference,  $V$ . How much charge and energy that can be stored depends on the size of the plates, how close together they are, and the properties of the insulation. These define the *capacitance*.

$$C = \frac{Q}{V}$$

The more charge (and energy) a capacitor can hold (per volt), the larger its capacitance, (the more water a bucket can hold, the larger it must be).

$$V = \frac{Q}{C}$$

Taking the time derivative of both sides gives

$$\frac{dV}{dt} = \frac{1}{C} \frac{dQ}{dt}$$

But, current is defined as

$$i = \frac{dQ}{dt}$$

$$\frac{dV}{dt} = \frac{1}{C} i$$


$$i = C \frac{dV}{dt}$$

**“Ohm’s Law”  
for capacitors**

Current is the flow of charge onto and off of the capacitor as it charges and discharges. So, even though a charged capacitor looks like an open (to DC), *as* the capacitor charges or discharges, current flows onto and off of it. There is an insulator between the two plates, but *transient* current still flows (onto and off of => through). The more rapidly the voltage across the capacitor *changes* the more quickly charge flows on and off of the capacitor and the higher the resulting current.

### Example 3-1

The voltage waveform shown in Figure 3-11 is impressed across a 5  $\mu\text{F}$  capacitor. *Accurately* draw the current flowing into (and out of) the capacitor.

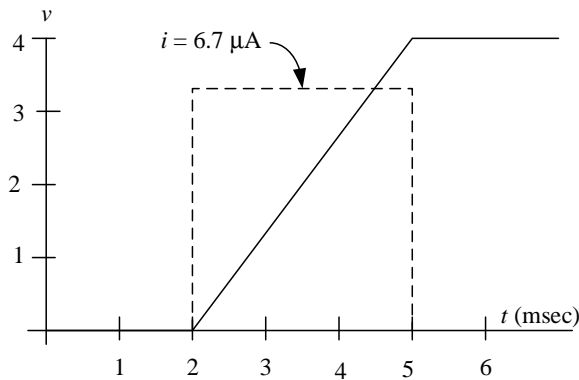

**Figure 3-11** Ramp voltage resulting in a pulse of current

### Solution

$$i = C \frac{dV}{dt}$$

From  $t = 0$  to 2 msec, the voltage does not *change*.

$$i_{0 \text{ to } 2 \text{ msec}} = 0 \text{ A}$$

From  $t = 2$  msec to 5 msec, the voltage is a ramp, changing 4 V.

$$i = C \frac{dV}{dt} = 5 \mu\text{F} \frac{4 \text{ V}}{5 \text{ sec} - 2 \text{ sec}} = 6.7 \mu\text{A}$$

Since the voltage changes at a steady rate, the current is a constant  $5\text{ }\mu\text{A}$ .

For  $t > 6\text{ msec}$ , the voltage does not *change*.

$$i_{t > 6\text{ msec}} = 0\text{ A}$$


### Example 3-2

The voltage across the  $5\text{ }\mu\text{F}$  capacitor is changed to an exponential rise

$$v = 4\text{ V}(1 - e^{-10t})$$

Calculate and plot the equation for the current.

### Solution

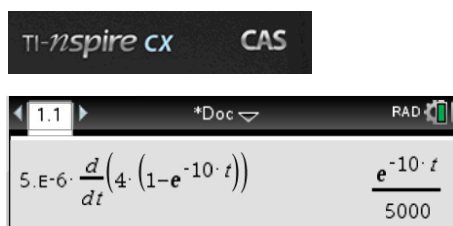

(a) TI-Nspire derivative

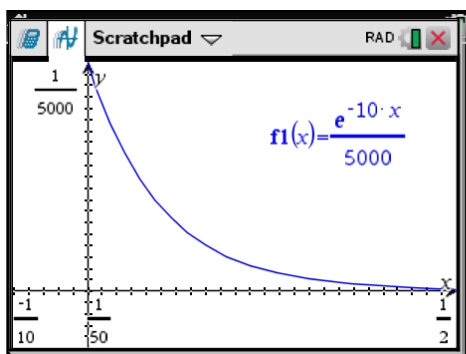


Figure 3-12 (b) Plot of current for Example 3-2

$$i = C \frac{dV}{dt} = 5\text{ }\mu\text{F} \frac{d}{dt} (4\text{ V}(1 - e^{-10t}))$$

$$\frac{d}{dt} \left[ A \left( 1 - e^{-\frac{t}{\tau}} \right) \right] = \frac{A}{\tau} e^{-\frac{t}{\tau}}$$

$$A = 4\text{ V}$$

$$\tau = 0.1\text{ sec}$$

$$i = 5\text{ }\mu\text{F} \frac{4\text{ V}}{0.1\text{ sec}} e^{-10t}$$

$$i = 200\text{ }\mu\text{A} e^{-10t}$$

In Figure 3-12(a) the TI-Nspire completed the derivative. The answer was then copied, the calculator mode changed to Graph, and then the function pasted. The graph expects the horizontal axis to be  $x$ , not  $t$ , so that variable was changed. Finally the scaling was adjusted to show the full plot, *and* a little of the 0,0 origin.

Driving an exponentially increasing voltage across a capacitor produces a *spike* of current that falls to 0 when the voltage becomes constant at its maximum value.

Given the voltage, the current can be calculated.

$$i = C \frac{dV}{dt}$$

But, if current is driven into the capacitor, how is the voltage calculated?

$$i dt = C dv$$

$$dv = \frac{1}{C} i dt$$

$$v = \frac{1}{C} \int i dt$$

To evaluate this integral requires limits.

$$v = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \left( \int_{-\infty}^0 i dt + \int_0^t i dt \right)$$

Integrating from the beginning of time ( $t = -\infty$ ) could be a problem. So, that part of the integral is separated. Whatever has happened before the beginning of the calculation ( $t = 0$ ) is just the initial charge on the capacitor,  $V_o$  however it got there.

$$v = \frac{1}{C} \int_0^t i dt + V_o$$

Given  $i_{\text{cap}}$ , find  $v_{\text{cap}}$ .

---

### Example 3-3

Given an exponential *spike* of current into a 5  $\mu\text{F}$  capacitor with:

$$i_{\text{max}} = 1.5 \text{ A}$$

$$\tau = 100 \mu\text{sec}$$

$$V_o = -10 \text{ V}$$

determine the equation for the voltage across the capacitor and plot it.

**Solution**

$$i = Ae^{-\frac{t}{\tau}} = 1.5 \text{ A } e^{-\frac{t}{100 \mu\text{sec}}}$$


$$v = \frac{1}{C} \int_0^t i \, dt + V_o = \frac{1}{5 \mu\text{F}} \int_0^t 1.5 \text{ A } e^{-\frac{t}{100 \mu\text{sec}}} dt - 10 \text{ V}$$

From the preceding section:

$$\int_0^t \left( Ae^{-\frac{t}{\tau}} \right) dt = A\tau \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$v = \frac{1}{5 \mu\text{F}} \int_0^t 1.5 \text{ A } e^{-\frac{t}{100 \mu\text{sec}}} dt - 10 \text{ V} = \frac{1.5 \text{ A}}{5 \mu\text{F}} \times 100 \mu\text{sec} \left( 1 - e^{-\frac{t}{100 \mu\text{sec}}} \right) - 10 \text{ V}$$

$$v = 30 \text{ V} \left( 1 - e^{-\frac{t}{100 \mu\text{sec}}} \right) - 10 \text{ V}$$

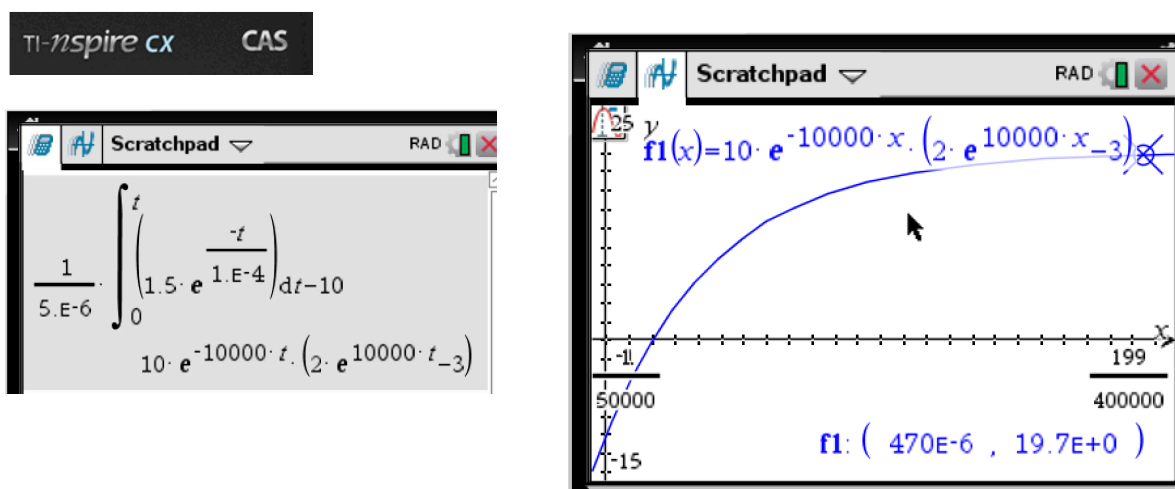

**Figure 3-13** Calculator integration and plot

Although the calculator's answer to the integration seems different than the manual solution, a little algebra will show that the two results agree. The plot starts at  $V_o = -10 \text{ V}$ , and in 5 time constants ( $500 \mu\text{sec}$ ) rises exponentially to  $20 \text{ V}$ , a total rise of  $30 \text{ V}$ .