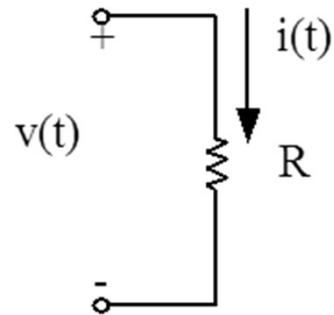



Resistor's Laplace Impedance



$$v_R(t) =$$

$$Z_R(s) =$$

Capacitor's Laplace Impedance

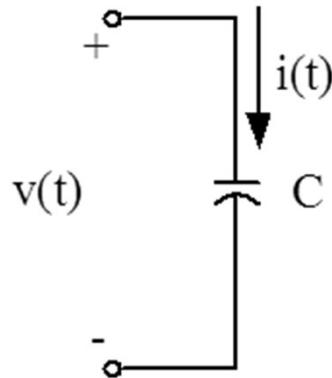


$$i_C(t) =$$

$$Z_C(s) =$$

TABLE A-1 (continued)


No.	$F(s)$	
7.	$\frac{As}{s^2 + \omega^2}$	$A \cos \omega t$
8.	$aF(s)$	$af(t)$
9.	$\frac{n!}{s^{n+1}}$	t^n
10.	$sF(s) - f(0)$	$\frac{df(t)}{dt}$
11.	$s^2F(s) - sf(0) - \frac{df(0)}{dt}$	$\frac{d^2f(t)}{dt^2}$
12.	$\frac{F(s)}{s}$	$\int f(t) dt$
13a.	$\frac{A}{\tau s + 1}$	$\frac{A}{\tau} e^{-\nu t}$
13b.	$\frac{A}{s + a}$	Ae^{-at}
14a.	$\frac{A}{s - \sigma}$	$\frac{A}{\tau} e^{-(\nu - \sigma)t}$

RC Circuit – Transfer Function

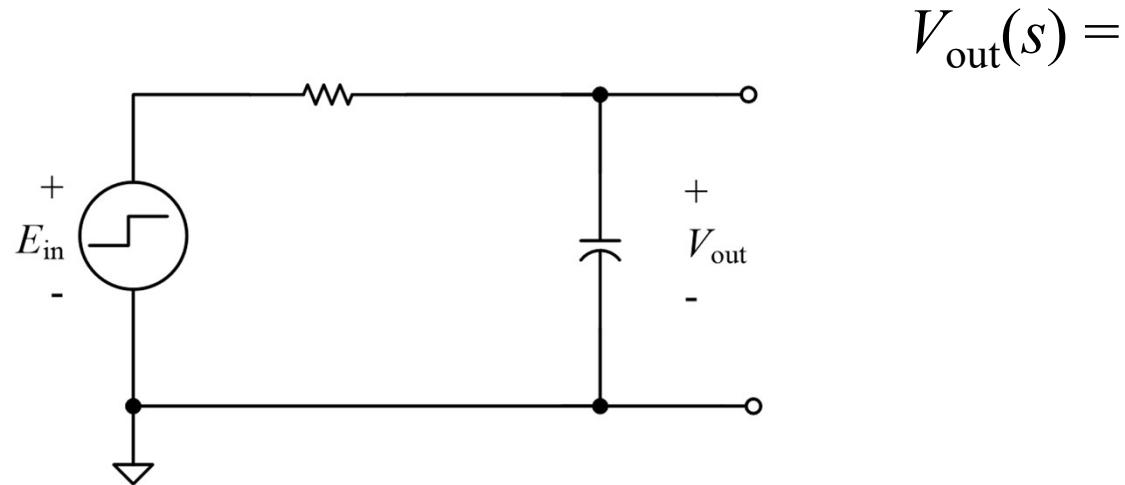

$$\frac{V_{\text{out}}(s)}{E_{\text{in}}(s)} =$$

RC Circuit – Response to 5 V step

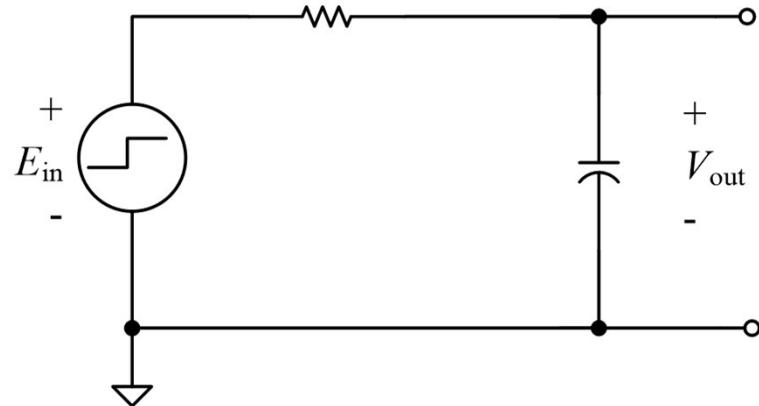


$$\frac{V_{out}(s)}{E_{in}(s)} =$$

$$V_{out} =$$

$$E_{in \text{ step}} =$$

TABLE A-1 LAPLACE TRANSFORMS

No.	$F(s)$	$f(t)$	Comments
1.	1	$\delta(t)$	Unit impulse
2.	$\frac{A}{s}$	$A(t) = \begin{cases} 0 & t < 0 \\ A & t \geq 0 \end{cases}$	Step
3.	$\frac{1}{s}$	$U(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$	Unit step
4.	$\frac{A}{s^2}$	At	Ramp
5.	$\frac{2A}{s^3}$	At^2	Parabola
6.	$\frac{A\omega}{s^2 + \omega^2}$	$A \sin \omega t$	Sine

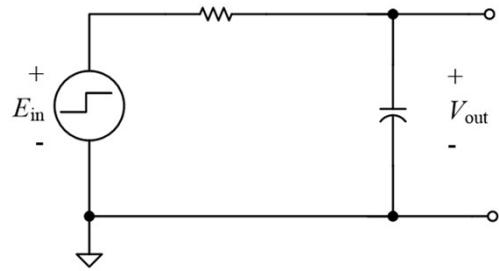

RC Circuit – Response to 5 V step

$$V_{\text{out}}(s) =$$


TABLE A-1 (continued)

No.	$F(s)$	$f(t)$	Comments
7.	$\frac{As}{s^2 + \omega^2}$	$A \cos \omega t$	Cosine
8.	$aF(s)$	$af(t)$	
9.	$\frac{n!}{s^{n+1}}$	t^n	
10.	$sF(s) - f(0)$	$\frac{df(t)}{dt}$	
11.	$s^2F(s) - sf(0) - \frac{df(0)}{dt}$	$\frac{d^2f(t)}{dt^2}$	
12.	$\frac{F(s)}{s}$	$\int f(t) dt$	
13a.	$\frac{A}{ts + 1}$	$\frac{A}{\tau} e^{-\nu t}$	Free response of first-order system
13b.	$\frac{A}{s + a}$	Ae^{-at}	
14a.	$\frac{A}{(\tau_1 s + 1)(\tau_2 s + 1)}$	$\frac{A}{\tau_1 - \tau_2} (e^{-\nu \tau_1} - e^{-\nu \tau_2})$	Free response of second-order system ($\zeta > 1$)
14b.	$\frac{A}{(s + a)(s + b)}$	$\frac{A}{b - a} (e^{-\nu t} - e^{-bt})$	
15a.	$\frac{A}{(\tau s + 1)^2}$	$\frac{At}{\tau^2} e^{-\nu t}$	Free response of second-order system ($\zeta = 1$)
15b.	$\frac{A}{(s + a)^2}$	$At e^{-at}$	
16.	$\frac{A\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$	$\frac{A\omega_n e^{-\zeta\nu t}}{\sqrt{1 - \zeta^2}} \sin(\omega_n \sqrt{1 - \zeta^2} t)$	Second-order system, free response ($\zeta < 1$)
17a.	$\frac{A}{s(ts + 1)}$	$A(1 - e^{-\nu t})$	First-order system response to a step input
17b.	$\frac{A}{s(s + a)}$	$\frac{A}{a} (1 - e^{-at})$	
18a.	$\frac{A}{s^2(\tau s + 1)}$	$A\tau \left(e^{-\nu t} + \frac{t}{\tau} - 1 \right)$	First-order system response to a ramp input
18b.	$\frac{A}{s^2(s + a)}$	$\frac{A}{a^2} (e^{-at} + at - 1)$	

$$V_{\text{out}}(t) =$$

$$V_{\text{out}}(t = 0 +) =$$
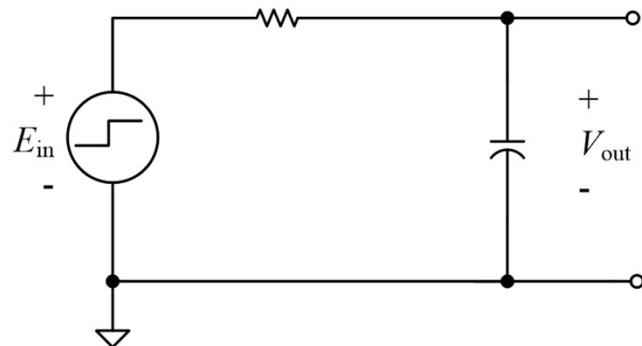
$$V_{\text{out}}(t \rightarrow \infty) =$$




RC Circuit – Response to 5 V step

$$V_{\text{out}}(s) =$$

$$V_{\text{out}}(t) =$$

clc
clear

s=tf('s')
R=
C=
tau=
Ein=

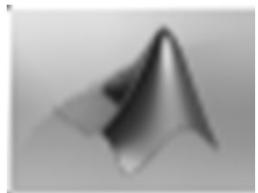

G=
Vout=

ltiview(Vout)

TABLE A-1 LAPLACE TRANSFORMS

No.	$F(s)$	$f(t)$	Comments
1.	1	$\delta(t)$	Unit impulse
2.	$\frac{A}{s}$	$A(t) = \begin{cases} 0 & t < 0 \\ A & t \geq 0 \end{cases}$	Step
3.	$\frac{1}{s}$	$U(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$	Unit step